
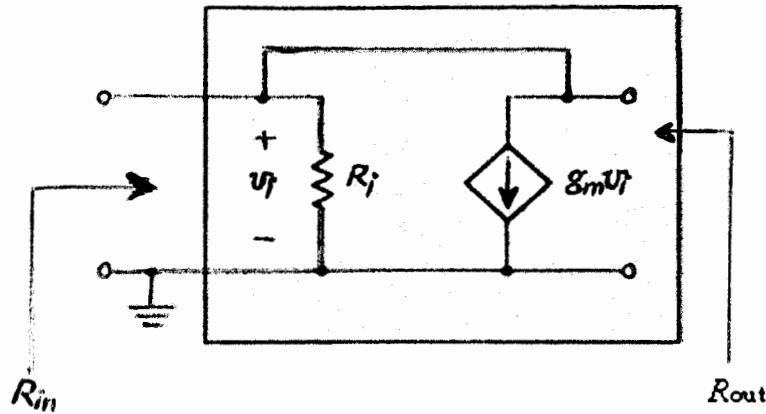


※ 考生請注意：本試題可使用計算機

 
1. (a) Find the input and output resistances. Notice that when determining R_{out} , v_T should be removed (or shorted). (10 分)



- (b) Find the Thevenin and Norton equivalent circuits between terminals 1 and 2. (5 分)



 
2. (1) Determine the output resistance of the Wilson MOS mirror. Note that output resistances of MOS, r_o , cannot be ignored. (10 分) (2) Determine the current transfer ratio. Note that output resistances of MOS, r_o , can be ignored. (10 分)



(背面仍有題目，請繼續作答)

※ 考生請注意：本試題可使用計算機

 3. A commercial $\mu A741$ is employed in the noninverting configuration, $R_1 = 1\text{ k}\Omega$, $R_2 = 9\text{ k}\Omega$, and $C_2 = 100\text{ nF}$. The op amp has its open-loop gain (or transfer function) as $A(s)$.




(a) If the op amp is ideal and has an infinite open-loop gain, $A(s) = \infty$, find the closed-loop gain, $G(s)$. (5 分)

(b) If the op amp is ideal except that its open-loop gain is finite, $A(s) = \frac{10^4}{1 + \frac{s}{2\pi \times 100}}$, find the closed-loop gain, $G(s)$. (5 分)


(c) Plot the magnitude plot of $G(s)$ in (a). (5 分)

 4. This is a limiter circuit. All diodes in forward region can be represented by a constant-voltage drop of 0.7V. The specified zener voltage 8.2 V is measured in breakdown region with a current of 10 mA and that $r_z = 100\ \Omega$, represent the zener by a piecewise-linear model. Sketch and clearly label the transfer characteristic for $-20\text{ V} \leq v_i \leq 20\text{ V}$ by considering three cases (a) $I_{ZK} = 0\text{ mA}$ (5 分) (b) $I_{ZK} = 20\text{ mA}$ (5 分) (c) $I_{ZK} = 400\text{ mA}$. (5 分)



※ 考生請注意：本試題可使用計算機

 5. Design the circuit to obtain a dc voltage of +0.2V at each of the drains of Q_1 and Q_2 when $v_{G1} = v_{G2} = 0V$. Operate all transistors at $V_{ov}=0.2V$ and assume that for the process technology in which the circuit is fabricated, $V_{tn}=0.5V$ and $\mu_n C_{ox} = 250 \mu A/V^2$. Neglect channel-length modulation. (1) Determine the values of R , R_D , and the W/L ratios of Q_1 , Q_2 , Q_3 , and Q_4 . (12 分) (2) What is the input common-mode voltage range for your design? (8 分)



6. For the feedback amp, if the op amp has an open-loop gain μ and a very large input resistance, find $A_f \equiv I_o/V_s$, A , and $\beta \equiv V_f/I_o$. (15 分)

