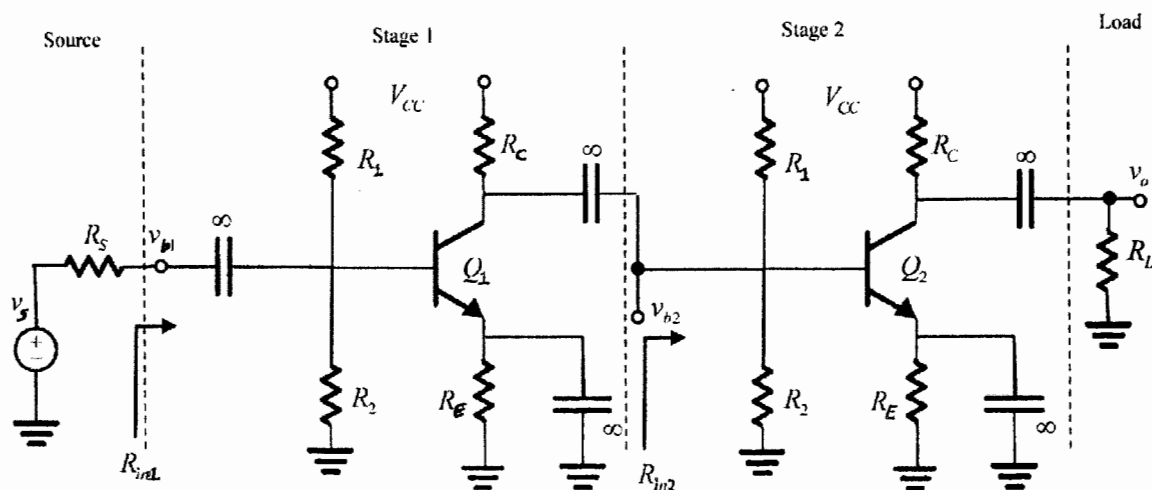


※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。請依題號順序作答。

1. Mark each of the following statements True (T) or False (F). (Need NOT to give reasons.) (20 分)

- (a) When performing DC analysis, the capacitors including coupling, bypass, and internal parasitic capacitors should be opened circuit because their impedances are zero.
- (b) When performing low-frequency response analysis, the coupling and bypass capacitors should be analyzed, while internal parasitic capacitors should be shorted circuit.
- (c) When performing high-frequency response analysis, the internal parasitic capacitors should be analyzed, while coupling and bypass capacitors should be opened circuit.
- (d) The ideal voltage amplifier has infinite input resistance, zero output resistance, and infinite voltage gain.
- (e) The common drain amplifier can be used to obtain the bulk of the voltage gain.
- (f) The input stage of an operational amplifier typically uses the differential amplifier to reject the common-mode signals.
- (g) Feedback can be used to extend the bandwidth of an amplifier.
- (h) Feedback cannot desensitize the closed-loop gain introduced by the variation of the open-loop gain of the basic amplifier.
- (i) The current mirror is typically employed to bias the discrete-component circuits.
- (j) The saturation region of an MOS is used to amplify the small signals.


2. The amplifier consists of two identical common-emitter amplifiers connected in cascade. $V_{CC} = 15V$, $R_1 = 100K\Omega$, $R_2 = 47K\Omega$, $R_E = 3.9K\Omega$, $R_C = 6.8K\Omega$, $\beta = 100$ and $V_T = 25\text{ mV}$. Neglect the output resistance r_{o1} and r_{o1} for both transistors. (a) Determine the DC collector current and collector voltage of each transistor. (4 分) (b) Find R_{in1} and v_{b1}/v_s for $R_S = 5K\Omega$. (4 分) (c) Find R_{in2} and v_{b2}/v_{b1} . (4 分) (d) For $R_L = 2K\Omega$, find v_o/v_{b2} . (4 分) (e) Find the overall voltage gain v_o/v_s . (4 分)




(背面仍有題目，請繼續作答)

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

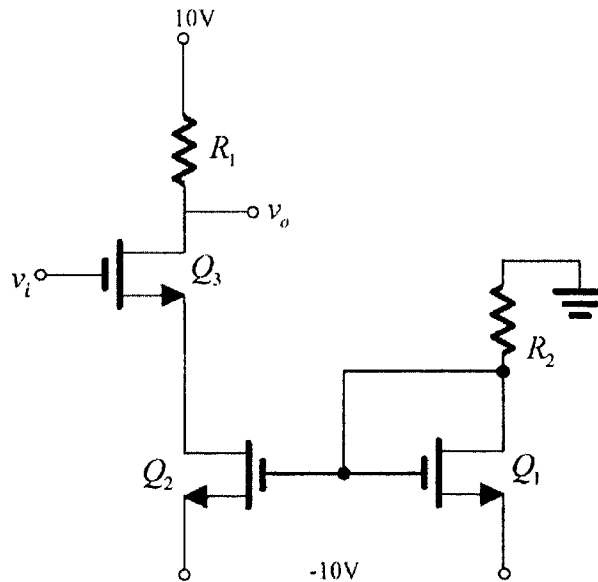3. Consider the circuit shown below. All transistors are identical with $\frac{1}{2}k'_n\left(\frac{W}{L}\right) = 1 \text{ mA/V}^2$, $V_t = 2\text{V}$, and $V_A = 1/\lambda = \infty$. $R_1 = 500\Omega$ and $R_2 = 250\Omega$. (a) Determine the bias drain current of Q_3 . (6 分) (b) Determine the small-signal voltage gain. (8 分) (c) What is the allowed range of v_i for Q_1 , Q_2 and Q_3 operating in the saturation region? (6 分)



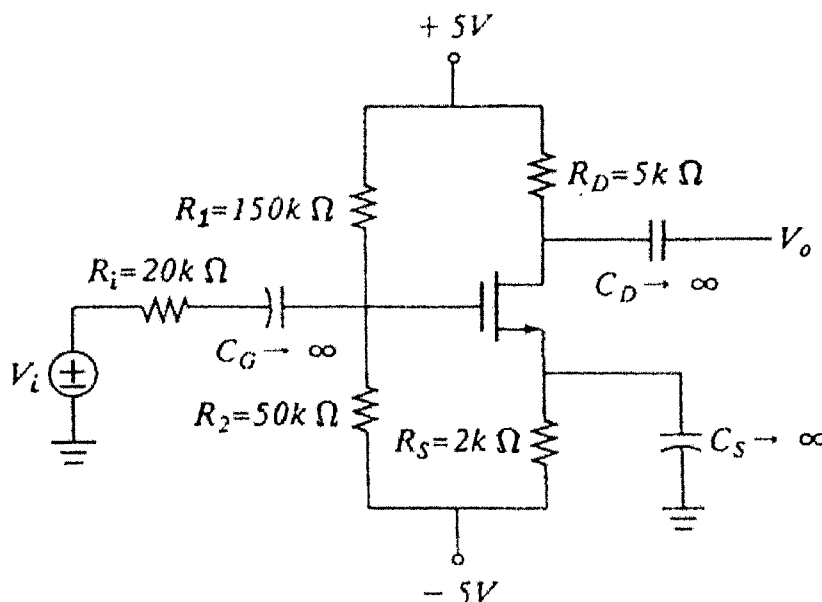4. For the circuit shown below, the transistor has $\frac{1}{2}k'_n\left(\frac{W}{L}\right) = 1 \text{ mA/V}^2$, $V_t = 0.8 \text{ V}$, $r_o = \infty$, $C_{gs} = 2 \text{ pF}$, and $C_{gd} = 0.2 \text{ pF}$. Determine: (a) the midband voltage gain V_o/V_i (10 分), and (b) the upper 3-dB frequency, f_H in Hz. (10 分). Hint: You can apply Miller's theorem and, then use the open-ckt time constant.



※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

5. The transistors Q_1 and Q_2 have $h_{fe} = 80$ and $V_T = 25 \text{ mV}$, and are biased at $I_{c1} = 0.2 \text{ mA}$ and $I_{c2} = 8 \text{ mA}$, respectively. (a) What are the feedback β and the **current gain** of basic amplifier A ? (10 分)
 (b) Find $A_f \equiv V_o / V_s$ and R_{in} . (10 分)

