
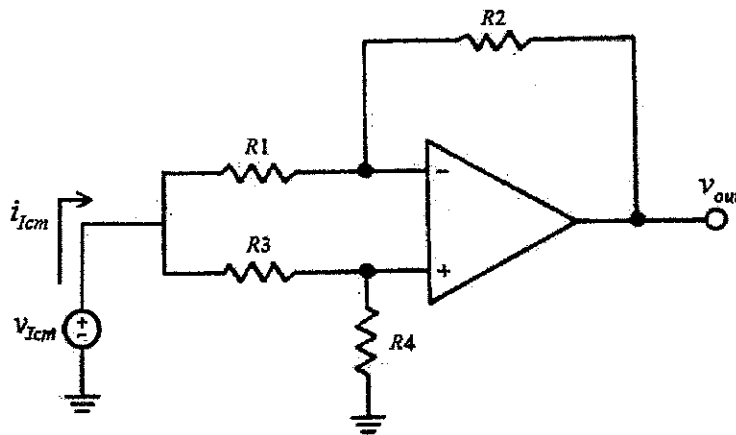


※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。請依題號順序作答。

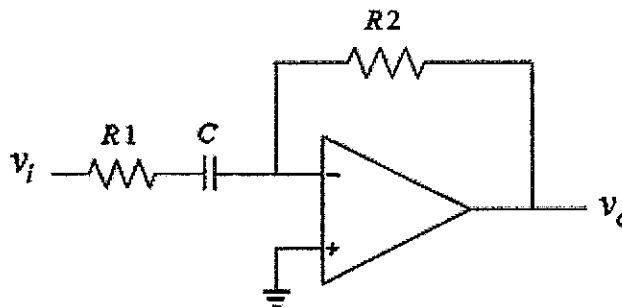
1. A device is characterized by its current i_D (mA) and voltage v_D (V) as $i_D = K(1+v_D)^3$, where $K = 1 \text{ mA/V}^3$. (a) Find its small-signal equivalent model (10 pt.). (b) If the DC voltage $V_D = 2 \text{ V}$, find the DC current I_D and the transconductance g_m . (10 pt.)
2. In the following circuit, (a) if $R_1 = 1 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, $R_3 = 4 \text{ k}\Omega$, and $R_4 = 2 \text{ k}\Omega$, find v_{out} expressed by v_{Icm} (5 pt.); (b) if $R_1 = 1 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, $R_3 = 4 \text{ k}\Omega$, and $R_4 = 2 \text{ k}\Omega$, find $R_{Icm} \equiv \frac{v_{Icm}}{i_{Icm}}$ (5 pt.); (c) if $R_1 = R_3 = 1 \text{ k}\Omega$ and $R_2 = R_4 = 2 \text{ k}\Omega$, find v_{out} expressed by v_{Icm} (5 pt.); (d) if $R_1 = R_3 = 1 \text{ k}\Omega$ and $R_2 = R_4 = 2 \text{ k}\Omega$, find $R_{Icm} \equiv \frac{v_{Icm}}{i_{Icm}}$ (5 pt.).



3. The following circuit performs the high-pass, single-time-constant function. Such a circuit is known as a first-order high-pass active filter. (a) Design the circuit to obtain a high-frequency input resistance of $100 \text{ k}\Omega$, a high-frequency gain of 40 dB , and a 3-dB frequency of 100 kHz . (15 pt.) (b) At what frequency does the magnitude of the transfer function reduce to unity? (5 pt.)



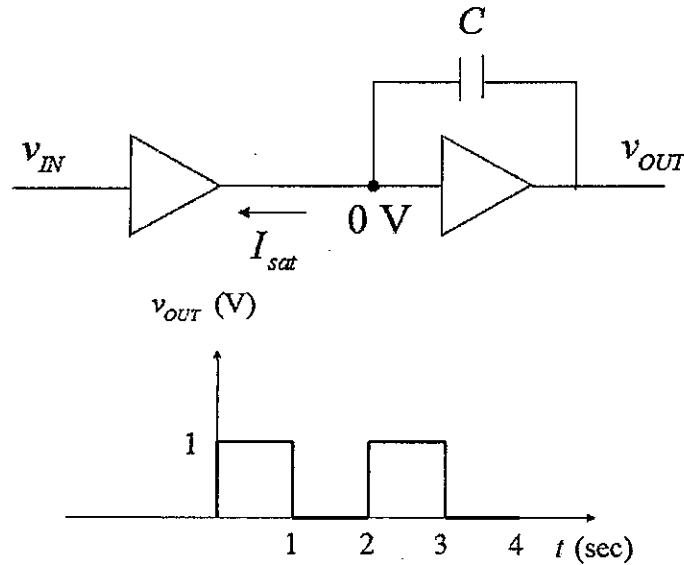4. The figure shows a two-stage amp, the 1st stage saturates owing to the large input voltage, where $I_{sat} = 0.1 \text{ mA}$ and $C = 100 \mu\text{F}$. (a) Find the slew rate. (5 pt.) (b) If the ideal output is a square wave shown below, plot the real output waveform which is distorted by the slew rate. (10 pt.)



5. For the circuit shown below, assume $V_t = 1.5 \text{ V}$, $V_A = \infty \text{ V}$, and $k'_n \left(\frac{W}{L}\right) = 0.25 \text{ mA/V}^2$. Find (a) DC operating point. (5 pt.) (b) Its small-signal voltage gain. (5 pt.) (c) The amplitude of the largest allowable input signal and the minimum allowable v_{DS} , i.e., $v_{DS,min}$. (5 pt.) (d) Please change the resistance of R_D such that the DC drain voltage $V_D = \frac{V_{DD} + v_{DS,min}}{2}$, where $v_{DS,min}$ denotes the minimum allowable v_{DS} obtained in (c). (5 pt.) (e) Also, find the amplitude of the largest allowable input signal and the new minimum allowable v_{DS} , i.e., $v'_{DS,min}$ in this case again. (5 pt.)

