 


※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。


1. Mark each of the following statements True (T) or False (F). (Need NOT give reasons.) (20 pt.)
 - (a) The typical diode can never work in the breakdown region except the Zener diode.
 - (b) When typical diodes work in the breakdown region, they will definitely break down.
 - (c) Diodes can be applied for the rectifier and limiter circuits.
 - (d) The small-signal model of a typical diode in the forward region is a resistance.
 - (e) The small-signal model of the Zener diode in the breakdown region is a DC voltage plus a resistance.
 - (f) The power used for the amplification of a signal mainly comes from the AC power.
 - (g) The input terminals of an OP AMP are virtual shorted because their input currents are zero.
 - (h) If we need a closed-loop gain which is finite and predictable, the very high gain of an OP AMP makes it impossible to use by itself.
 - (i) When designing an amplifier, there typically exists a tradeoff between gain and bandwidth.
 - (j) The supply electricity of the wall outlet in Taiwan is 110 V, which represents the peak amplitude of the electricity.

2. A transmission line has a voltage drop of 10% and resistance of 10Ω . (a) Find the root-mean-square (rms) amplitude of the current flowing through the transmission line for AC supply of 200 V peak amplitude. (b) Find the line loss, i.e., the power consumed in the transmission line. (10 pt.)

3. The transistors in the circuit have $\beta = 100$ and $|V_A| = 50 \text{ V}$. Find R_{in} and the overall voltage gain $A_v \equiv v_o / v_{sig}$. (20 pt.)



 4. In the circuit, Q_1 and Q_2 have following parameters: $k'_n \left(\frac{W}{L}\right)_1 = 2 \text{ mA/V}^2$, $k'_n \left(\frac{W}{L}\right)_2 = 0.2 \text{ mA/V}^2$, $V_{t1} = V_{t2} = 1 \text{ V}$, and $\lambda = 0$. Find (a) V_{GG} that makes V_{DS2} of Q_2 be 4 V. (b) $A_v \equiv \frac{v_o}{v_i}$. (c) R_o . (d) The maximum allowable input amplitude of v_i . (Hint: Besides saturation, you must also guarantee voltages at all nodes are not larger than $V_{DD} = 9 \text{ V}$.) (30 pt.)



5. A MOS differential pair with the drain resistors R_D implemented using diode-connected PMOS transistors, Q_3 and Q_4 , as shown below. Let Q_1 and Q_2 be matched, and Q_3 and Q_4 be matched as well. Assume $g_{m1} = g_{m2} = g_{m3} = g_{m4} = 1 \text{ mA/V}$ and $r_{o1} = r_{o2} = r_{o3} = r_{o4} = 10 \text{ k}\Omega$, find the differential gain $A_d \equiv \frac{v_o}{v_{id}}$. (20 pt.)

