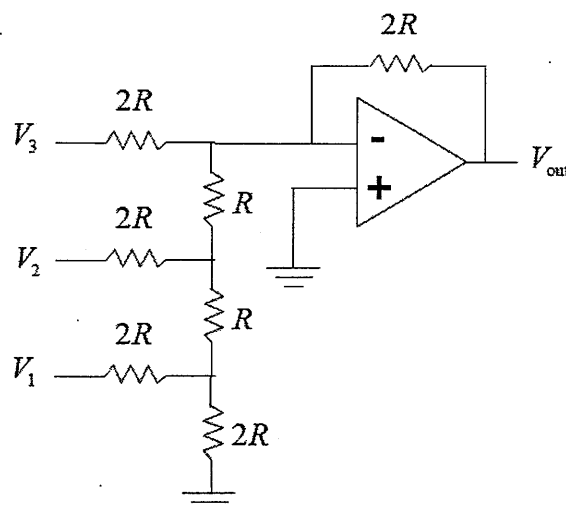


※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. Mark each of the following statements True (T) or False (F). (Need NOT give reasons.) (20 pt.)


- (a) Provided that the power supplied by the power plant is the same, while the supplied voltage changes from 350000 V to 175000 V. Assuming that the transmission line obeys the Ohm's law, the power dissipated in the transmission line reduces to a factor of 0.25.
- (b) The small signal model of a Zener diode in the breakdown region is a DC voltage plus a resistor.
- (c) The large signal model of a typical diode in the forward region can be approximated as a DC voltage plus a resistor.
- (d) The input currents of ideal amplifiers are 0 because their open-loop gains are infinite.
- (e) Typical diodes can function in the breakdown region irrespective of the current flowing through it.
- (f) Differential amplifier can reject the common-mode input under all conditions.
- (g) Low-pass single-time-constant circuits mean that only signals with low amplitudes can be passed (or amplified) to the output.
- (h) One of the advantages of a differential amplifier is that DC coupling can be applied in it.
- (i) Doping intrinsic silicon with impurity atoms like a trivalent element forms  $n$  type semiconductor.
- (j) At room temperature, there are no free electrons and holes in intrinsic silicon.

2. (a) Find  $V_{out}$ , when  $V_1 = V_2 = V_3 = 5$  V. (b) Find  $V_{out}$ , when  $V_1 = V_3 = 5$  V and  $V_2 = 0$  V. (20 pt.)



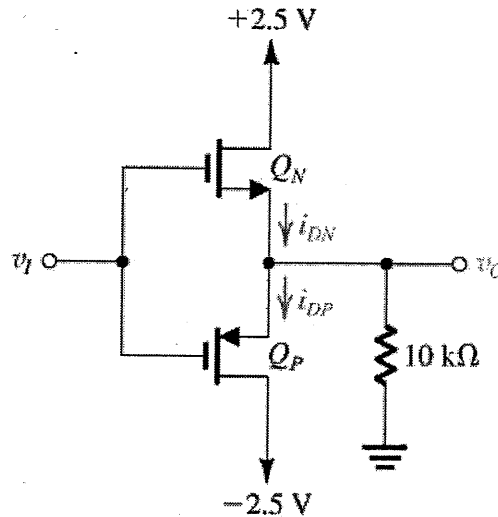
3. The NMOS and PMOS transistors are matched with  $k'_n \left(\frac{W}{L}\right)_n = k'_p \left(\frac{W}{L}\right)_p = 1 \text{ mA/V}^2$  and  $V_{tn} = -V_{tp} = 1 \text{ V}$ .

Besides,  $\lambda = 0$  for both devices. Find  $i_{DN}$ ,  $i_{DP}$ , and  $v_o$  for (a)  $v_i = 0 \text{ V}$  and (b)  $+2.5 \text{ V}$ . (20 pt.)



4. (a) Consider the dc bias. Neglect the base current of  $Q_2$ . Assume the dc bias current in  $Q_1$  is  $100 \mu\text{A}$ , find the dc bias current in  $Q_2$ . (Assume  $|V_{BE}| = |V_t| = 0.7 \text{ V}$ ,  $\mu_n C_{ox} (W/L) = 2 \text{ mA/V}^2$ )

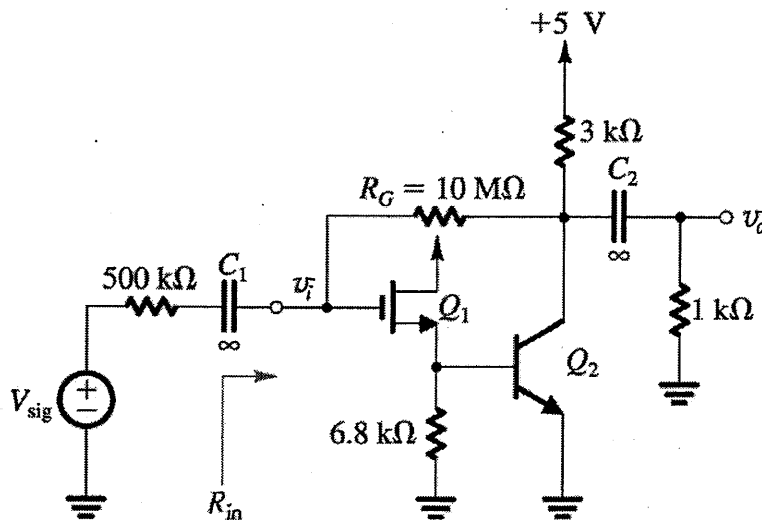(b) Determine the voltage gain  $A_v = v_o / v_i$ . For this purpose you can neglect  $R_G$ . (20 pt.)



5. For the circuit below, find the overall voltage gain  $v_o/v_i$  with  $g_{m1}=g_{m2}=5\text{mA/V}$  and neglect  $r_o$ . (20 pt.)

