
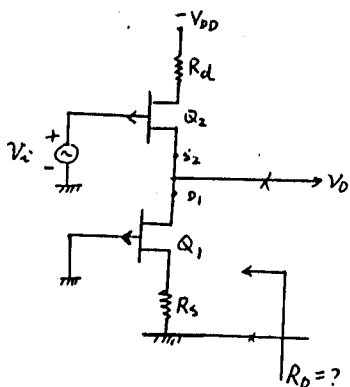


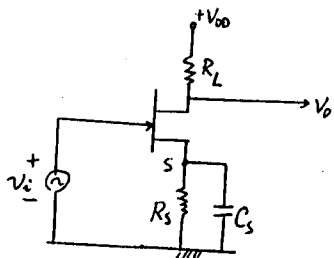(←) In the following circuit, two FETs are identical with parameters μ , r_d and g_m . Please find $A_v \cong \frac{v_o}{v_i} = ?$ and output impedance $R_o = ?$




(⇒) For the circuit shown, please analyze the effect of a source bypass capacitor C_s on low frequency response. Please find $A_v(s) \cong \frac{v_o(s)}{v_i(s)}$ and plot the idealized Bode magnitude plot.



(⇨) The following circuit is a bootstrapped emitter-follower. Please use the approximate model of the transistor and neglect the reactances of capacitors.

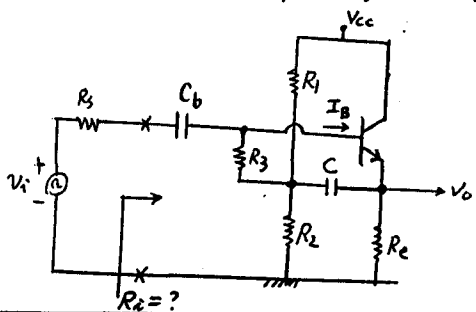- (a) For dc-analysis, please find $I_B = ?$
- (b) For ac-analysis, please find $R_i = ?$



(四) (i) For Fig. (a), please use the approximate model for the transistor to obtain the lower 3-dB frequency $f_L = ?$

(ii) In Fig. (b), please find $A_v(s) \cong \frac{v_o(s)}{v_i(s)} = ?$

(iii) please draw a complete circuit of astable multivibrator to generate an unsymmetrical square-wave.

(iv) what is the circuit in Fig. (c)?

(v) what is the circuit in Fig. (d)?

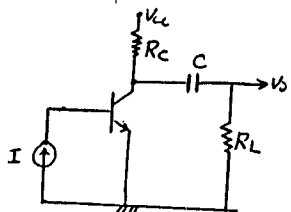


Fig. (a)

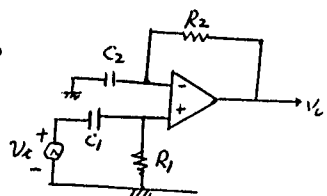


Fig. (b)

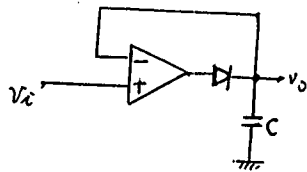


Fig. (c)

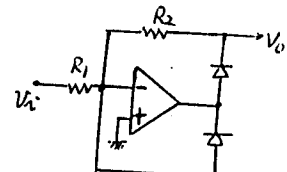


Fig. (d)

(五) (i) For Fig. (a), please find $R_i = ?$

(ii) For Fig. (b), please verify that J-K flip-flop truth table is satisfied by the difference equation $Q_{n+1} = J_n \bar{Q}_n + \bar{K}_n Q_n$ where $Q_n \cong$ the present state $Q_{n+1} \cong$ the next state

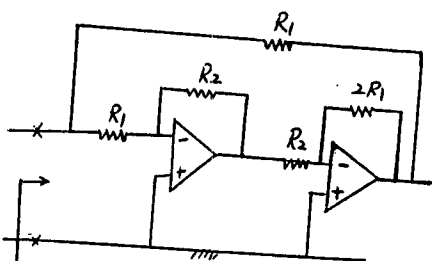


Fig. (a)

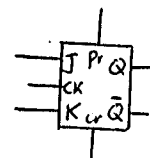


Fig. (b)