

1. For the circuit in Fig. 1(a) and Fig. 1(b), determine the output  $v_o$ . (20%)

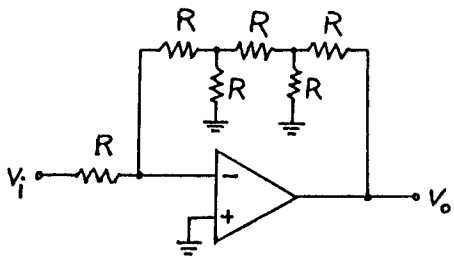


Fig. 1(a)

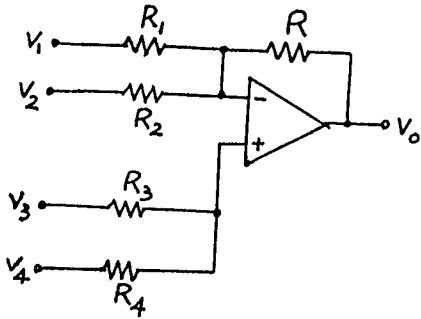


Fig. 1(b)

2. A circuit shown in Fig. 2, the parameters of the JFET are:  $g_m = 1 \text{ mS}$ ,  $r_d = 40 \text{ k}\Omega$ ,  $C_{gs} = 5 \text{ pF}$ ,  $C_{gd} = 1 \text{ pF}$  and  $C_{ds} = 1 \text{ pF}$ . Determine the approximate value of the upper 3-dB frequency. (20%)

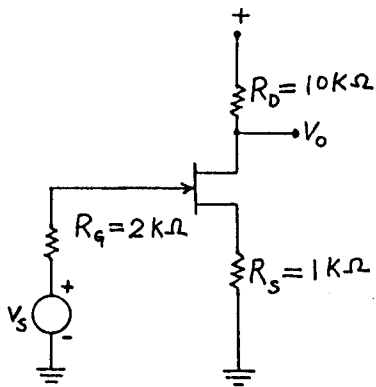


Fig. 2

3. An astable multivibrator circuit is shown in Fig. 3. Explain its operation and determine the frequency of the output  $v_o$ . (20%)

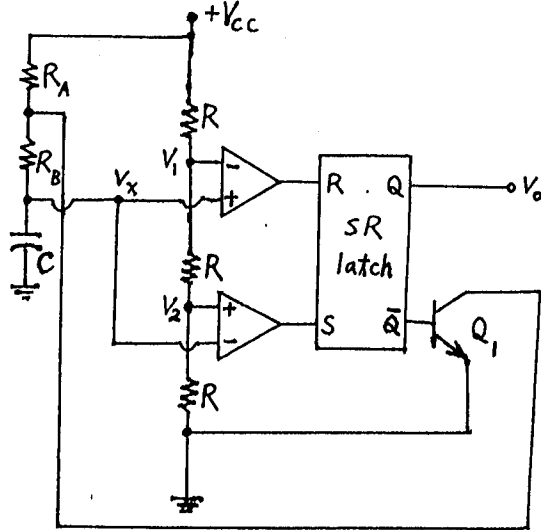


Fig. 3

4. For the circuit in Fig. 4, assuming all transistors to be identical with  $\beta$  infinite, and keeping the current in each junction the same.

- Derive an expression for the output current  $I_o$ . (5%)
- What must the relationship of  $R_E$  to  $R$  be? (5%)
- For  $V_{CC} = 15 \text{ V}$ , and assuming  $V_{BE} = 0.7 \text{ V}$ , determine  $R_E$  and  $R$  to obtain an output current of  $1 \text{ mA}$ . (5%)
- What is the lowest voltage that can be applied to the collector of  $Q_3$ ? (5%)

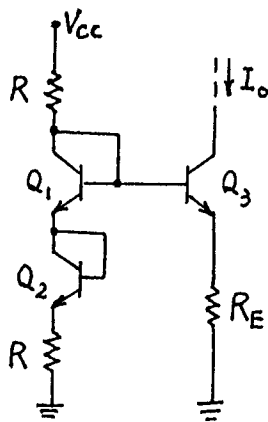


Fig. 4

5. The BJT in the circuit shown in Fig. 5 begins to conduct at  $v_{BE}=0.7$  V and is fully conducting at  $v_{BE}=0.8$  V. The same applies to  $D_7$ . The Schottky diodes have a voltage drop of 0.5 V.
- (a) What is the logic function performed? (6%)
- (b) Find the noise margins. (8%)
- (c) Find the current drawn from the supply when A is high, B is high, and C is low. (6%)

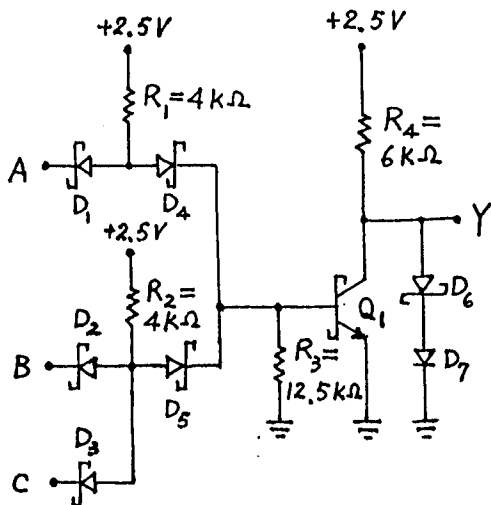


Fig. 5