

1. A D/A converter is shown in Fig. 1.

- (a) Show that the current I drawn from V_r is a constant independent of the digital word. Explain why propagation-delay time transients are eliminated with this system (6%)
- (b) What the switch current and V_o if the MSB is 1 and all other bits are zero? (4%)
- (c) Repeat (b), assuming that the next MSB is 1 and all other bits are zero. (5%)
- (d) Calculate V_o for all bits are 1. (5%)

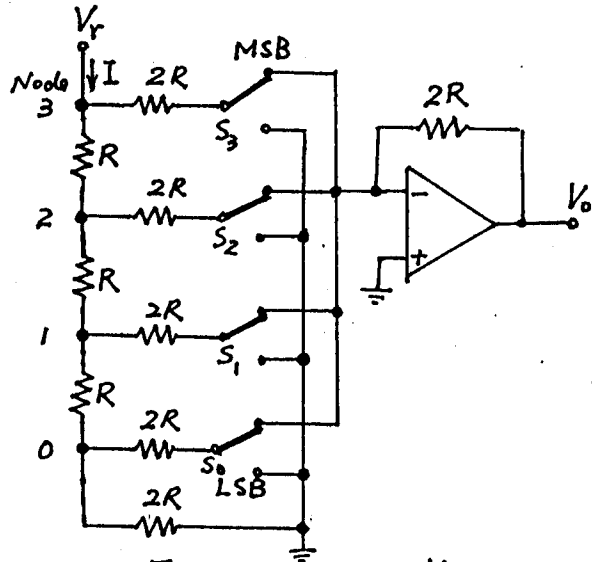


Fig. 1

2. A circuit shown in Fig. 2 uses a transistor having $\beta_F = 100$ and parameter values $R_C = 0.5 \text{ k}\Omega$, $R_E = 1.0 \text{ k}\Omega$, $R_B = 44 \text{ k}\Omega$, $V_{CC} = 15 \text{ V}$, $V_{EE} = -15 \text{ V}$, and $V_{BB} = 0$.

- (a) Determine V_{o1} and V_{o2} . (8%)
- (b) Determine the value of V_{BB} which just barely saturates the transistor. (12%)

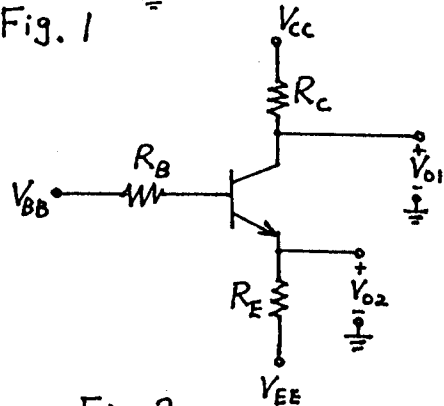


Fig. 2

3. A ECL OR gate shown in Fig. 3, assume that all transistors have $V_{BE(ON)} = 0.75 \text{ V}$ and all base currents are negligible, and all diodes have $V_D = 0.75 \text{ V}$.

- (a) Calculate the value of V_r . (4%)
- (b) Determine the logic levels, $V(1)$ and $V(0)$. (8%)
- (c) Calculate the noise margins, NM_H and NM_L . (8%)

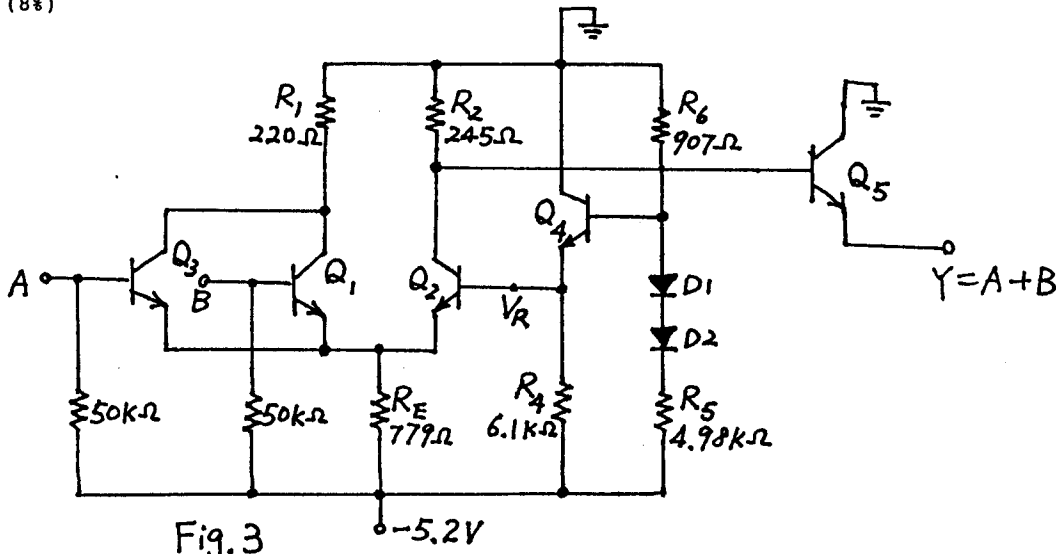


Fig. 3

4. A triangle-wave generator is shown in Fig. 4.

- (a) Calculate the peak-to-peak amplitude of the triangle wave. (10%)
- (b) Calculate the oscillation frequency of the triangle wave if $V_S \neq 0$. (10%)

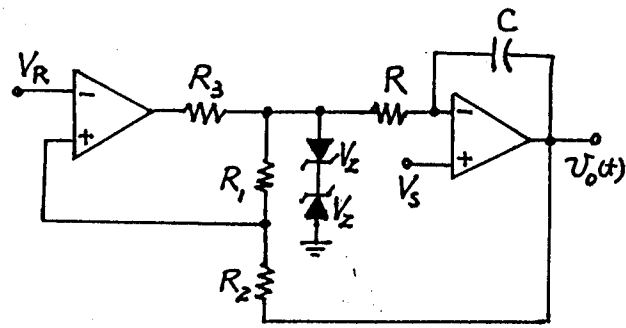


Fig. 4

5. A circuit is shown in Fig. 5. Transistor Q_1

has $r_{d1} = 10 \text{ k}\Omega$ and $g_{m1} = 3 \text{ mS}$; Q_2 has $r_{d2} = 15 \text{ k}\Omega$ and $g_{m2} = 2 \text{ mS}$.

- (a) Find the gain V_o/V_2 for $V_1 = 0$. (8%)
- (b) Find the gain V_o/V_1 for $V_2 = 0$. (8%)
- (c) For $v_1 = 5 \sin \omega t$ and $v_2 = -2.5 \sin \omega t$, find v_o . (4%)

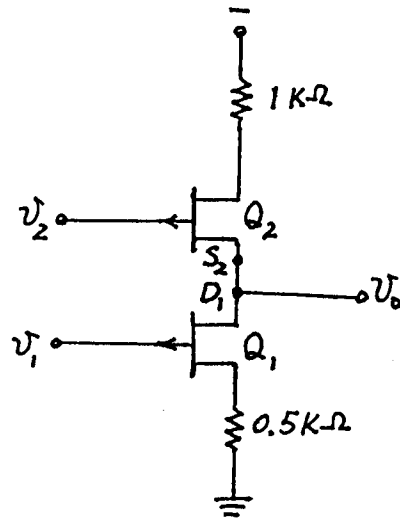


Fig. 5