

1. For the circuit shown in Fig. 1, assume that the two JFETs are matched.

(a) show that the two JFETs to operate in pinch-off (10分) the following two conditions must be satisfied.

$$I_D R_S \geq 0.5 |V_p|$$

$$V_{DD} - I_D R_S \geq 1.5 |V_p|$$

(b) For $V_{DD} = 10V$, $|V_p| = 2V$, and $I_{DSS} = 4mA$, design (10分) R_S and R_D so that $V_{D_{G1}} = |V_p|$ and $V_{D_{G2}} = 2|V_p|$.

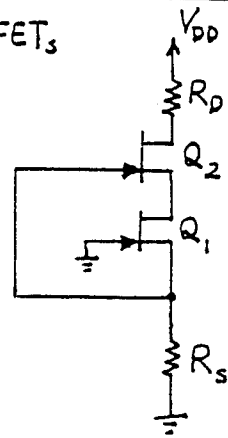


Fig. 1

2. Sketch and clearly label the transfer characteristic of the circuit in Fig. 2, for $-20V \leq v_i \leq 20V$. assume that the diodes can be represented by a piecewise-linear model with $V_{D0} = 0.65V$ and $r_D = 25\Omega$. Assuming that the specified zener voltage (6.2V) is measured at a current of 10mA at that $r_z = 20\Omega$, represent the zener by a piecewise-linear model. (15分)

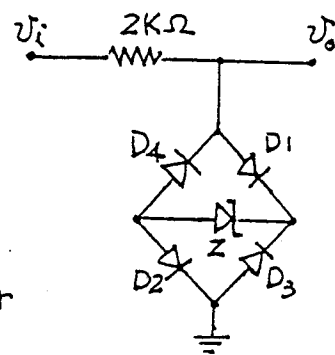


Fig. 2

3. The transistors in the circuit of Fig. 3 have $\beta_0 = 100$, $V_A = 100V$, $C_u = 0.2PF$. At a bias current of $100\mu A$, $f_T = 400MHz$. (Note that the bias details are not shown)

Find an estimate of the upper 3-dB frequency f_H . (15分)

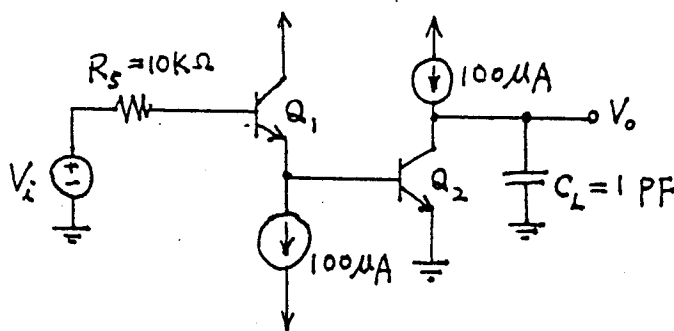


Fig. 3

4. For the circuit in Fig. 4, assume that the diodes has a constant 0.7-V drop when conducting and that the OP amp saturates at $\pm 15V$.

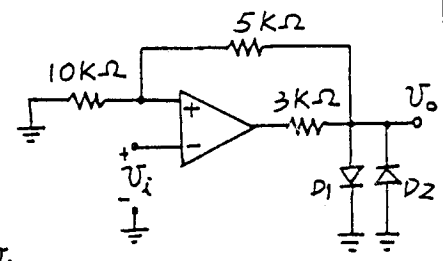


Fig. 4

- (5分) (a) Sketch and label the transfer characteristic, $U_o - U_i$.
- (5分) (b) What is the maximum diode current?

5. A class AB output stage using a two-diode bias network as shown in Fig. 5, utilizes diodes having the same junction area as the output transistors. Assume that $V_{cc} = 10V$, $I_{bias} = 0.5mA$, $R_L = 100\Omega$, $\beta_N = 50$, $|V_{CEsat}| = 0V$.

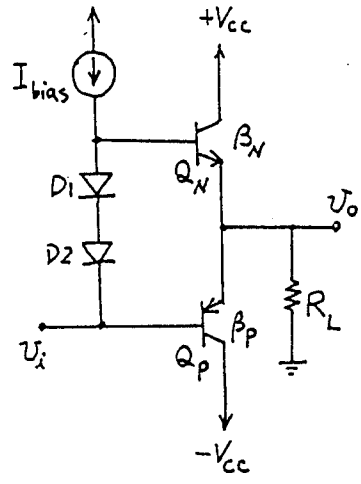


Fig. 5

- (5分) (a) What is the quiescent current?
- (5分) (b) What are the largest possible positive and negative output signal levels?
- (5分) (c) To achieve a positive peak output level equal to the negative peak level, what value of β_N is needed if I_{bias} is not changed? and
- (5分) (d) what value of I_{bias} is needed if β_N is held at 50?

6. Fig. 6 shows a circuit for a voltage-controlled current source employing series-series feedback through the resistor R_E . (The bias circuit is not shown)

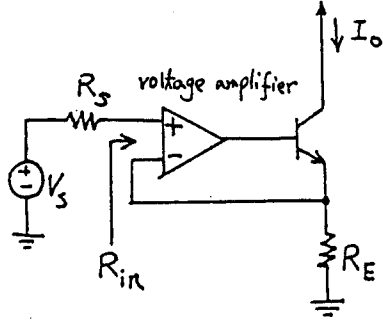


Fig. 6

- (5分) (a) If the loop gain is very large, find the value of R_E to obtain a circuit transconductance (I_o/V_s) of $1mA/V$.

If the voltage amplifier has a differential resistance of $100K\Omega$, a voltage gain of 100, and an output resistance of $1K\Omega$, and if the transistor is biased at a current of $1mA$ and has h_{fe} of 100, and r_o of $100K\Omega$, $R_s = 10K\Omega$.

- (10分) (b) Find the actual value of transconductance (I_o/V_s) realized.
- (5分) (c) Find the input resistance R_{in} .