

請按題目順序作答於答案紙

1. A class B output stage is shown in Fig. 1.
Derive the maximum power-conversion efficiency
and the maximum power dissipation.
(10分)

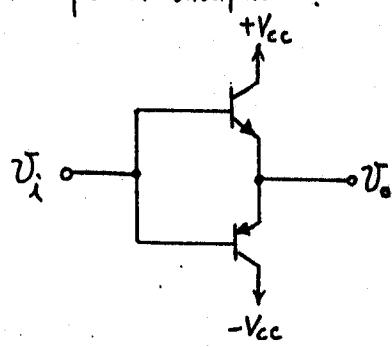


Fig. 1

2. The MOSFETs in the circuit of Fig. 2 are matched, with $K = 25 \text{ mA/V}^2$, and $|V_{t1}| = |V_{t2}| = 2V$.
The resistance $R = 5 \text{ M}\Omega$. For G and D open,
what are the drain currents I_{D1} and I_{D2} ?
For $r_o = \infty$, what is the voltage gain of the
amplifier from G to D?
(10分)

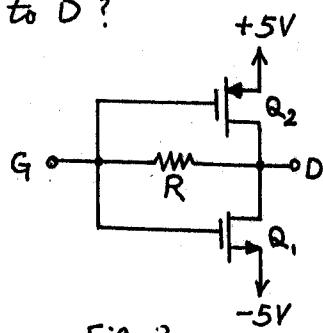


Fig. 2

3. Sketch and label the transfer characteristic
of the circuit in Fig. 3
(10分)

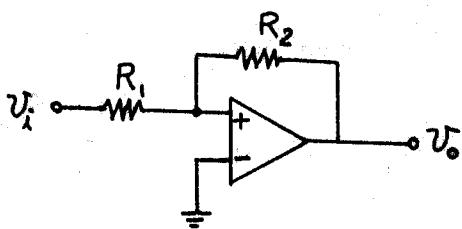


Fig. 3

4. Determine the input impedance $Z_{in}(s)$ of Fig. 4.
(10分)

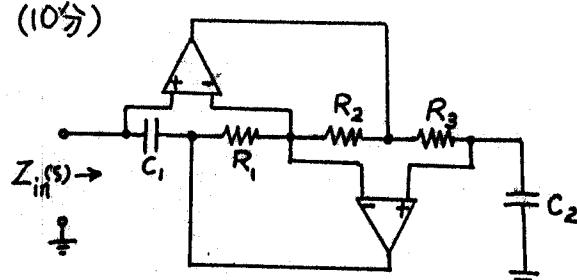


Fig. 4

5. For the circuit of Fig. 5, use the feedback
method to find the voltage gain V_o/V_s .
The op amp has open-loop gain $A = 10^4 \text{ V/V}$,
 $R_{id} = 100 \text{ k}\Omega$, $R_{icm} = \infty$, and $r_o = 1 \text{ k}\Omega$.
(15分)

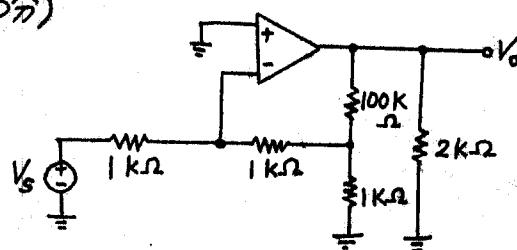


Fig. 5

6. Fig. 6 shows an astable multivibrator.
Derive an expression for the period T
of V_o .
(15分)

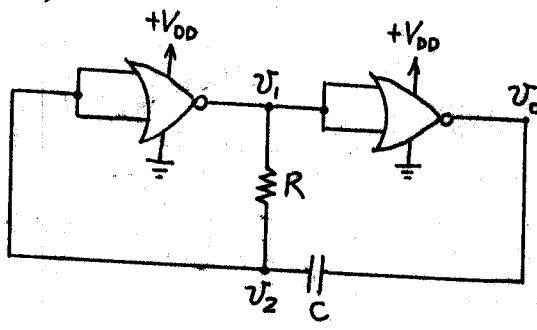


Fig. 6

7. It is required to design a zener shunt regulator (Fig. 7) to provide a regulated voltage of about 10V. The zener diode is specified as follows: $V_z = 10V$ and $R_z = 7\Omega$ for $I_z = 25\text{ mA}$. The raw supply available has a nominal value of 20V but can vary by as much as $\pm 25\%$. The regulator is required to supply a load current of 0 to 20 mA. Design for a minimum zener current of 5 mA.
- Calculate the required value of R .
 - What is the change in V_o expressed as a percentage, corresponding to the $\pm 25\%$ change in V_s ?
 - What is the maximum current that the zener in your design should be able to conduct?

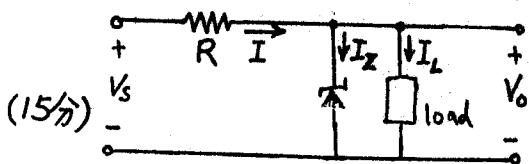


Fig. 7

8. Find the transfer function of a Butterworth filter that meets the following low-pass specifications: $f_p = 10\text{ kHz}$, $A_{max} = 2\text{ dB}$, $f_s = 15\text{ kHz}$, and $A_{min} = 15\text{ dB}$.
- (15分)