

請按題號順序作答 (每題分數 20 分)

1. In the circuit of Fig. 1, the NMOS transistor has $|V_t| = 0.9 \text{ V}$ and $V_A = 50 \text{ V}$, and operates with $V_D = 2 \text{ V}$.

- (a) What is the voltage gain v_o / v_i ?
(b) What do V_{th} and the gain become for I increased to 1 mA?

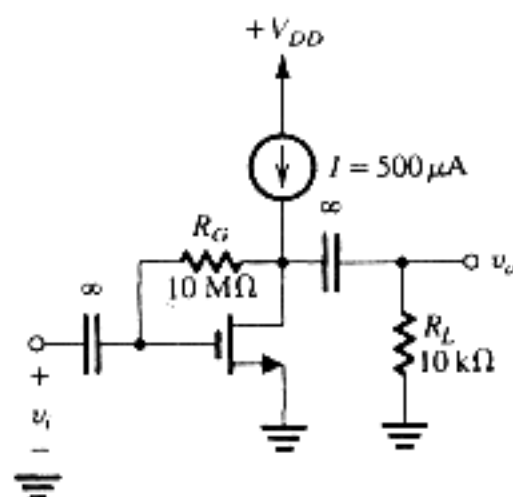


Fig. 1

2. For the differential amplifier shown in Fig. 2, find

- (a) the differential gain,
(b) the differential input resistance,
(c) the common-mode gain, and
(d) the common-mode input resistance.

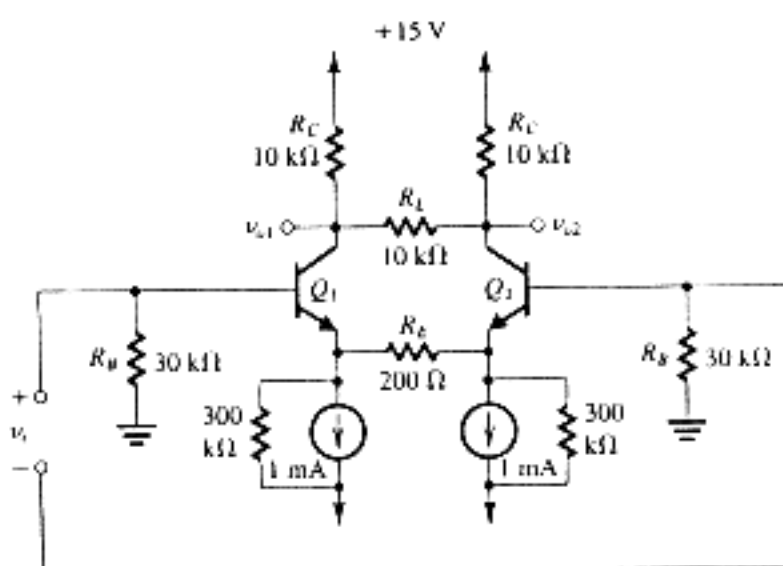


Fig. 2

4. For the circuits in Figs. 4(a) to 4(c), sketch and label the transfer characteristic $v_o - v_i$. Denoting the zener voltages of Z_1 and Z_2 by $V_{Z1} = 6 \text{ V}$ and $V_{Z2} = 4 \text{ V}$ and assuming that in the forward direction the voltage drop is approximately 0.7 V. The diodes are assumed to have a constant 0.7 V drop when conducting. The op amp saturates at $\pm 12 \text{ V}$.

5. Design a Chebyshev filter that meets the following low-pass specifications: $f_p = 3.4 \text{ kHz}$, $f_s = 4 \text{ kHz}$, $A_{\max} = 1 \text{ dB}$, and $A_{\min} = 35 \text{ dB}$. Find the required order N , the poles, and the transfer function $T(s)$.

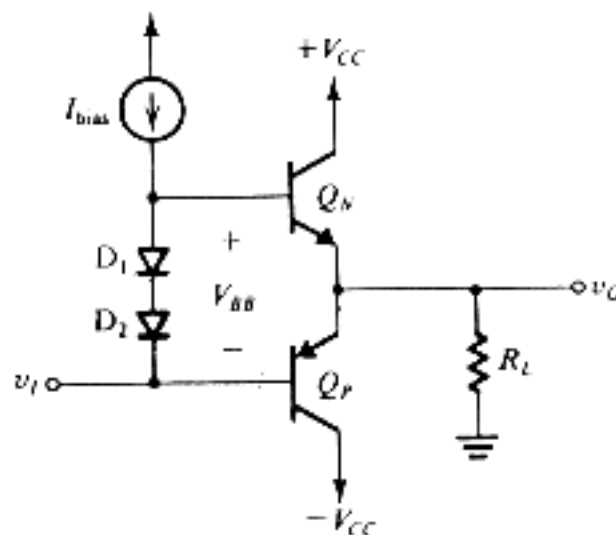


Fig. 3

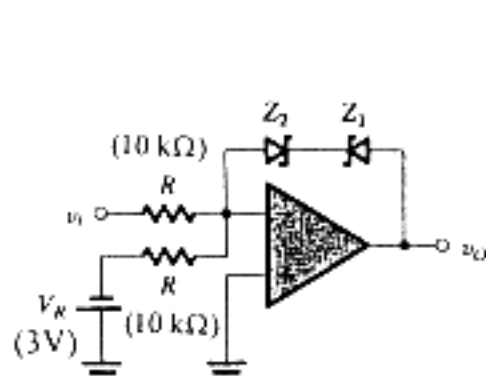


Fig. 4(a)

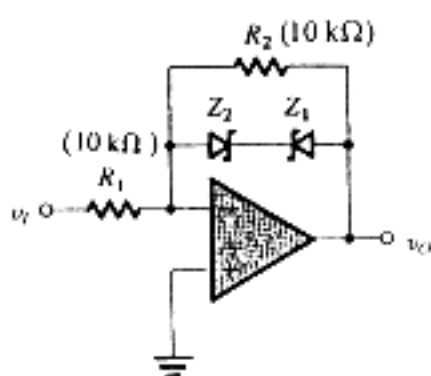


Fig. 4(b)

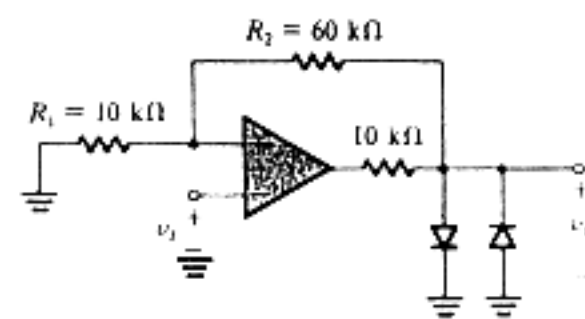


Fig. 4(c)