

- Find and sketch the voltage transfer characteristic of the circuit shown in Fig. 1, assuming that the diodes have a constant 0.7 V drop when conduct. (15 分)
- The CMOS circuit is shown in Fig. 2 for which  $Q_1$  has parameters  $g_{m1}$  and  $r_{o1}$  and  $Q_2$  has  $g_{m2}$  and  $r_{o2}$ . Find  $A_v = V_o/V_s$ . (15 分)
- For the CMOS monostable circuit shown in Fig. 3, sketch  $v_{o1}$ ,  $v_{o2}$ ,  $v_R$  and determine the pulse duration. (15 分)
- A circuit is shown in Fig. 4, determine the value of  $v_o$ . (15 分)
- For the circuit in Fig. 5 in which the transistors have  $V_{BE} = 0.7$  V and  $\beta = 100$ , find  $v_o/v_i$  and  $R_{in}$ . (20 分)
- An amplifier having a low-frequency gain of  $10^3$  and poles at  $10^4$  and  $10^5$  Hz is operated in a closed negative-feedback loop with a frequency-independent  $\beta$ .
  - For what value of  $\beta$  do the closed-loop poles become coincident? At what frequency? (7 分)
  - What is the low-frequency gain corresponding to the situation in (a)? (3 分)
  - What is the value of pole  $Q$  factor corresponding to the situation in (a)? (3 分)
  - If  $\beta$  is increased by a factor of 10, what are the new pole locations? What is the corresponding pole  $Q$  factor? (7 分)

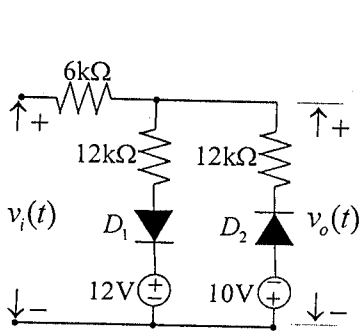


Fig. 1

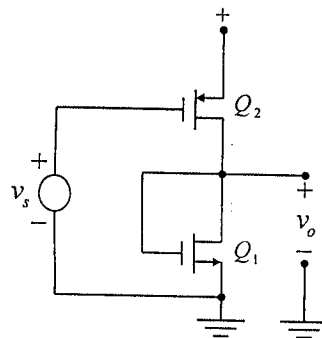


Fig. 2

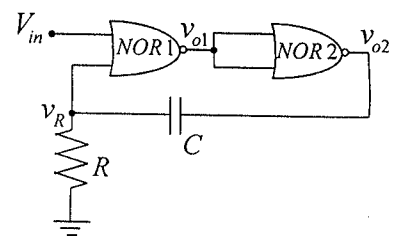


Fig. 3

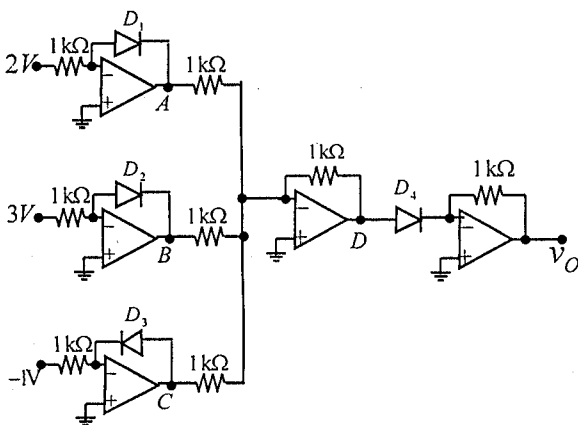


Fig. 4

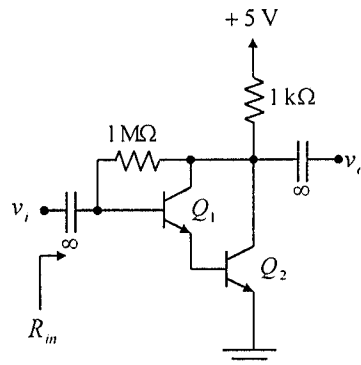


Fig. 5