

請按題目順序作答

1. Consider the class-B output stage shown in Fig. 1. The transistor parameters are $|V_{th}| = 0$ and $k'_n = k'_p = 0.4 \text{ mA/V}^2$. Let $R_L = 5 \text{ k}\Omega$.

- (a) Find the maximum output voltage such that Q_N remains biased in the saturation region. What are the corresponding values of i_L and v_i for this condition? (8分)
- (b) Determine the conversion efficiency for a symmetrical sine-wave output signal with the peak value found in part (a). (8分)

 


Fig. 1

2. Consider the current-to-voltage converter circuit shown in Fig. 2. The input resistance R_f is assumed to be small, the output resistance is $R_o = 0$, and the op-amp gain A is large. The closed-loop transfer function can be written in the form

$$A_f = \frac{v_o}{i_s} = \frac{A}{1 + A\beta}$$

- (a) What is the expression for β . (8分)
- (b) If $A = 5 \times 10^6 \Omega$ and $A_f = 5 \times 10^4 \Omega$, what is the required R . (8分)

 


Fig. 2

3. Find the frequency of oscillation and the R_2/R_1 required for oscillation for the circuit shown in Fig. 3. (16分)

 


Fig. 3

4. For the circuit in Fig. 4(a), utilizing ideal diodes, determine and sketch the output $v_o(t)$ for the input $v_i(t)$ shown in Fig. 4(b). Assume $CR = T$. (16分)

 


Fig. 4(a)

 


Fig. 4(b)

- 5. An amplifier is formed by cascading n identical amplifier stages, each having a high-pass single-time-constant frequency response with a 3-dB frequency f_1 and a low-pass single-time-constant frequency response with a 3-dB frequency f_2 . Find the lower 3-dB frequency and upper 3-dB frequency of the overall amplifier in terms of f_1 , f_2 and n . (18分)
- 6. (a) Sketch a CMOS realization for the function $Y = \overline{A + B(C + DE)}$. (b) Sketch a CMOS logic circuit that realizes the function $Y = ABC + \overline{A} \overline{B} \overline{C}$. (18分)