

1. (a) Figure 1 shows a noninverting amplifier utilizing a single internally-compensated op amp. The gain of the op amp may be expressed as  $A(s) = A_o / (1 + \frac{s}{\omega_o})$ , where  $A_o$  and  $\omega_o$  are the dc gain and 3-dB frequency, respectively. Derive the 3-dB frequency of the noninverting amplifier. (14分)

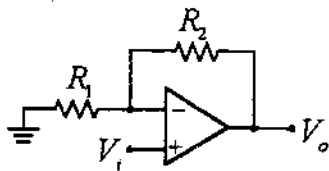


Fig. 1

(b) Redesign the amplifier by cascading three identical noninverting amplifiers. Each noninverting amplifier is the same as Fig. 1. Derive the 3-dB frequency of the overall amplifier. (6分)

2. For the circuit shown in Fig. 2, both diodes are identical, conducting 10 mA at 0.7 V and 100 mA at 0.8 V. In the forward region the  $i_D - v_D$  relationship of the diode is approximated by  $i_D = I_s e^{v_D/nV_T}$ , where  $I_s$  is the saturation current and  $V_T = 25$  mV.

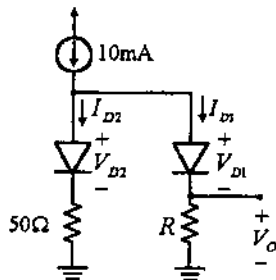


Fig. 2

3. A circuit is shown in Fig. 3. The BJT has  $\beta = 200$  and neglect the effect of  $r_o$ .

(a) Find the dc emitter current,  $g_m$  and  $r_\pi$  of the BJT. (5分)

(b) Replace the BJT with its hybrid- $\pi$  model and determine the input resistance  $R_i$ . (5分)

(c) Determine the voltage gain  $v_o/v_i$ . (10分)

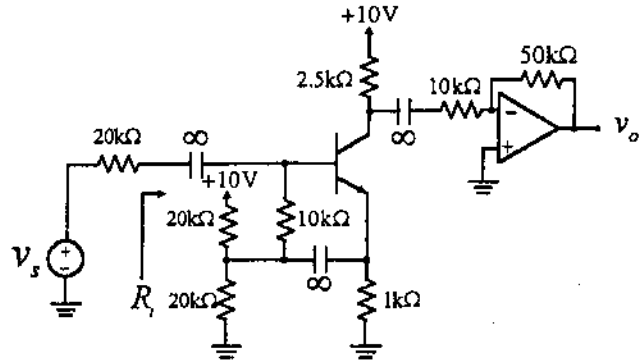


Fig. 3

4. Determine a Butterworth filter transfer function  $T(s)$  that meets the specifications shown in Fig. 4. (20分)

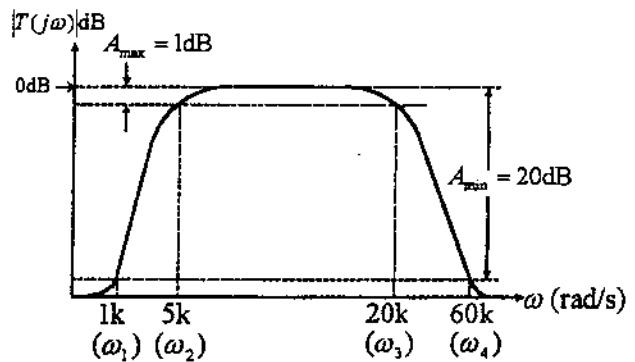


Fig. 4

5. Determine the transfer function  $V_o(s)/V_i(s)$  in Figs. 5(a) and 5(b). (20分)

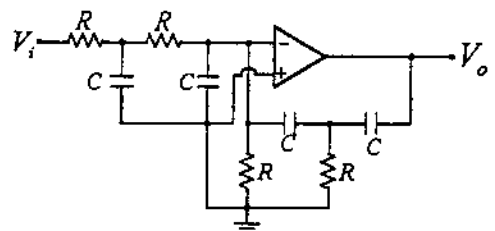


Fig. 5(a)

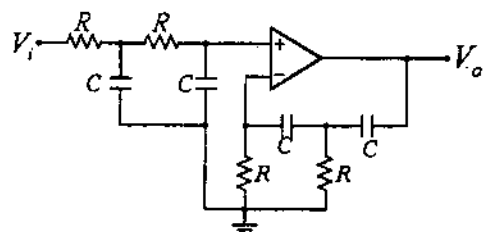


Fig. 5(b)