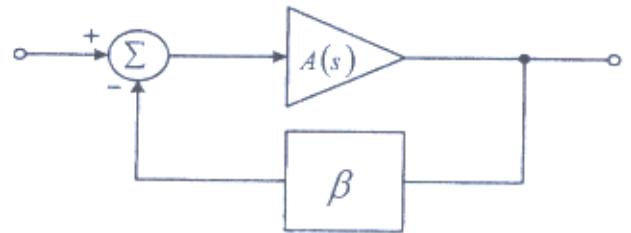


戊組

1. (20%) (a) (5%) The amplifier in a feedback circuit as shown in **Fig. 1(a)** has a transfer function of


$$A(s) = \frac{100}{\frac{s}{10^5} + 1}$$



**Fig. 1(a)**


What value of  $\beta$  will increase the upper  $-3\text{db}$  frequency by a factor of 10 for the closed-loop circuit? What is the low frequency gain of the closed-loop circuit?

- (b) (15%) (i) Please find the transfer function,  $V_{out}(s)/V_{in}(s)$ , of the circuit as shown in **Fig. 1(b)** and identify the location of the poles and zeros. (ii) Sketch the asymptotic (straight-line) plot for the magnitude of the transfer function. (iii) What is the gain in the region where the transfer function is independent of frequency?

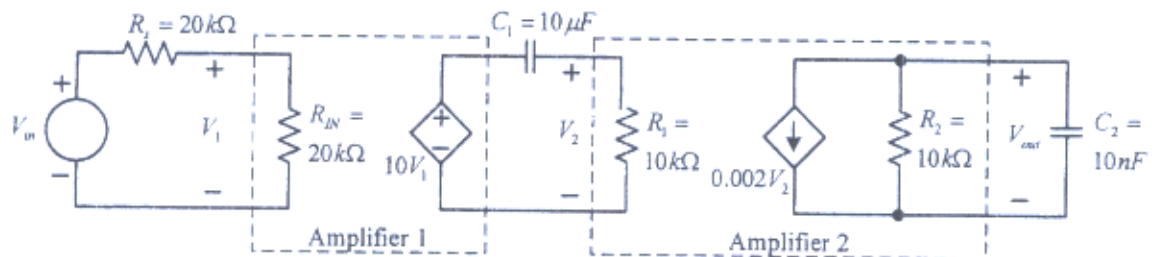

**Fig. 1(b)**

2. (20%) Assume that the op amps are ideal in the circuit as shown in **Fig. 2**; please find  $i_{out}/(v_1 - v_2)$  and the input resistance defined as  $R_{in} = (v_2 - v_1)/i_{in}$ .

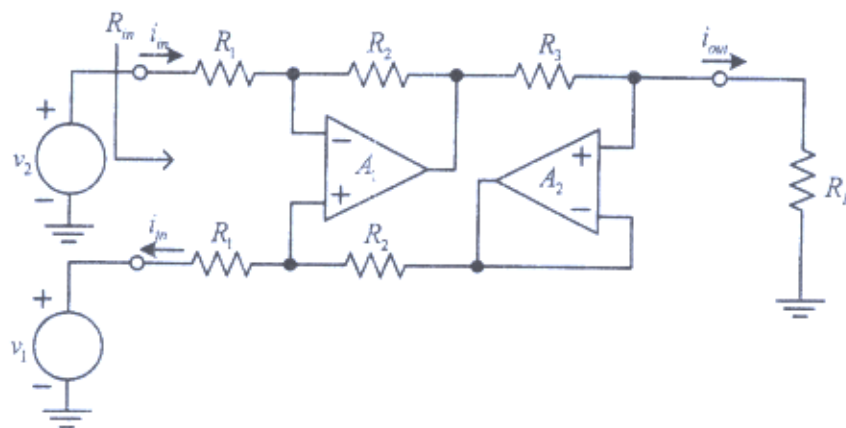

**Fig. 2**

(背面仍有題目,請繼續作答)

3. (20%) A shunt-shunt feedback amplifier is shown in Fig. 3. Please use the methods of feedback analysis to find the values of  $v_2/v_1$ ,  $v_1/i_1$  and  $v_2/i_2$ . Assume that all transistors are matched and that  $V_T = 25mV$ ,  $\beta = 100$  (of the BJT),  $I_{C1} = I_{C2} = 100\mu A$  and  $r_o = \infty$ .

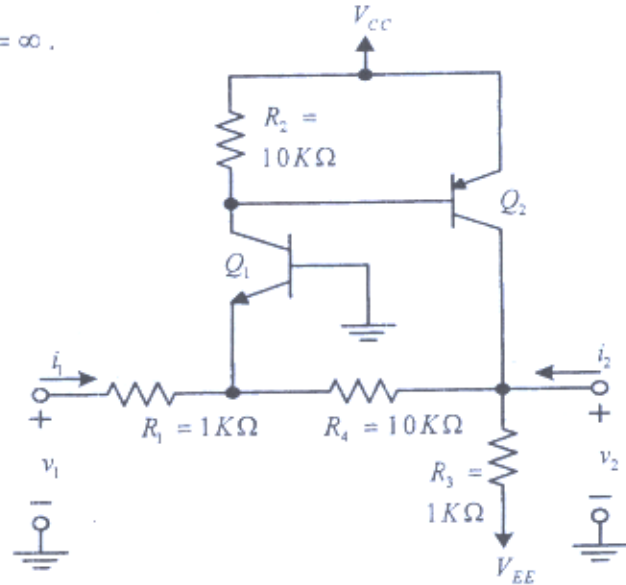


Fig. 3

4. (20%) A pnp BJT circuit is shown in Fig. 4. (a) Find the dc values of  $I_E$ ,  $I_C$ ,  $I_B$ ,  $V_E$ ,  $V_C$  and  $V_B$  if  $\beta = 50$  and  $V_{EB(on)} = 0.65$ . (b) For what value of  $R_C$  does the BJT become saturated?

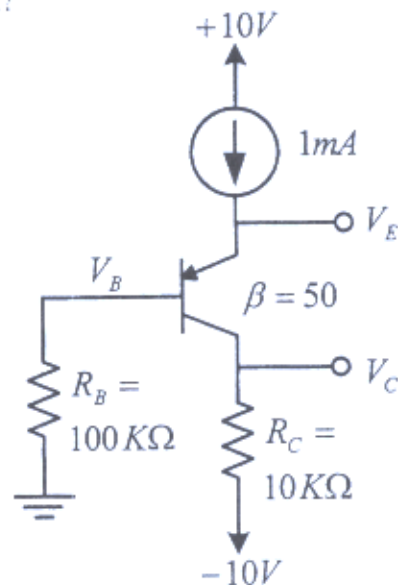


Fig. 4

5. (20%) Assume that the op amp is ideal and the diodes have a drop voltage  $V_D = 0.7V$  in the circuit of Fig. 5. (a) Please find and sketch the voltage transfer ( $V_o$  with respect to  $V_i$ ) characteristics of the circuit. (b) If  $V_i(t) = 15 \sin(2\pi t)$ , please plot the output voltage  $V_o(t)$  in the time domain.

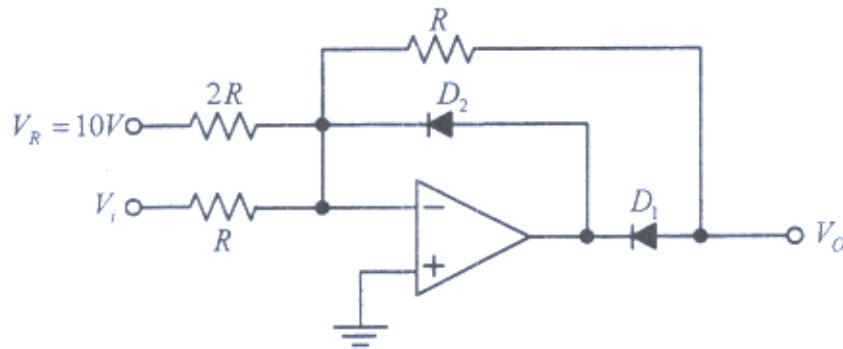


Fig. 5