

※ 考生請注意：本試題 可 不可 使用計算機

1. (15%) (a) (7%) The circuit shown in Fig. 1.1 is biased with a constant-current source I_Q . The transistor has $\beta = 120$ and the E-B turn-on voltage is $V_{EB(on)} = 0.65V$. Determine I_Q such that $V_{ECQ} = 3V$.
- (b) (8%) Consider the circuit with $\beta = 120$ and $V_{BE(on)} = 0.7V$ as shown in Fig. 1.2. Design R_1 and R_2 such that $V_{CEQ} = 5V$.

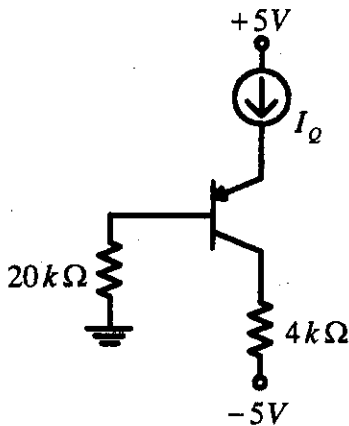


Fig. 1.1

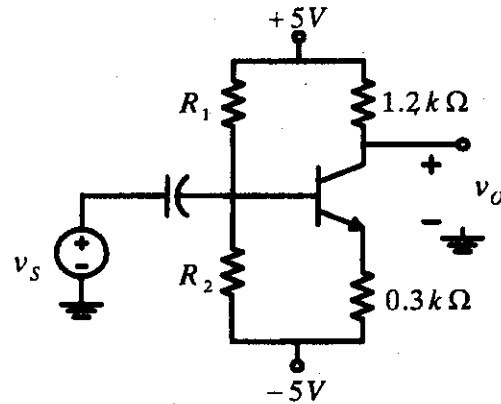


Fig. 1.2

2. (20%) A feedback amplifier is shown in Fig. 2. Assume that all transistors are matched and that $V_T = 25mV$, $\beta = 100$ (of the BJT), $I_{C1} = I_{C2} = 1.0mA$ and $r_o = \infty$. Please determine (a) (5%) g_m , r_e , r_{π} ; (b) (5%) the voltage gain v_2/v_1 ; (c) (5%) the input resistance R_i ; (d) (5%) the output resistance R_o .

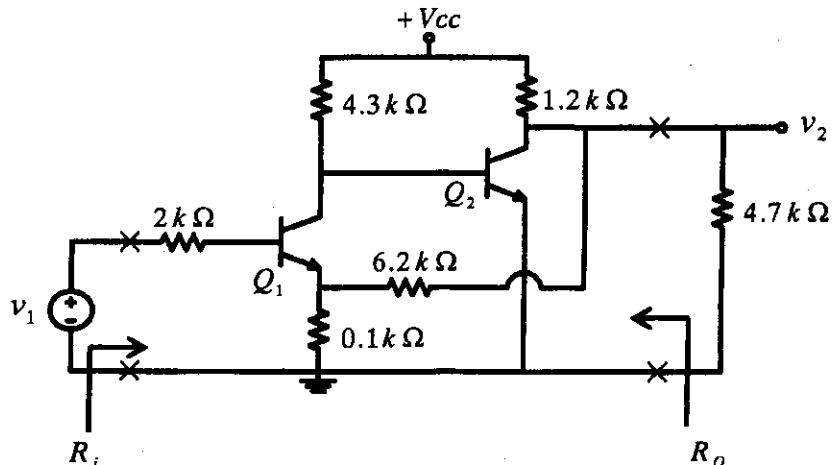


Fig. 2

(背面仍有題目,請繼續作答)

系所組別： 工程科學系甲、戊、己組

考試科目： 電子電路

考試日期： 0307，節次： 1

※ 考生請注意：本試題 可 不可 使用計算機

3. (15%) Consider the circuit shown in Fig. 3. The two port circuit A has the hybrid parameters: $h_{11}=1\Omega$, $h_{12}=\frac{1}{3}$, $h_{21}=-3$ and $h_{22}=\frac{1}{3}\Omega^{-1}$. Please determine (a) (5%) the voltage gain V_1/V_2 ; (b) (5%) the voltage V_2 ; (c) (5%) the input resistance R_i .

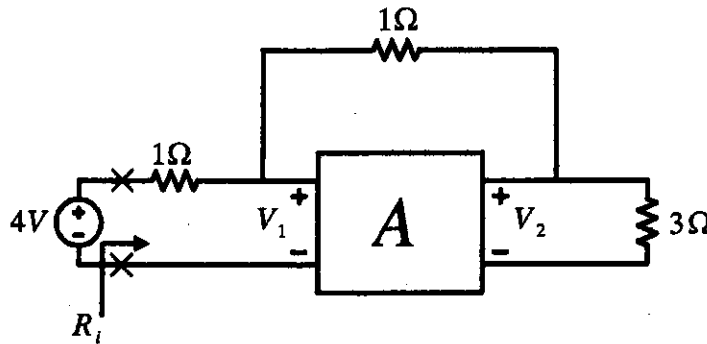


Fig. 3

4. (15%) Assume that the OP amp and diodes are ideal in the circuit of Fig. 4. (a) (8%) Please plot the transfer characteristic (v_o with respect to v_i) of the circuit. (b) (7%) If $v_i(t) = 5\sin(2\pi t)$, please plot the output voltage $V_o(t)$ in the time domain.

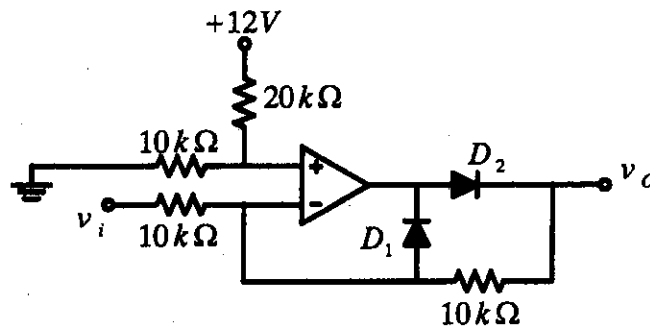


Fig. 4

5. (15%) (a) (10%) Assume that the op amp is ideal and all initial conditions are zero in the circuit of Fig. 5. (i) (5%) Please determine the transfer function $\frac{V_o(s)}{V_i(s)}$ of the circuit. (ii) (5%) Please derive the input-output differential equation in the time domain. (b) (5%) Please design an analog circuit to solve the following differential equation (all initial conditions are zero)

系所組別： 工程科學系甲、戊、己組

考試科目： 電子電路

考試日期： 0307 · 節次： 1

※ 考生請注意：本試題 可 不可 使用計算機

$$\frac{d^2 v_o(t)}{dt} + \frac{dv_o(t)}{dt} + v_o(t) = 1.$$

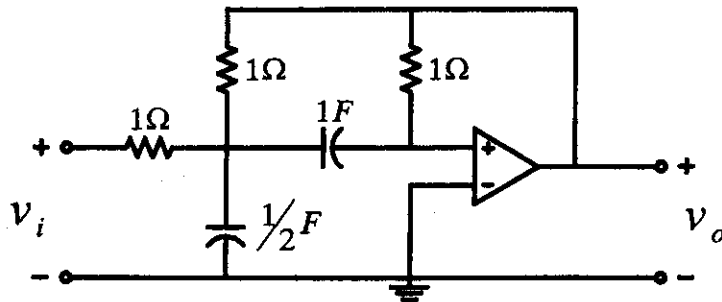


Fig. 5

6. (20%) Consider the differential amplifier in the Fig. 6, the component's characteristic as following, Q_1 and Q_2 are matched JFETs with $I_{DSS} = 2.5 \text{ mA}$, $V_p = -2 \text{ V}$ and Q_3 is the BJT with $\beta = \infty$. The input voltages of the JFETs, represented by v_{s1} and v_{s2} , are only small signal without DC component.

(a) (10%) Find the DC quiescent point ($I_{15.3k\Omega}$, I_{C3} , V_{C3} and V_{D2}).

(b) (10%) Determine the small signal voltage gain if the output is taken differentially. ($r_o = \infty$ for all the JFETs and BJT).

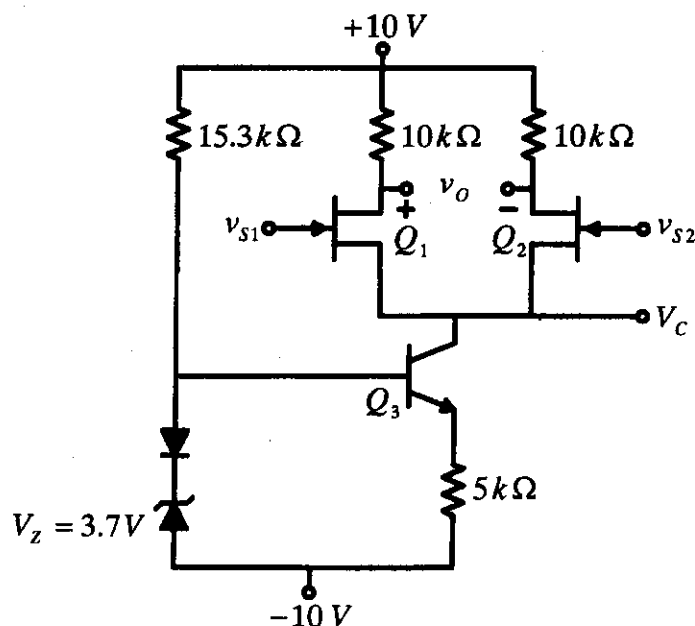


Fig. 6