

PI/2

Electric Circuit and Electronics

Institute of Aeronautics and Astronautics

- In Figure 1, (a) Find an equivalent circuit by Bartlett Bisection Theorem, (巴萊特平分定理)
 (b) Find branch current I ,
 (c) Find node voltage V_{ab} . (15%)

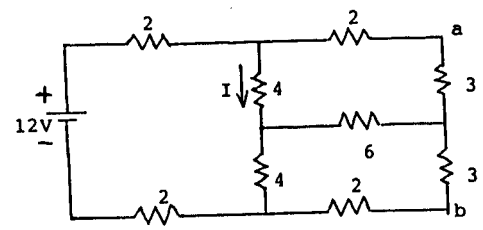


Figure 1.

- In Figure 2, if $i_1(0^+) = 2$, $i_2(0^+) = -1$, $v_c(0^+) = 3$,
 (a) Formulate the state equations to solve this circuit,
 (b) Calculate $v_2(0^+)$, $\frac{dv_2}{dt}(0^+)$. (15%)

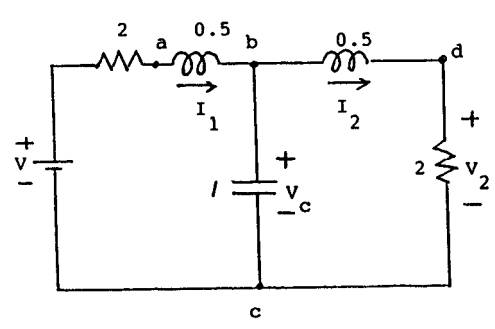


Figure 2.

- (a) Describe the V-I characteristic of a tunnel diode. (5%)
 (b) Describe the R-S Flip-Flop circuit and its truth table. (5%)
 (c) Define the input offset voltage for an operational amplifier. (5%)

P2/2

4. An amplifier is shown in Figure 3, with its specifications in Table 1.
 (a) Draw the alternative equivalent circuit by using Miller's Theorem,
 (b) Calculate R_i , R_i' , A_v , A_{vs} , and $A_{I'} = -I_2/I_1$. (15%)

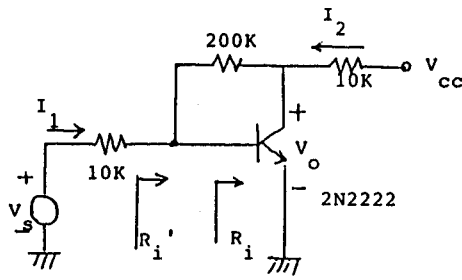


Figure 3.

Table 1.
 (h-Parameters of 2N2222 at $I_E = 1.3 \text{ mA}$)

	CE	CC	CB
h_i	1,100'	1,100	21.6 ohm
h_r	2.5×10^{-4}	~ 1	2.9×10^{-4}
h_f	50	-51	-0.98
h_o	24	25	0.49 $\mu\text{A/V}$
$1/h_o$	40K	40K	2.04M

5. Prove how does transistor transconductance g_m vary with $|I_c|$ and T at high frequency operation. (15%)
6. In stability problem, define (a) rise time,
 (b) delay time,
 (c) overshoot,
 (d) settling time.

Draw a step response of a two-pole feedback amplifier for a damping factor $K=0.3$, and show the above items in the response curve. (15%)

** The drawing is not necessary to be precision in scale.
 (此圖毋需十分精確，僅可示意即可)

7. (a) Explain what is the "thermal runaway". (5%)
 (b) Define and explain the Common Mode Rejection Ratio. (5%)