

1. In the basic circuit theory, the duality (對偶性) is a nature existing as the electric circuit phenomenon.

(1) describe the Duality Law,

(2) Figure 1 shows a DC circuit, determine the duality circuit, and be sure to indicate all terms which are shown in the circuit by Duality Law.

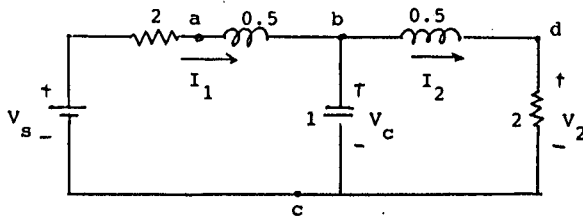


Figure 1.

2. Assume a voltage wavefor  $V_{in}(t)$  is sinusoidal, and varies with its center null from 0 V to 6 V by one step.  $V_{in}(t)$  is shown in Figure 2.a.

(1) draw the input waveforms for these two cases,

(2) describe the  $V_o$  of Figure 2.b with two  $V_{in}(t)$  cases,

(3) describe the  $V_o$  of Figure 2.c with two  $V_{in}(t)$  cases,

(4) describe the  $V_o$  of Figure 2.d with two  $V_{in}(t)$  cases.

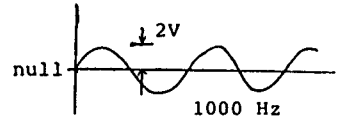


Figure 2.a

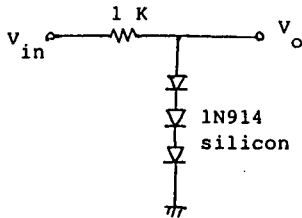


Figure 2.b

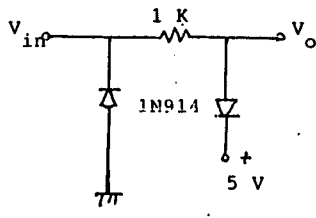


Figure 2.c

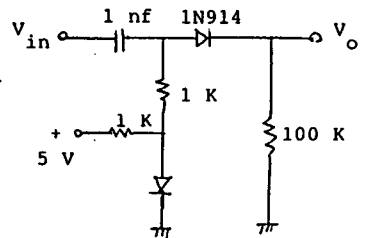


Figure 2.d

3. The transistor 2N3904 and FET 2N5457 are made of silicon material, their data are shown:

2N3904:  $h_{ie} = 3.5 \text{ K-Ohm}$ ,  $h_{re} = 1.3 \times 10^{-4}$ ,  $h_{fe} = 120$ ,  $h_{oe} = 8.5 \text{ Micro-Mho}$ ;

2N5457:  $g_m = 4275 \text{ Micro-Mho}$ .

(1) calculate  $I_e$ .

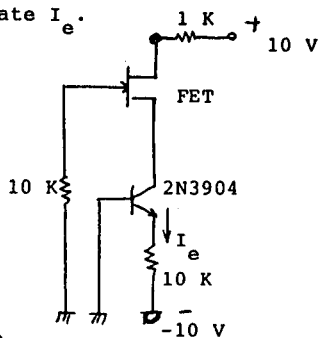


Figure 3.

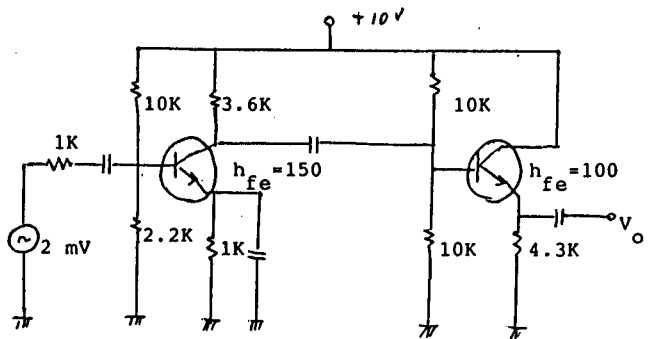


Figure 4.

4. A two stage amplifier, the first stage is a CE amplifier, the second stage is an Emitter follower, is shown in Figure 4. From the calculation, the first stage has been known as:

$A = -159$ ,  $Z_{in} = 1.18 \text{ K-Ohm}$ ,  $Z_o = 3.6 \text{ K-Ohm}$ .

(1) draw the AC equivalent circuit specified all components,

(2) calculate the output voltage when the input voltage is 2 mV.