

- Figure 1 shows the circuit with two impedances Z_S and Z_L .
 - Derive the necessary condition of Z_S and Z_L (Load) to fulfill the Maximum Power Transfer Theorem, from which load Z_L will receive maximum power delivery from power source $V_c(t)$.
 - Under direct current (d.c.) condition, what is the necessary condition of maximum power delivery.
 Note: R_S and R_L are the only parts of concern from Z_S and Z_L . (15%)
- Find a Thevenin Equivalent Circuit from Figure 2 across terminals a and b with 80 Ohms load. (10%)
- Following Figure 3, use any small signal transistor equivalent circuit model to process the problems:
 - Calculate C_E for resistor $R_{E2} = 560$ Ohms, if the operating frequency is 1000 Hz to 200 KHz.
 - Draw the a.c. equivalent circuit of Fig. 3.
 - Derive the overall voltage gain V_L/V_S . (15%)

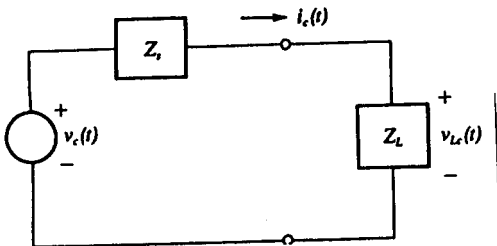


Figure 1.

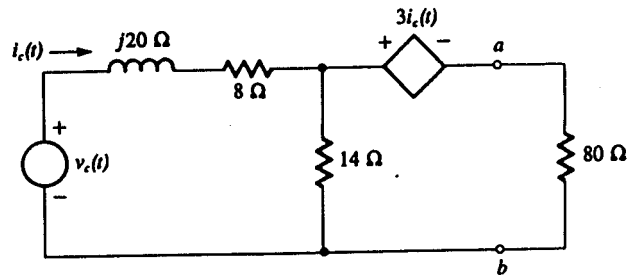


Figure 2.

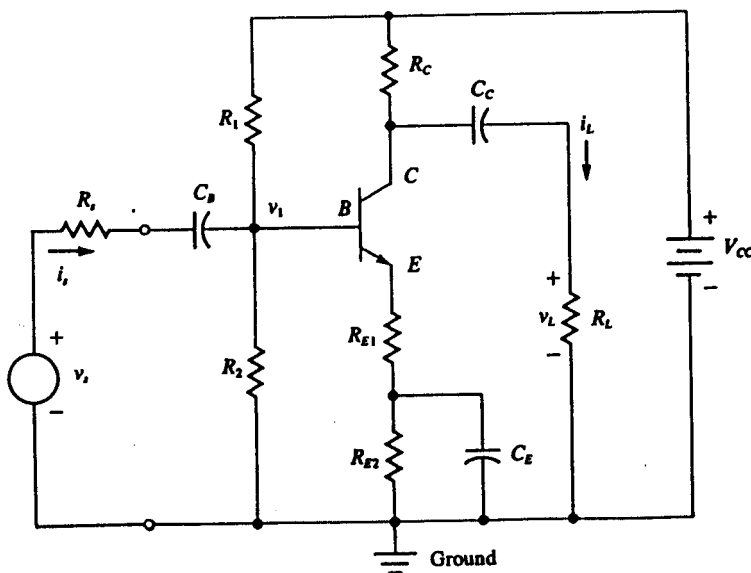


Figure 3.

4. An adaptor is designed using Figure 4. If the design conditions are determined as:
- (1) transformer secondary is 12V a.c. at 60Hz,
 - (2) use silicon rectifier 1N4001,
 - (3) use 2500 μf capacitor for C,
 - (4) load current is 0.15 A maximum when load resistance is varying.

Process the following problems:

- (a) Calculate the average voltage of V_o ,
- (b) Calculate the Maximum voltage of V_o .

(10%)

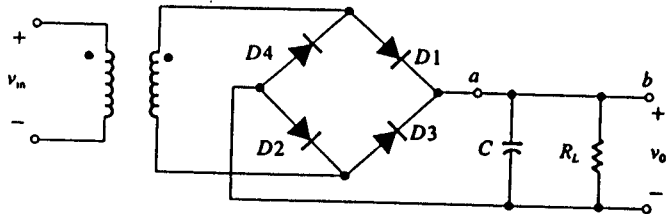


Figure 4.

5. Short answers to the following questions:
- (a) Draw a Non-inverting summer OPA circuit.
 - (b) Draw a logic circuit to carry out:

$$F = \bar{A} \cdot B + B \cdot C$$

(10%)

6. A 10-Kg wheel as shown in Figure 6 has a moment of inertia of $I_G = 0.156 \text{ Kg}\cdot\text{m}^2$. Assuming that the wheel does not slip or rebound, determine the minimum velocity v_G to roll over the obstruction at A.
7. Block D in Figure 7 moves with a speed 3 m/sec. Determine the angular velocity of its link BD and AB, and the velocity of point B at the instant shown on figure.
8. Write the necessary equations to describe the motion of two masses between three springs as shown in Figure 8.

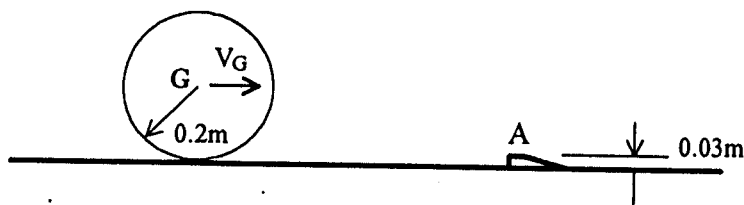


Figure 6.

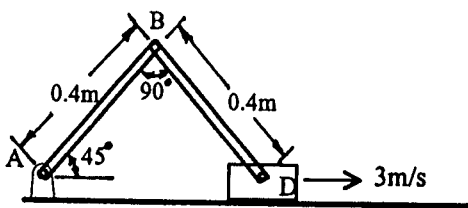


Figure 7.

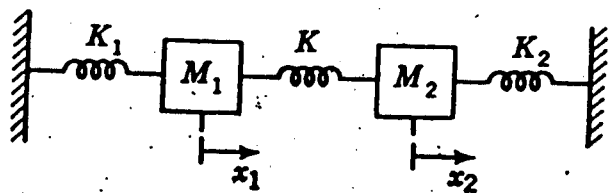


Figure 8.