

Part A. Figure 1 shows a single transistor amplifier circuit.

Solve or discuss the following problem using this figure.


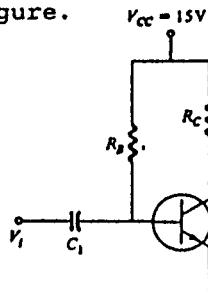



Figure 1.

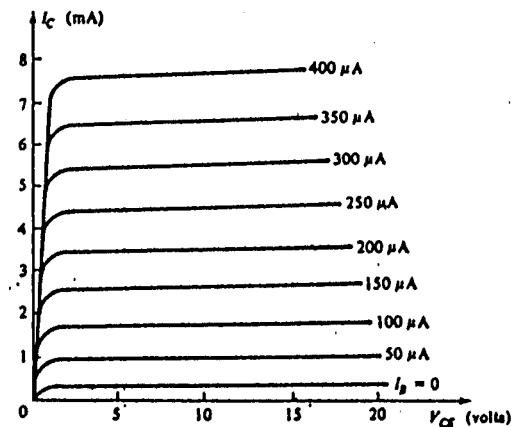



- Describe and discuss the design process and consideration to determine a load line and operating point (Q-point) for this transistor.
Following your idea, calculate R_B and R_C to meet the requirement. (10%)
- Use an appropriate small signal equivalent model to convert Figure 1 into a.c. equivalent circuit, by assuming a voltage signal V_s in series with a resistance R_s is applied to V_i , and a load resistance R_L is applied to V_o . (10%)
- Following Problem 2, formulate the relation equation of voltage gain $A_V = V_o / V_s$. (10%)
- In Figure 1, what is the purpose to apply the capacitors, C_1 and C_2 ? Following Problem 2, formulate the equation to calculate C_1 and C_2 . (10%)

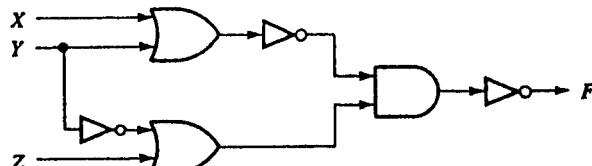Part B.

- Derive the Boolean expression of Figure 2. Find the possible combination of inputs X, Y, Z to get output F logic 1. Assume positive logic is applied. (10%)



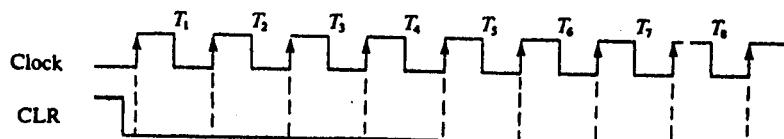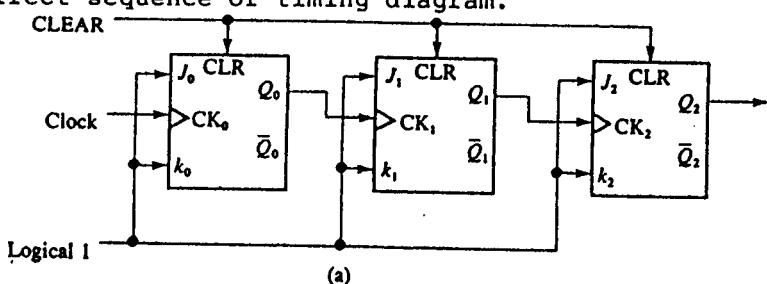- Figure 3 is a 3-bit ripple counter logic diagram. If the clock and clear diagram is shown as below, sketch the logic diagram of Q_1 and Q_2 following correct sequence of timing diagram. (10%)



Part C

[第七題] 在右圖中，考慮一質點，其質量為 m ，受到力 \vec{F} 與重力 $m\vec{g}$ 之作用。力 \vec{F} 總是沿著速度 \vec{V} 之方向，重力 $\vec{m}\vec{g}$ 係沿著負 y 軸之方向， xy 為慣性軸， \vec{V} 與 x 軸之夾角為 γ 。利用(1)位置向量之微分為速度，(2)加速度為單位質量所受之總力。

- 導出運動方程式，並以一階微分方程式表示之，此即，將運動方程式寫成


$$\dot{\mathbf{x}} = \mathbf{f}(\mathbf{x}, \mathbf{u})$$

之形式，式中， $\mathbf{x} = [x(t) \ y(t) \ V(t) \ \gamma(t)]^T$ 為描述此質點運動所需最少之變數，亦稱為狀態變數 (state variables)， $\mathbf{u} = [m \ g \ F(t)]^T$ ，其中 g 為重力加速度，在此保假設為常數。 (15%)


- 用數質分析法解此方程式與利用計算機模擬 (simulate) 此質點運動有何關係？ (5%)

[第八題] 在右圖中，考慮一半徑為 r ，質量為 m 之均勻實心圓盤，置於與水平夾角為 θ 之斜坡上，重力加速度為 g ，

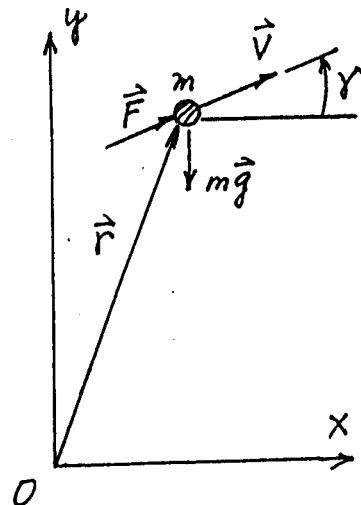- 若圓盤與斜坡均為光滑無摩擦之表面，求圓盤之角加速度與其中心點之加速度。 (7%)
- 若圓盤為純滾動，求圓盤之角加速度與其中心點之加速度。 (7%)
- 若圓盤於一平面 ($\theta = 0$) 之上純滾動，接觸處之摩擦力係與圓盤運動之方向同向或反向？圓盤應加速或減速？試以作用於圓盤之力，與其對於圓盤中心點所產生之力矩說明之。 (6%)



圖：第七題

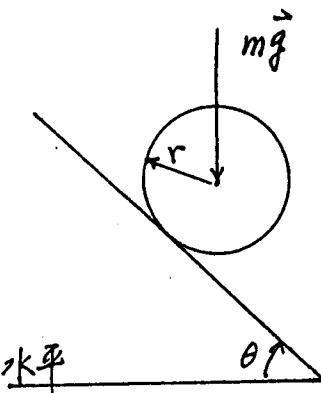

圖：第八題