

系所組別： 系統及船舶機電工程學系丁組


考試科目： 電路學

考試日期：0225，節次：2

請勿在本試題紙上作答，否則不予計分

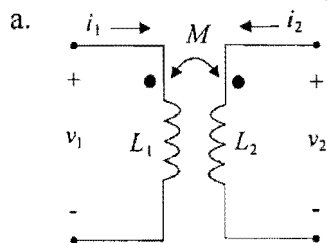
**Problem #1: (14 points, 2 pts each)** Please write your answers on the answer sheet

Use the passive sign convention and the dot conventions to write expressions for the voltage ( $v$ ), current ( $i$ ), power absorbed ( $p$ ), or energy stored ( $w$ ), as specified by each of the problems below.




$v_1 =$  \_\_\_\_\_

$v_2 =$  \_\_\_\_\_

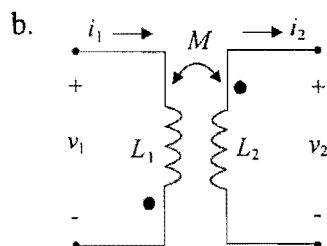


$v_1 =$  \_\_\_\_\_

$v_2 =$  \_\_\_\_\_

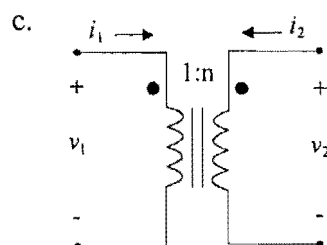


$v_2/v_1 =$  \_\_\_\_\_

$i_2/i_1 =$  \_\_\_\_\_

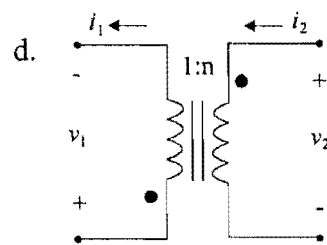


$v_2/v_1 =$  \_\_\_\_\_

$i_2/i_1 =$  \_\_\_\_\_

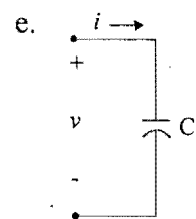


$i =$  \_\_\_\_\_

$w =$  \_\_\_\_\_

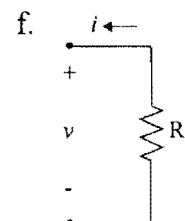

$v =$  \_\_\_\_\_

$p =$  \_\_\_\_\_

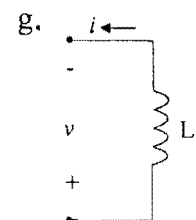

$v =$  \_\_\_\_\_

$p =$  \_\_\_\_\_

(背面仍有題目,請繼續作答)

**Problem #2: (10 points, 1 pts each)**


Please write either *True* (T) or *False* (F) on the answer sheet for the following questions.

- a. By convention, the direction of current is defined as the direction of positive charge flow.
- b. The passive sign convention is satisfied if the labeled current is leaving the terminal labeled with the negative polarity, “-”.
- c. An ideal current source that produces a current of 0 A is equivalent to a short circuit.
- d. Kirchhoff’s laws tell us how the voltage and current within a circuit element are related.
- e. Phasors are complex numbers that represent the phase and amplitude of sinusoidal signals.
- f. Any two terminals in a circuit containing operational amplifiers, dependent sources, independent sources, and resistors is electrically equivalent to a Norton equivalent current source in parallel with the Norton equivalent resistance.
- g. The “real” model of operational amplifiers is less accurate than the “ideal” model, but we use the “real” model because it simplifies analysis.
- h. Capacitors, inductors, and dependent sources are called “energy storage” elements because they cannot dissipate or produce power.
- i. The ideal model of an operational amplifier has an infinite input resistance and gain.
- j. Source transformations combined with phasors enable us to solve for the steady-state response of circuits containing independent sinusoidal sources operating at different frequencies.

**Problem #3: (16 points)**

Your answers to the following questions should include the voltage  $V_s$  and should not include the voltages  $V_a$ ,  $V_b$ ,  $V_c$ , or  $V_d$ , or the currents  $I_3$ ,  $I_X$ ,  $I_s$ , or  $I_4$ , unless otherwise specified.

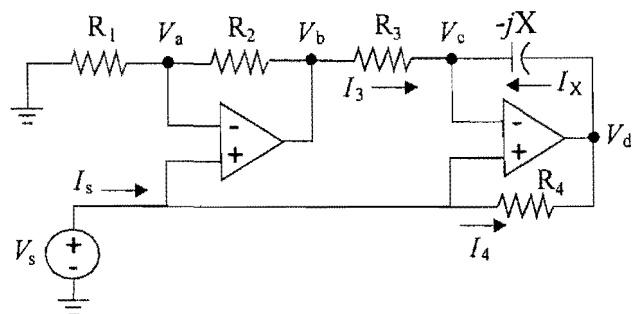- a. (4 pts) Write expressions for  $V_a$ ,  $V_b$ , and  $V_c$ .
- b. (2 pts) Write an expression for  $I_3$ .
- c. (2 pts) Write an expression for  $V_d$ .
- d. (2 pts) Write an expression for  $I_4$ .
- e. (2 pts) Write an expression for  $I_4$ . Your answer should not include  $V_s$  and should include  $I_s$ .
- f. (2 pts) What is the equivalent impedance seen by the voltage source? Your answer should not include  $V_s$  or  $I_s$ .
- g. (2 pts) What type of circuit element does this equivalent impedance resemble? Choose one.  
Resistor      Inductor      Capacitor      Linear Transformer



**Problem #4: (10 points, 5 pts each)**

(a) A series *RLC* circuit contains a resistor  $R = 3 \Omega$  and a capacitor  $C = 4 \text{ F}$ . Select the value of the inductor so that the circuit is critically damped.


(b) Design a parallel *RLC* circuit with  $R \geq 1 \text{ k}\Omega$  that has the characteristic equation

$$s^2 + 2 \times 10^7 s + 2 \times 10^{14} = 0$$

If we let  $R = 1 \text{ k}\Omega$ , please find the values of  $L$  and  $C$ .

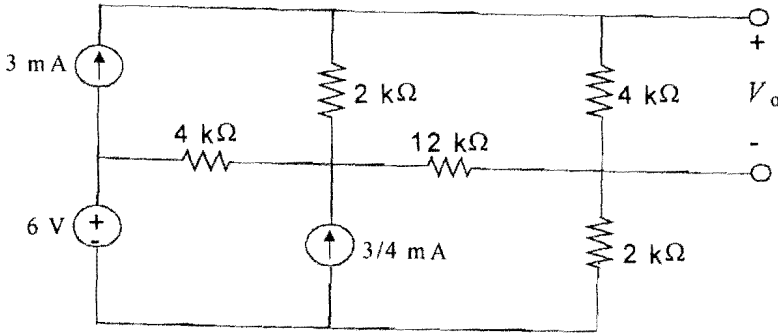
**Problem #5: (20 points)**

Find  $V_o$  in the figure using Thevenin's theorem.



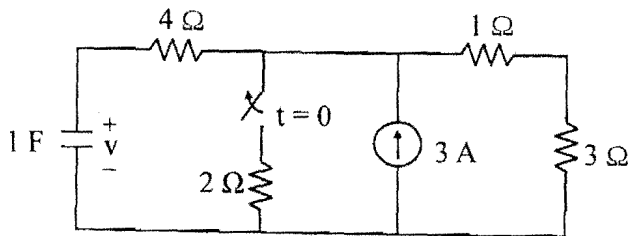**Problem #6: (15 points)**

Find  $v$  for  $t > 0$  if the circuit is in steady state at  $t = 0^-$  in the network shown.



**Problem #7: (15 points)**

Find the AC steady state voltage  $v$  in the network shown.

