

※考生請注意：本試題不可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. Please translate the following paragraph into Chinese.

Magnetic resonance imaging (MRI, 磁振造影) is receiving more and more attention as scientists strive to improve the quality of the cross-sectional images of the body so useful in medical diagnosis and treatment. MRI does not expose the patient to potentially hazardous X-rays or injected contrast materials such as those employed to obtain computerized axial tomography (CAT, 電腦斷層掃描) scans. (12%)

2. For the circuit shown in Fig 1, the switch closes at $t = 0$. There is no energy stored in the capacitor for $t < 0$. Solve for the following:

(1) For $V=10$ V, $L = 1.8$ mH and $C = 0.2$ mF, determine R such that the system is critically damped (denoted R_c here). (8%)

(2) For $R = 50\% R_c$, determine $V_C(t)$. Indicate the type of damping. (12%)

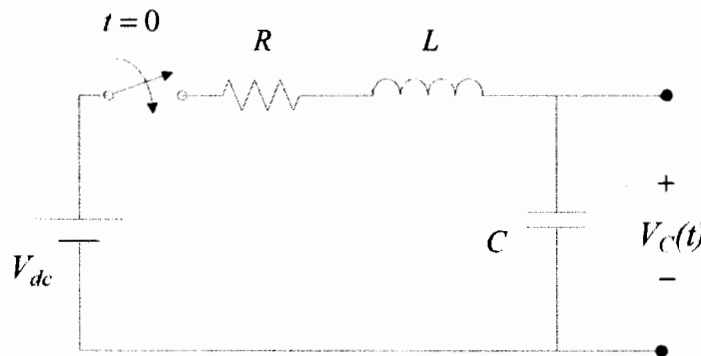


Fig. 1

3. As shown in Fig. 2(a), the circuit is in sinusoidal steady state. With the output waveform $v_{out}(t)$ shown in Fig 2(b), sketch the input waveform $v_{in}(t)$ on the same graph. Indicate the magnitude and the phase difference with $v_{out}(t)$. (Note: $\pi = 3$ for simplicity)(18%)

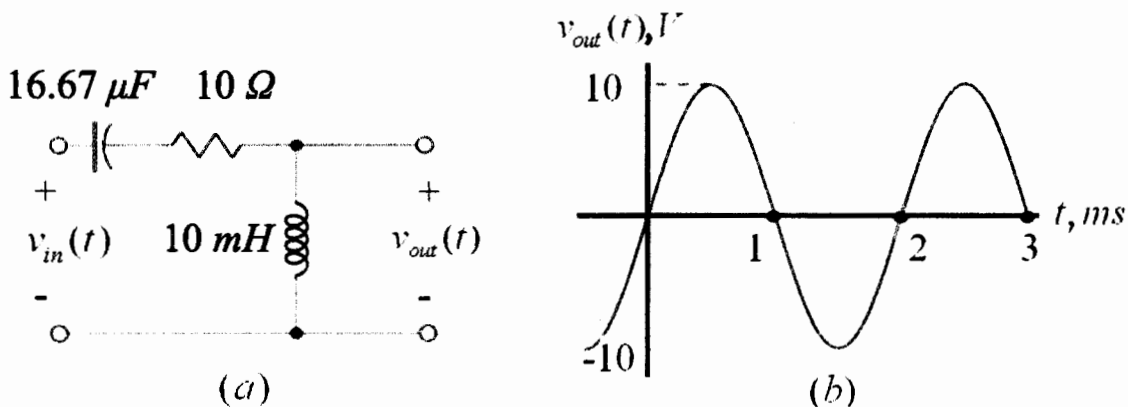


Fig. 2

4. A voltage source with $V_s(t) = 120\sqrt{2} \cos(250t) V$ is connected in series with a resistor $R=100 \Omega$, an inductor $L=0.8 H$ and a capacitor $C=25 \mu F$.

- (1) Find the equivalent impedance for all R, L and C at the source frequency. (5%)
- (2) Determine the sinusoidal steady-state current, $i(t)$. (5%)
- (3) Draw a phasor diagram to describe the voltages across all the elements (including the source and R, L, C) and the current. Indicate the magnitudes and phase angles. (6%)
- (4) What is the apparent power out of the voltage source and what is the power factor? (4%)

5. After being open a long time, the switch in Fig. 3 is closed at $t=0$ for 4 s, then opened again. Determine and sketch the voltage $V_R(t)$ for $t > 0$. (15%)

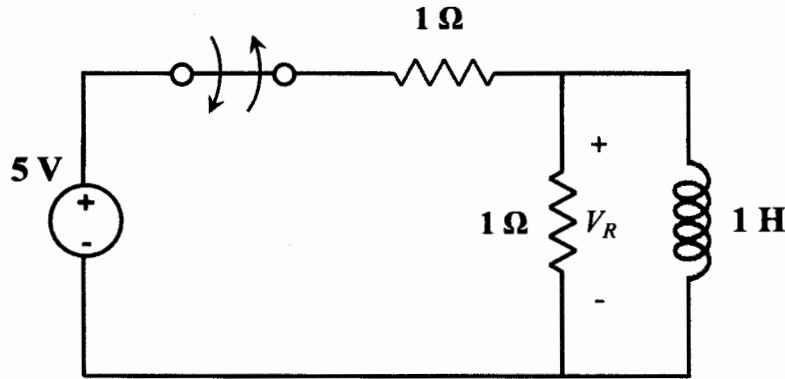


Fig. 3

6. A load is connected to an ac voltage source of 460 Vrms and 60 Hz. The load consumes a power of 12 kW at a power factor of 0.75. To improve the power factor to 0.9, a capacitor is connected in parallel with the load. What is the capacitance needed? Draw a phasor diagram to indicate how this works. ($\cos^{-1}0.75=41.4^\circ$, $\cos^{-1}0.9=25.8^\circ$) (15%)