

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1、Choice question (20%)

- (1) The low frequency response of an amplifier is determined in part by (a) the voltage gain, (b) the type of transistor, (c) the supply voltage, (d) the coupling capacitors.
- (2) The Miller input capacitance of an amplifier is dependent, in part, on (a) the input coupling capacitor, (b) the voltage gain, (c) the bypass capacitor, (d) none of these.
- (3) Ideally, the mid-range gain of an amplifier (a) increases with frequency, (b) decreases with frequency, (c) remains constant with frequency, (d) depends on the coupling capacitors
- (4) The purpose of a pentavalent impurity is to (a) reduce the conductivity of silicon (b) increase the number of holes (c) increase the number of free electrons (d) create minority carriers
- (5) Which one is NOT true when a reverse bias is applied to P-N junction. (a) current flows from n-type to p-type region ; (b) depletion-layer width increases ; (c) diffusion capacitance dominates ; (d) breakdown may take place if the reverse voltage is too high

2、Sketch v_o versus time for the circuit in Figure 1(a) and (b) with the input shown.

Assume $V_\gamma = 0$ and $r_f = 0$ for Figure 1(a) ; $V_\gamma = 0.7$ and $r_f = 10\Omega$ for Figure 1(b). (10%)

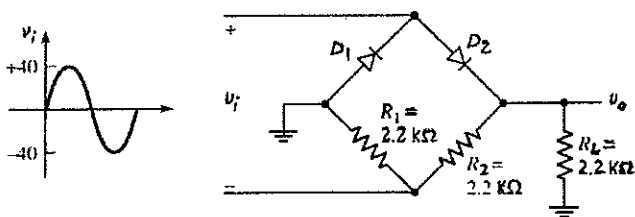


Figure 1 (a)

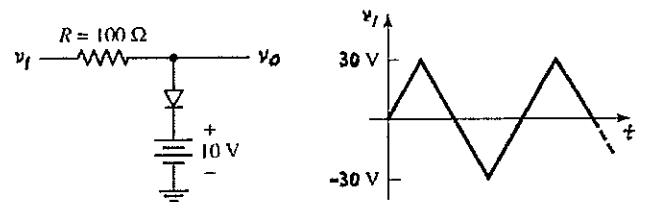


Figure 1 (b)

- 3、The bridge power amplifier is shown in Figure 2. This amplifier has a very high input resistance since the input is to the noninverting terminal of an op-amp. (a) Derive the expression for the voltage gain $A_v = v_L / v_i$. (b) Design the circuit to provide a gain of $A_v = 10$ so that the magnitudes of v_{o1} and v_{o2} are equal. Let $R_1 = 50k\Omega$. (c) If $R_L = 20\Omega$ and if the average power delivered to the load is 10W, determine the peak amplitude of v_{o1} and v_{o2} and the peak load current. (20%)

4. For each transistor in Figure 3, the parameters are $\beta = 100$ and $V_A = \infty$. (a) Determine the Q-point values for both Q_1 and Q_2 . (b) Draw the hybrid- π model of the amplifier circuit. (c) Determine the overall small-signal voltage gain $A_v = v_o / v_s$. (d) Determine the input and output resistances R_{is} and R_o . (20%)

5. The circuit in Figure 4 is a low-pass active filter. (a) Derive the voltage transfer function $A_v = v_o/v_i$ as a function of frequency. (b) At what frequency is the magnitude of the voltage gain a factor of $\sqrt{2}$ less than the dc value? (This is the -3dB frequency.) (c) Design the low-pass active filter, assume the input resistance is $R_1 = 20 \text{ k}\Omega$, the low frequency gain is -15, and the -3dB frequency is 5kHz. (15%)

6. Consider the basic MOSFET amplifier with active load in Figure 5. The transistor parameters are: $V_{TN} = 1 \text{ V}$, $V_{TP} = -1 \text{ V}$, $(\frac{1}{2})\mu_n C_{ox} = 20 \mu\text{A}/\text{V}^2$, $(\frac{1}{2})\mu_p C_{ox} = 10 \mu\text{A}/\text{V}^2$ and $\lambda_n = \lambda_p = 0.02 \text{ V}^{-1}$. (a) Design the circuit such that $I_{REF} = I_O = 0.1 \text{ mA}$. Assume M_1 and M_3 are matched, and the quiescent input voltage is $V_{IQ} = 2 \text{ V}$. The quiescent output voltage is to be $V_{OQ} = 2.5 \text{ V}$. (b) Determine the open-circuit small-signal voltage gain. (15%)

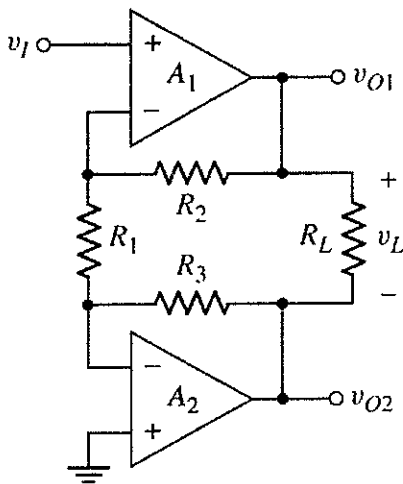


Figure 2

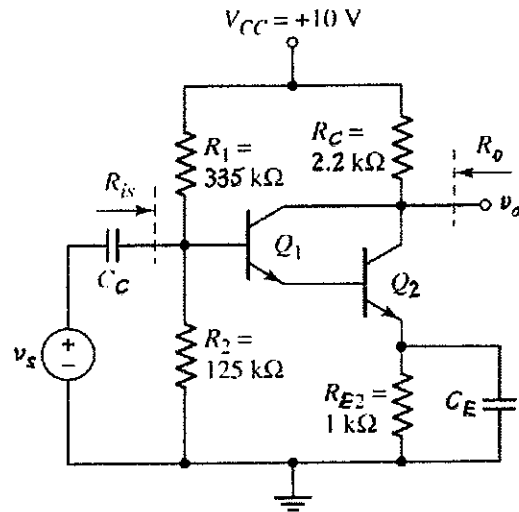


Figure 3

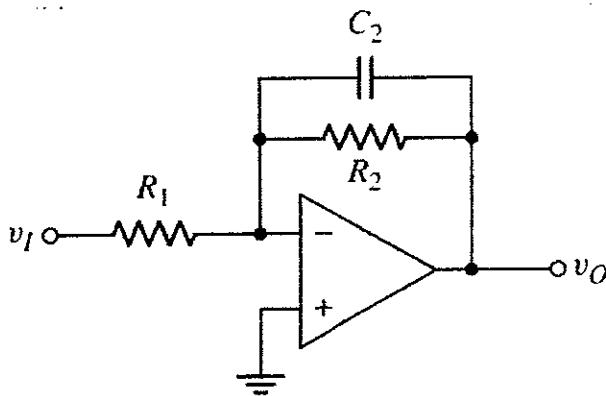


Figure 4

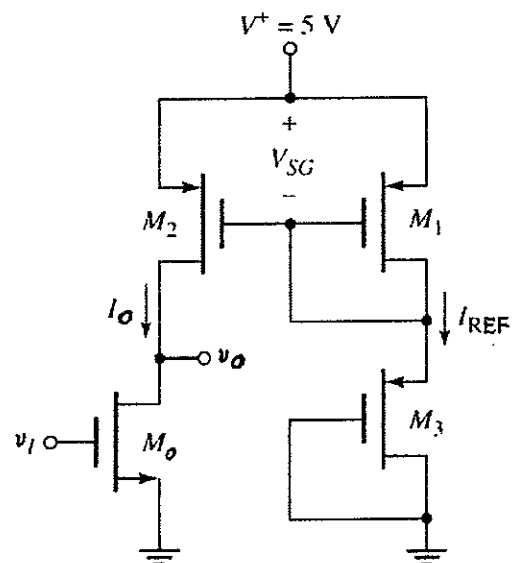


Figure 5