

國立成功大學

114學年度碩士班招生考試試題

編 號：104

系 所：系統及船舶機電工程學系

科 目：電子學

日 期：0210

節 次：第 2 節

注 意：1. 可使用計算機
2. 請於答案卷(卡)作答，於
試題上作答，不予計分。

一、選擇題: (20 分，每題 2 分)

1. The atomic number is the number of
 - a. protons in the nucleus
 - b. neutrons in the nucleus
 - c. protons plus neutrons in the nucleus
 - d. electrons in the outer shell
2. Valence electrons are
 - a. in the outer shell
 - b. involved in chemical reactions
 - c. relatively loosely bound
 - d. all of the above
3. The atomic particle responsible for electrical current in solid metallic conductors is the
 - a. proton
 - b. electron
 - c. neutron
 - d. all of the above
4. For constant voltage in a circuit, doubling the resistance means
 - a. halving the current
 - b. doubling the current
 - c. there is no change in the current
 - d. depends on the amount of voltage
5. Holding the voltage constant, and plotting the current against the resistance as resistance is varied will form a
 - a. straight line with a positive slope
 - b. straight line with a negative slope
 - c. hyperbola
 - d. parabola
6. A battery stores
 - a. electrons
 - b. protons
 - c. ions
 - d. chemical energy
7. The unit of conductance is the
 - a. ohm
 - b. coulomb
 - c. siemen
 - d. ampere

8. A four-color resistor with the color bands gray-red-black-gold is

- a. $73\ \Omega$
- b. $82\ \Omega$
- c. $680\ \Omega$
- d. $820\ \Omega$

9. A $330\ \text{k}\Omega \pm 5\%$ resistor has the color bands


- a. red-red-brown-gold
- b. orange-orange-yellow-gold
- c. yellow-yellow-red-gold
- d. yellow-yellow-green-gold

10. The circular mil is a unit of


- a. length
- b. resistance
- c. volume
- d. area

二、計算題: (80 分)

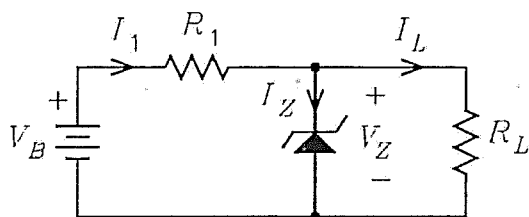1. The figure shows a Zener diode regulator circuit. It is given that $V_B = 45\ \text{V}$, $V_Z = 24\ \text{V}$, $I_Z = 5\ \text{mA}$, $r_Z = 20\ \Omega$, $R_L = 12\ \text{k}\Omega$. (25 分，每小題 5 分)



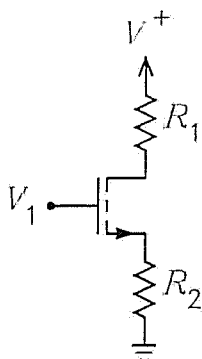- (a) In the large signal model of the Zener diode, what is the voltage V_{Z0} ?
 - (b) What is the values of I_L and I_1 ?
 - (c) What is the required value of R_1 ?
 - (d) Calculate the power dissipated in R_1 , in the Zener diode, and in R_L .
 - (e) If the load current doubles, calculate the decrease in the voltage across the Zener diode.
2. The figure shows a MOSFET circuit. It is given that $V^+ = 18\ \text{V}$, $R_1 = 7.5\ \text{k}\Omega$, $R_2 = 500\ \Omega$, $K = 0.001\ \text{A/V}^2$, and $V_{TH} = 1.5\ \text{V}$. (25 分)
- (a) Find the value of V_1 required to obtain a drain-to-source voltage of $10\ \text{V}$. (20 分)
 - (b) Calculate the power dissipation in the MOSFET. (5 分)



3. A half-wave rectifier is shown. It is given that $v_S(t)$ is a 60 Hz sinusoidal voltage with an rms value of 24 V. When the diode is forward biased, its voltage drop is $V_{D0} = 0.6$ V. The circuit values are $R_L = 200\ \Omega$ and $C = 1000\ \mu\text{F}$. (30 分，每小題 10 分)

- (a) Calculate the peak load voltage.
- (b) Calculate the maximum reverse bias voltage across the diode.
- (c) The percent ripple is given by $\% \text{ ripple} = [1 - \exp(-T/R_L C)] \times 100\%$. When the diode is off, what is the lowest value that the load voltage can “droop” to before the diode conducts again?

