

A total of six problems are given below.

1. (16%) The circuit in Fig. 1 shows a circuit for a voltage source and “potentiometer” (電位計), which is a resistor with a sliding contact. The variable “ $a$ ” varies from 0 to 1, and the open-circuit voltage  $v_{out}$  increases in proportion with  $a$ .

(a) Determine a Thevenin equivalent circuit, as indicated in the right hand side of Fig. 1, for the voltage source, with the voltage and output impedance functions of  $a$ .

(b) What is the maximum output resistance if the total resistance of the potentiometer is  $R$ ?

(c) If the load resistor for this Thevenin equivalent circuit (i.e., connecting to  $v_{out}$ ) were equal to the resistance of the potentiometer,  $R$ , what would  $a$  have to be to give an output voltage of  $0.5 V_s$ ?

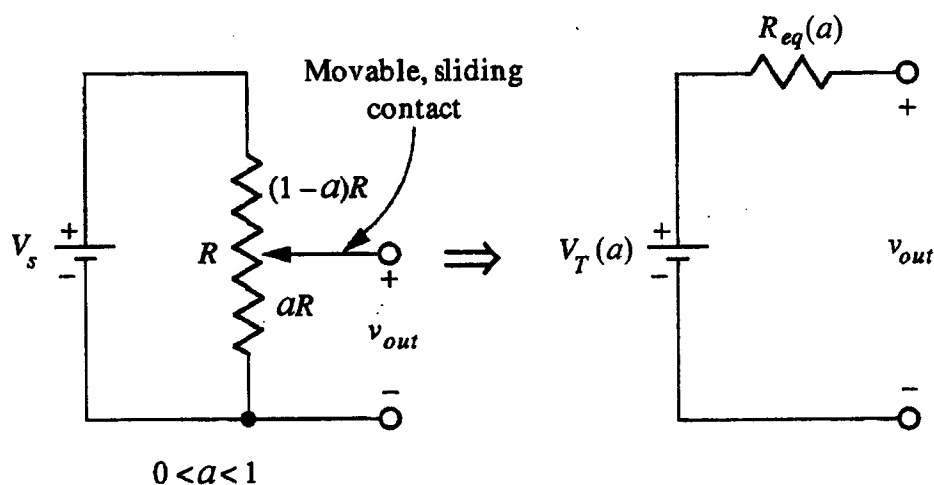


Fig. 1

2. (16%) The switch  $S_1$  in Fig. 2 has been closed for a long time. At  $t = 0$  s,  $S_1$  is opened at the same instant  $S_2$  is closed to avoid an interruption in current through the inductor.

(a) Find the general solution for  $i_L$  following the closing of  $S_2$ .

(b) Sketch  $i_L$  for positive time.


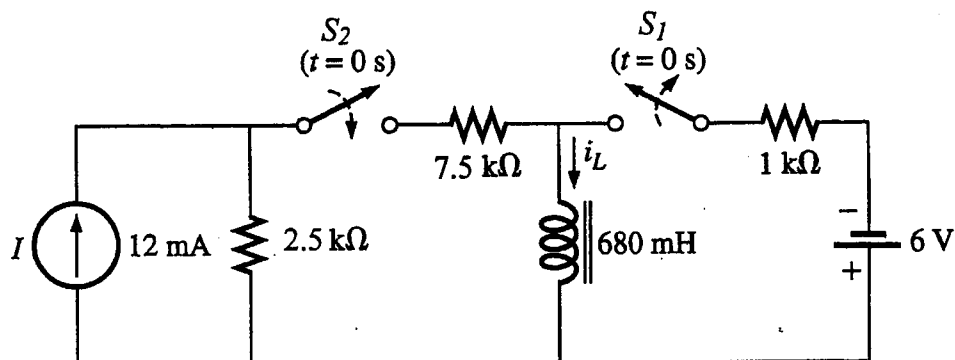


Fig. 2

(背面仍有題目,請繼續作答)

3. (16%) Consider the circuit shown in Fig. 3, answer the following questions:

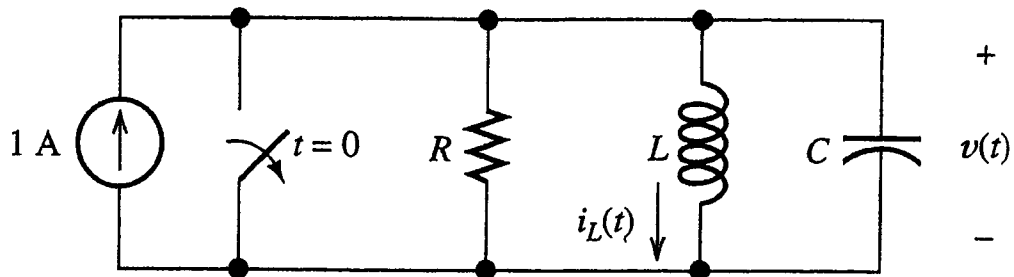- (a) What is the undamped resonant frequency and the damping coefficient?
- (b) Find the general solution for  $v(t)$ , giving the numerical values of all parameters. Assume that the initial conditions are  $v(0^+) = 0$  and  $i_L(0^+) = 0$ .



$$R = 25 \Omega \quad L = 10 \mu\text{H} \quad C = 1000 \text{ pF}$$

Fig 3

4. (16%) The switch shown in Fig. 4 is in position *a* for negative time, moved to *b* at  $t = 0$ , and to *c* at  $t = 5$  ms.

- (a) Sketch  $v_C$  for  $0 < t < 20$  ms.
- (b) At what time should the switch be switched to *c* for no "transient"? (無暫態)

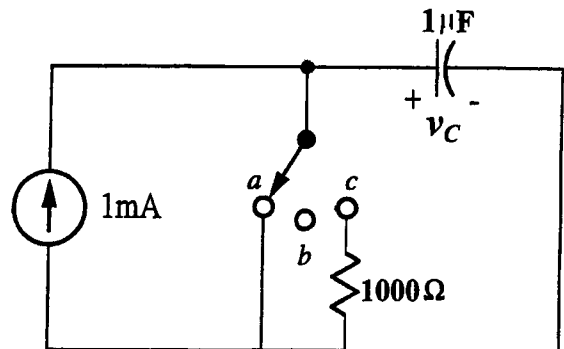


Fig. 4

5. (20%) Complex frequency is used to solve a circuit problem. The circuit impedance has the pole-zero pattern shown in Fig. 5 and has an impedance magnitude of  $10 \Omega$  at  $s = 1 \text{ s}^{-1}$ . The circuit is excited by a voltage source that is zero for negative time and has a value of  $v(t) = 5\cos(3t)$  for positive time.

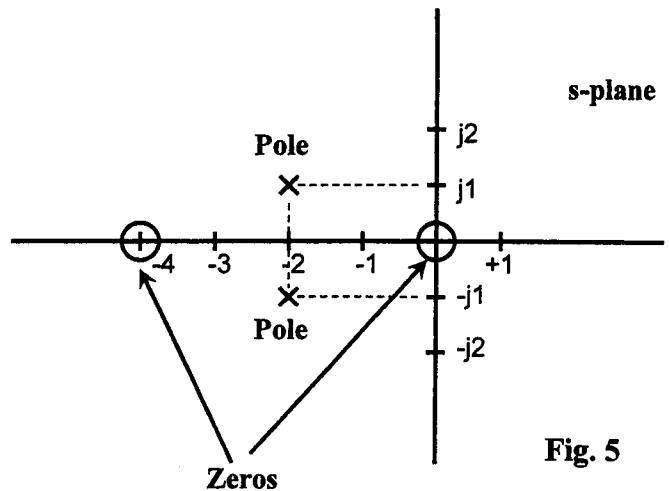


Fig. 5

- (a) Find the impedance  $Z(s)$  for the circuit.
- (b) Determine the total response of the current into the circuit for positive time, assuming zero for the initial value and initial derivative of the current.

6. (16%) By proper choice of  $X_C$  and  $X_L$ , the  $10\text{-}\Omega$  resistance in Fig. 6 can be transformed to “look” like a  $50\text{-}\Omega$  resistor (i.e., the impedance  $Z = 50 + j0\ \Omega$ ) at a specified frequency. Find  $X_C$  and  $X_L$  and, from them,  $C$  and  $L$  to accomplish this transformation at  $1\text{ kHz}$ .

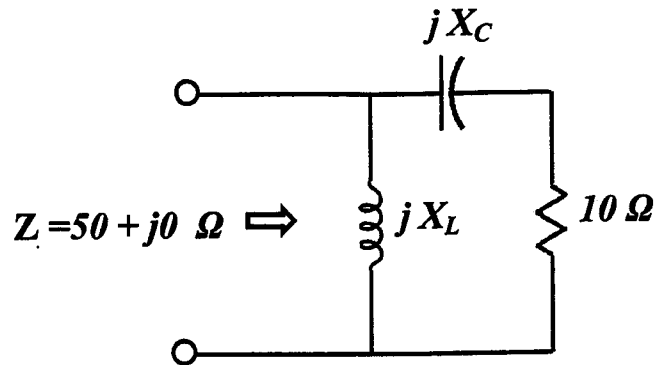


Fig. 6