

本試題是否可以使用計算機： 可使用， 不可使用（請命題老師勾選）

考試日期：0301，節次：2

There are a total of 6 problems in this exam.

1. (12%) For the circuit shown in Fig. 1, the switch is closed at $t = 0$. Solve for the current through the inductor $i_L(t)$ for $t > 0$.

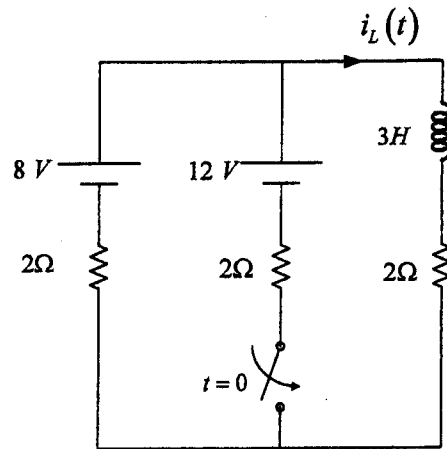


Fig. 1

2. The circuit shown in Fig. 2(a) can be represented by the Norton equivalent circuit in Fig. 2 (b).
 i) Determine the phasors I_N and Z_N (10%)
 ii) A load Z_L is connected to the circuit. For maximum average power transfer, find the average power transferred and Z_L . (8%)

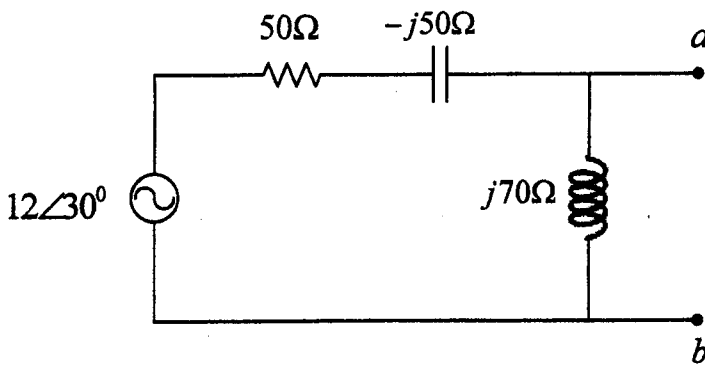


Fig. 2(a)

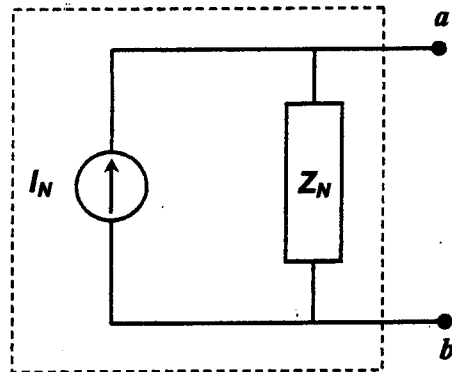


Fig. 2 (b)

3. (12%) The op-amp circuit shown in Fig. 3 has a transfer function

$$T(s) = \frac{V_{out}(s)}{V_{in}(s)} = -\frac{s+100}{s+20}$$

Design the values for C , R_1 and R_2 to realize the above transfer function.

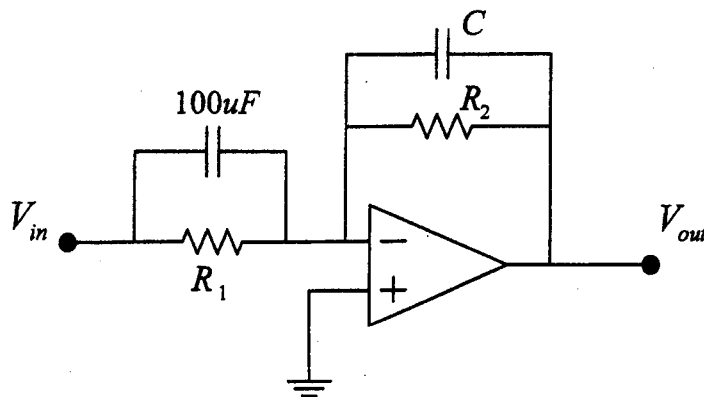


Fig. 3

(背面仍有題目,請繼續作答)

本試題是否可以使用計算機： 可使用， 不可使用（請命題老師勾選）

考試日期：0301，節次：2

4. For the circuit shown in Fig. 4,

i) Determine the resistance R which makes the transient response critical damping. (8%)

ii) For an input (V_{in}) of 0 at $t < 0$ and $10e^{-5t}$ at $t > 0$, determine the total response of $V_{out}(t)$ with a given $R = 5.2 \Omega$. (14%)

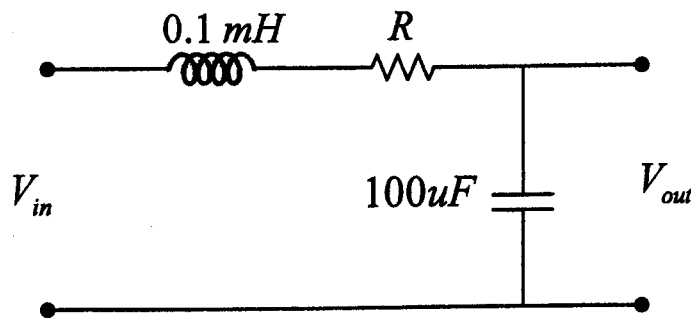


Fig. 4

5. (20%) The switch in the circuit shown in Fig. 5 has stayed at position a for a long time. At $t=0$, the switch is moved to position b . Determine the current $i_L(t)$ for $t > 0$.

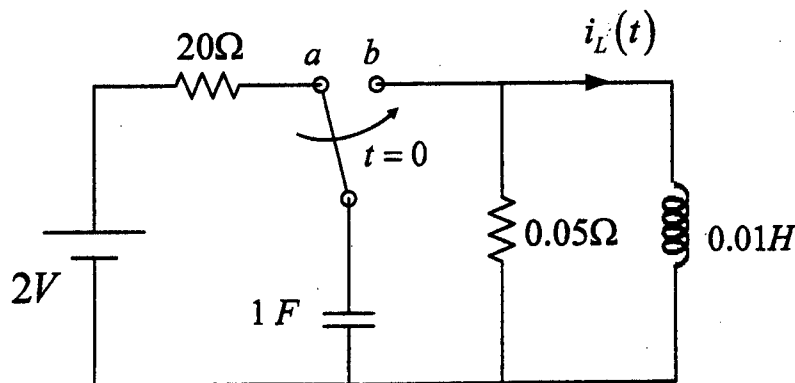


Fig. 5

6. (16%) The circuit shown in Fig. 6 has a current source of $i_s(t) = 15 \cos(2t + 45^\circ)$. Determine the voltage $V(t)$.

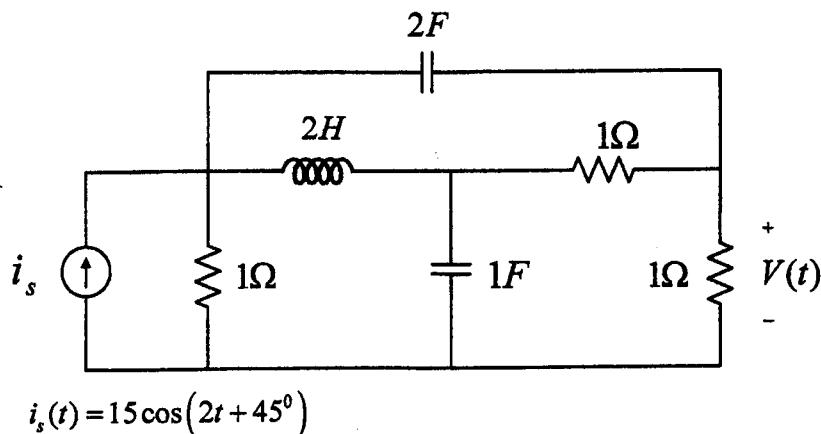


Fig. 6