

系所組別： 電機工程學系丙組

考試科目： 電路學

考試日期： 0220，節次： 1

※ 考生請注意：本試題 可 不可 使用計算機

1. For the circuit shown in Fig. P1, please determine:
  - (a) As  $Z = 10\Omega$  and  $v_s = 10V$ , what is the output voltage of  $v_o$ ? (10%)
  - (b) As  $Z = 100\mu F$ , what is the transfer function of  $v_o/v_s$ ? (10%)

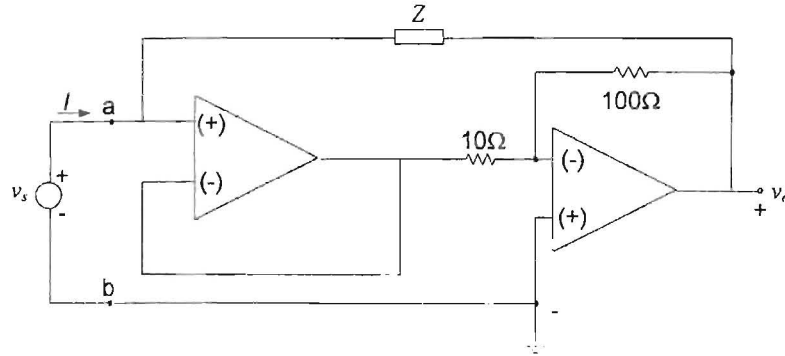


Fig. P1

2. Suppose in Fig. P2 the solar photovoltaic (PV) module has an open-circuit voltage of 90V and a short-circuit current of 3A in noonday sun. Assume the solar PV module is a linear circuit, though it may not be a very close approximation. As shown in the figure, the Solar PV module is used to charge a battery via a maximum-power tracker for maximum charging power. In the same noonday sun as above, please determine:
  - (a) What current should the maximum-power tracker require from the solar PV module? (5%)
  - (b) If the efficiency of the maximum-power tracker is 95%, what is the output power of the power tracker? (5%)

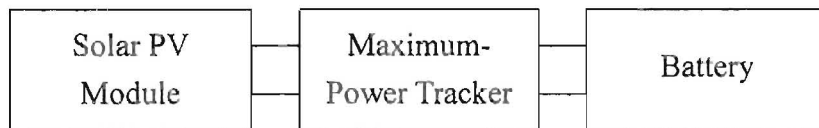


Fig. P2

3. In Fig. P3, the switch  $S_1$  has been closed for a very long time and is opened at  $t = 0$ . Please determine  $v(t)$  for  $t \geq 0$ . (20%)

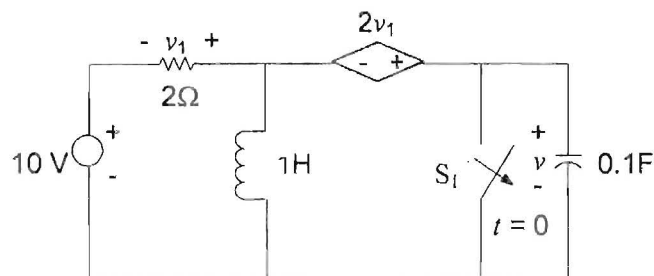


Fig. P3

(背面仍有題目,請繼續作答)

※ 考生請注意：本試題  可  不可 使用計算機

4. For the circuit shown in Fig. P4, the three-phase balanced  $\Delta$ -connected load has impedance of  $Z_{\Delta} = 60 + j80 \Omega/\text{phase}$  and the load is connected to a three-phase, 880 V, 60 Hz, acb-sequence balanced source. Determine:

- (a) the readings of the two wattmeters  $W_1$  and  $W_2$  and (10%)
- (b) the total active power  $P_T$  and the total reactive power  $Q_T$  of the load. (10%)

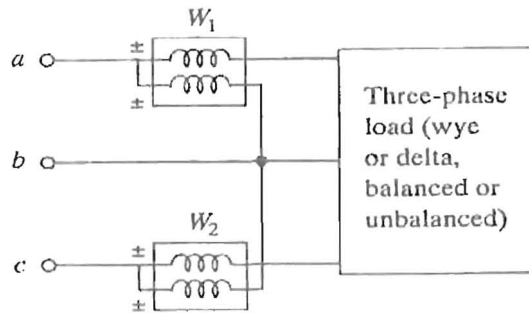


Fig. P4

5. For the ideal transformer circuit shown in Fig. P5, find the voltage  $V_o$ . (15%)

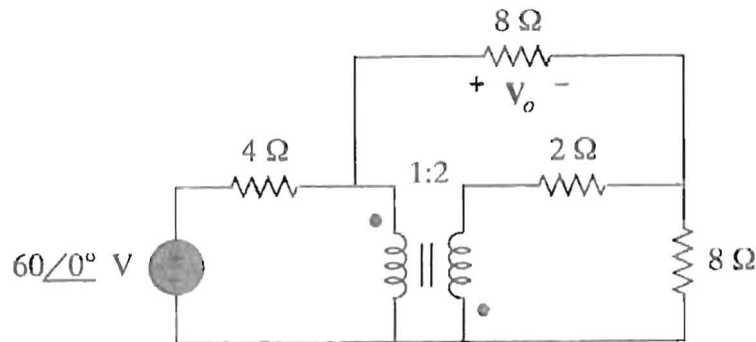


Fig. P5

6. If the current  $i(t)$  shown in Fig. P6 flows through a 100- $\Omega$  resistor, calculate the effective value and the average value of the current and the average power absorbed by the resistor. (15%)

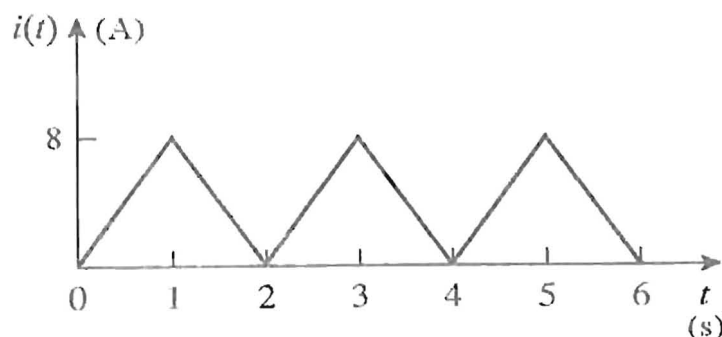


Fig. P6