

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. An ideal 9V Zener diode with zero incremental resistance is used in Fig. 1 for achieving voltage regulation.
 - (a) What is maximum load current I_L that can be drawn from the regulator if it is to maintain a regulated output? (5%)
 - (b) What is the minimum value of R_L that can be used and still have a regulated output voltage? (5%)

 


Fig. 1

2. Consider the amplifier circuit shown in Fig. 2, assume the transistor has $\beta=100$, $V_{BEQ}=0.7\text{V}$, and V_A (Early voltage) = 100 V.
 - (a) Find the dc bias current I_{CQ} . (4%)
 - (b) Calculate the overall (mid-band) voltage gain v_o/v_{sig} , assume that C_1-C_3 are all shorted (8%)
 - (c) What are the functions of capacitors C_1 , C_2 , and C_3 ? (3%)

 


Fig. 2

3. Consider the single amplifier biquad filter shown in Fig. 3, assume ideal operational amplifier is used.
- Please derive the transfer function, $V_O(s)/V_i(s)$, and find out its ω_0 and Q . (6%)
 - To realize a low-pass filter with $f_0=4$ KHz and maximally flat response, find the required values for C_1 and C_2 , if $R_1=R_2=10$ K Ω . (4%)

 


Fig. 3

4. Consider the circuit shown in Fig. 4, assume ideal operational amplifier is used.
- Please analysis and draw v_o-v_i transfer curve. (5%)
 - For a triangular input waveform, please draw the corresponding output voltage waveform (correct scale required). (5%)

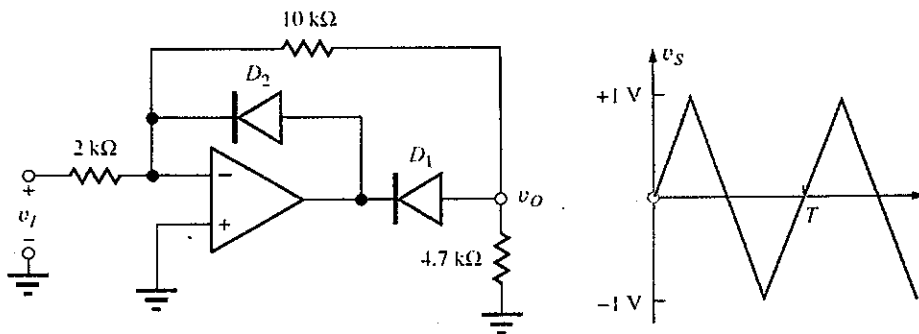


Fig. 4

5. The maximum junction temperature rating of a certain power transistor is 200°C. For a case temperature of 25°C, the maximum allowed power dissipation is 15W.
- Find the junction-to-case thermal resistance. (2%)
 - If this transistor is operated with a case-to-sink thermal resistance of 1°C/W in an ambient temperature of 75°C and with a power dissipation of 5W, find the maximum allowed sink-to-ambient thermal resistance. (3%)

6. As shown in Fig. 5, the op amp is ideal.
- Find the resistance looking into node 4, R_4 , in terms of R . (4%)
 - Find the current I_4 in terms of the input current I . (4%)
 - Find the voltage at node 4, that is V_4 , in terms of (IR) . (4%)

 


Fig. 5

7. Considering the design error because of the gross mismatch in the circuit of Fig.6. Specifically, Q_2 has twice the W/L ratio of Q_1 . If v_{id} is a small sine-wave signal and $k_n = \mu_n C_{ox}$, find:
- I_{D1} and I_{D2} in terms of I (4%)
 - V_{ov} ($=V_{GS} - V_{TH}$) for each of Q_1 and Q_2 in terms of I , k_n , and W/L (4%)
 - The differential gain A_d ($=V_{od}/V_{id}$) in terms of R_D , I , and V_{ov} (4%)

 


Fig. 6

8. Find the midband gain A_M (5%) and the upper 3-dB frequency f_H (5%) of a CS amplifier (Fig. 7) fed with a signal source having an internal resistance $R_{sig}=10\text{ k}\Omega$. The amplifier has $R_G=4.7\text{ M}\Omega$, $R_D=R_L=20\text{ k}\Omega$, $g_m=1\text{ mA/V}$, $r_o=100\text{ k}\Omega$, $C_{gs}=1\text{ pF}$, and $C_{gd}=0.4\text{ pF}$.

 


Fig. 7

9. Considering the transresistance amplifier with feedback as shown in Fig. 8, if $g_m=5\text{ mA/V}$, $r_o=50\text{ k}\Omega$, $R_f=10\text{ k}\Omega$, and $R_s=2\text{ k}\Omega$
- Find open-loop voltage gain A (4%)
 - Find the closed-loop gain $A_f = V_o/I_s$ (4%)
 - Find the input resistance R_{in} (4%)
 - Find the output resistance R_{out} (4%)

 


Fig. 8