

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. (15%) Three single-phase two-winding transformers, each rated 20kVA, 400/1000 V, with leakage reactance $X_{eq}=0.1$ per unit, are connected together to form a three-phase transformer. High voltage side is connected in Y and low voltage side is connected in Δ . Winding resistance and excitation current are neglected. A three-phase load connected at high voltage side absorbs 50kVA at 0.8 power factor lagging with phase voltage $V_{AN} = 1000V \angle 0^\circ$. Consider the phase shift between Δ and Y, determine the followings:
- phase a current I_a at low voltage side in per unit.
 - phase voltage V_{an} at the terminal of low voltage side in per unit.
 - magnitude of line-to-line voltage at low voltage side in real unit.

2. (15%) The zero-, positive-, negative-sequence bus impedance matrices for a three-bus three-phase power systems are shown as follows:

$$Z_{bus 0} = j \begin{bmatrix} 0.1 & 0 & 0 \\ 0 & 0.2 & 0 \\ 0 & 0 & 0.1 \end{bmatrix} \text{ per unit}$$

$$Z_{bus 1} = Z_{bus 2} = j \begin{bmatrix} 0.12 & 0.08 & 0.04 \\ 0.08 & 0.12 & 0.06 \\ 0.04 & 0.06 & 0.08 \end{bmatrix} \text{ per unit}$$

Assume the **prefault voltage is 1 per unit**, prefault current is neglected.

Determine the followings:

- per unit fault current at bus 2 if a three-phase bolted ground fault takes place at bus 2.
 - per unit sequence fault current at bus 2 if a single line-to-ground fault takes place from a phase to ground at bus 2.
 - Continue on section B, calculate per unit sequence voltage at bus 1.
3. (10%) A power system has two fossil-fueled units with the following operating cost functions.
 $C_1 = 10P_1 + 8 \times 10^{-3} P_1^2$, $C_2 = 8P_2 + 10 \times 10^{-3} P_2^2$ in \$/MWh
 where P_1 and P_2 are in megawatts. Each generating unit has the following output constraints
 $100 \leq P_1 \leq 600\text{MW}$, $400 \leq P_2 \leq 1000\text{MW}$.
 These two units are to support total load of 1300MW **on economic dispatch**.
 Determine the followings:
- power output of each unit.
 - total operating cost.

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

4. Plot the topology of the ideal CCM DC-DC Buck-Boost converter (4%) and use the volt-second balance equation to derive its voltage conversion ratio (6%).
5. Plot the topology of the ideal CCM DC-DC SEPIC converter (4%) and use the volt-second balance equation to derive its voltage conversion ratio (6%).
6. Plot the topology of the ideal CCM DC-DC Cúk converter (4%) and use the volt-second balance equation to drive it voltage conversion ratio (6%).
7. Plot the topology of the ideal CCM DC-DC forward converter (4%) and use the volt-second balance equation to derive it voltage conversion ratio (6%).
8. Plot the equivalent circuit of the non-ideal transformer, containing one ideal transformer, two leakage inductors, one magnetizing inductor, one primary-to-secondary parasitic capacitor, and two equivalent series resistors. Then, derive its voltage conversion ratio from the primary side to the secondary side at no-load condition (10%).
9. Plot the topology of the ideal voltage step-down autotransformer (4%) and derive its voltage conversion ratio (6%).