

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. As shown in Fig. 1, the op amp has  $V_{OS}=4\text{ mV}$  and the output saturation voltages of  $\pm 12\text{ V}$ . Consider a Miller integrator with a time constant of  $1\text{ ms}$  and  $R=20\text{ k}\Omega$ 
  - (a) Assume that, when the power supply is turned on, the capacitor voltage is zero, how long does it take for the amplifier to saturate (neglected  $R_F$ )? (4%)
  - (b) Select the largest possible value for a feedback resistor  $R_F$  so that at least  $\pm 10\text{ V}$  of output signal swing remains available. (4%)
  - (c) What is the corner frequency of the resulting single-time constant (STC) network? (4%)

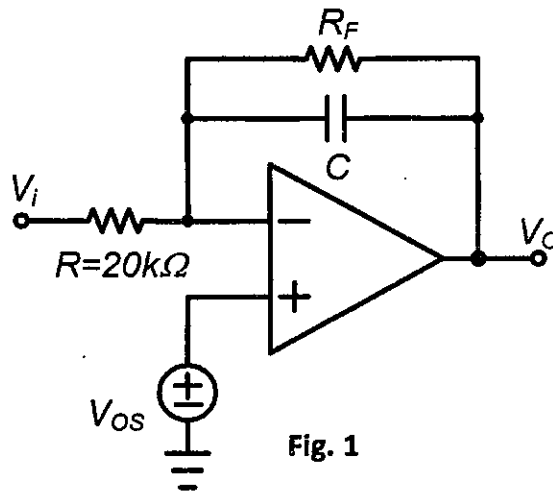


Fig. 1

2. The op amp in the precision rectifier circuit of Fig. 2 (a) is ideal with output saturation levels of  $\pm 13\text{ V}$ . Assume that when conducting the diode exhibits a constant voltage drop of  $0.7\text{ V}$ .
  - (a)  $V_i=+3\text{ V}$ , find  $V_O$  and  $V_A$ ? (4%)
  - (b)  $V_i=-1\text{ V}$ , find  $V_O$  and  $V_A$ ? (4%)
  - (c) Find the average output voltage obtained when  $V_i$  is a symmetrical square wave of  $1\text{-kHz}$  frequency,  $5\text{-V}$  amplitude, and zero average as shown in Fig. 2(b) (4%)

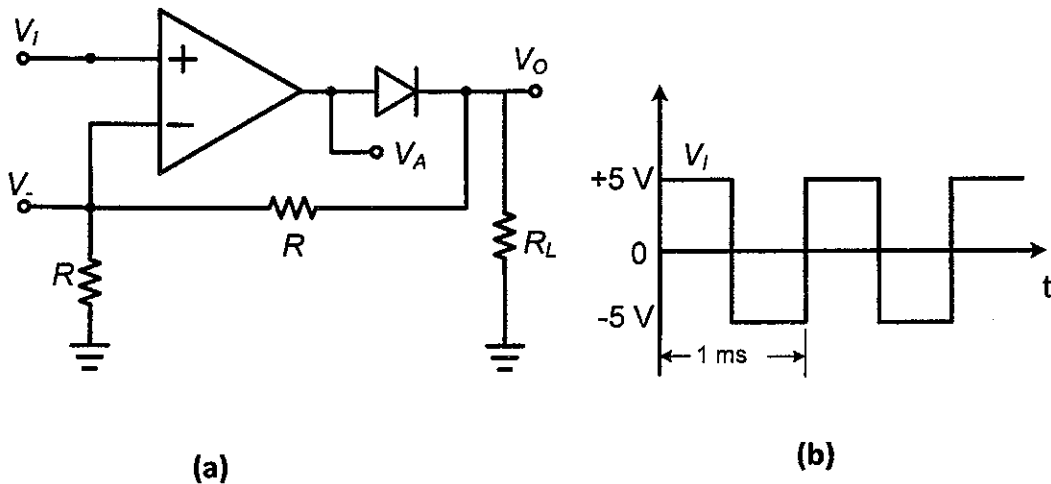


Fig. 2

3. As shown in Fig. 3, an IC CG amplifier is fed from a signal source with  $R_{sig}=r_o/2$ , where  $r_o$  is the MOSFET output resistance. It has a current-source load with an output resistance equal to  $r_o$ . The MOSFET is operated at  $I_D=100 \mu A$  and has  $g_m=1.5 \text{ mA/V}$ ,  $V_A=10 \text{ V}$ ,  $C_{gs}=0.2 \text{ pF}$ ,  $C_{gd}=15 \text{ fF}$ ,  $C_{db}=20 \text{ fF}$ , and  $C_L=30 \text{ fF}$  (neglected body effect).

- (a) Determine the input resistance,  $R_{in}$  (4%)
- (b) Find the output resistance,  $R_{out}$  (4%)
- (c) Find the midband gain,  $A=V_o/V_{sig}$  (4%)
- (d) Find the upper 3-dB frequency,  $f_H$ , using the method of open-circuit time constant (4%)

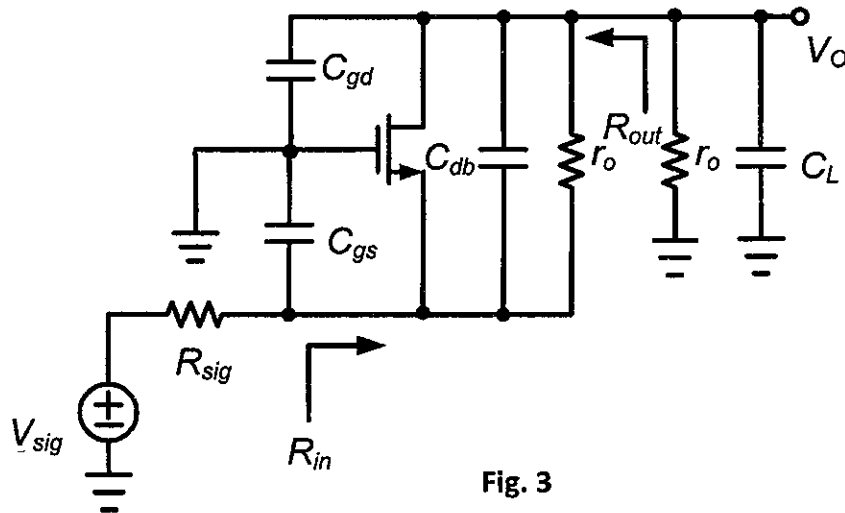


Fig. 3

4. Considering the multi-stage amplifier with feedback as shown in Fig. 4, if all three MOSFETs are biased to operate at  $g_m=4 \text{ mA/V}$ . You may neglect their  $r_o$ 's (channel-length modulation effect)

- (a) Select a value for  $R_F$  that results in a closed-loop gain that is ideally 10 V/V (3%)
- (b) Determine the loop gain,  $A\beta$  (4%), and hence the value of closed-loop gain,  $A_f$  (3%)

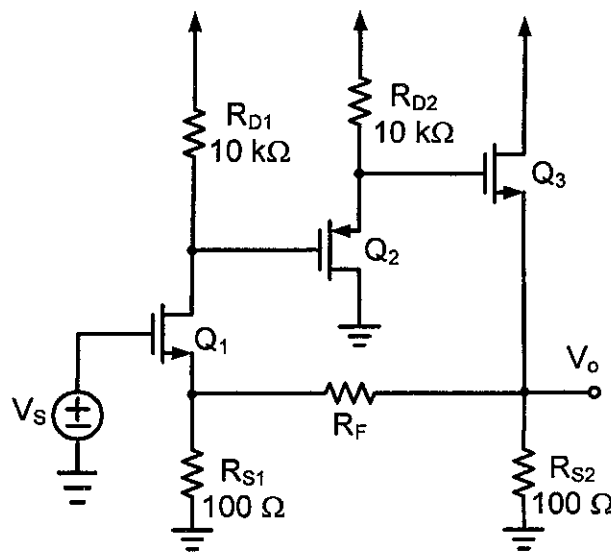


Fig. 4

5. An internally compensated op amplifier has a dc open-loop gain of  $10^6$  V/V and an ac open-loop gain of 40 dB at 10 kHz. Please estimate its 3-dB frequency (3%) and its gain-bandwidth product (3%).
6. An op amplifier having 106 dB gain at dc and a single-pole frequency response with unity-gain frequency  $f_t = 2$  MHz is used to design a non-inverting amplifier with nominal dc gain of 100. Please find the 3-dB frequency of the resulting amplifier. (5%)
7. For the circuit shown in Fig. 5, assuming that the op amplifier saturates at  $\pm 12$  V and the diodes have a constant 0.7V drop when conducting.
  - (a) Sketch and label the  $v_o$ - $v_i$  transfer characteristic. (6%)
  - (b) What is the maximum diode current? (3%)

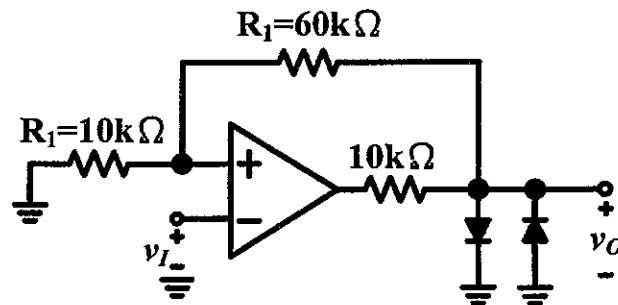


Fig. 5

8. For the output stage circuit shown in Fig. 6,  $V_{CC} = 15$  V,  $V_{CEsat} = 0.2$  V,  $V_{BE} = 0.7$  V (constant), and  $\beta$  is very high.
  - (a) Find the value of R that will establish a bias current sufficiently large to allow the largest possible output signal swing for  $R_L = 1$  k $\Omega$ . (4%)
  - (b) Determine the resulting output signal range (2%) and the minimum/maximum current for  $Q_1$  (2%).
  - (c) If the output voltage is an 8V-peak sinusoid, find (1) the power delivered to the load (2%); (2) the average power drawn from the supplies (2%); (3) the power-conversion efficiency (ignore the loss in  $Q_3$  and R). (2%).

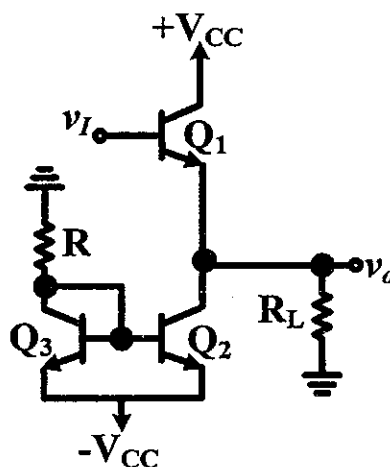


Fig. 6

9. For a second-order bandpass filter with center frequency of  $10^5$  rad/sec, a center-frequency gain of 10, and a 3-dB bandwidth of  $10^3$  rad/sec. Please derive and write down its s-domain transfer function. (6%)

10. Consider the circuit of Fig. 7. Break the loop at node X and find the resulting loop gain.

(a) Find the possible frequency of oscillation. (5%)

(b) Find the minimum value of  $R_f/R$  required for oscillation. (5%)

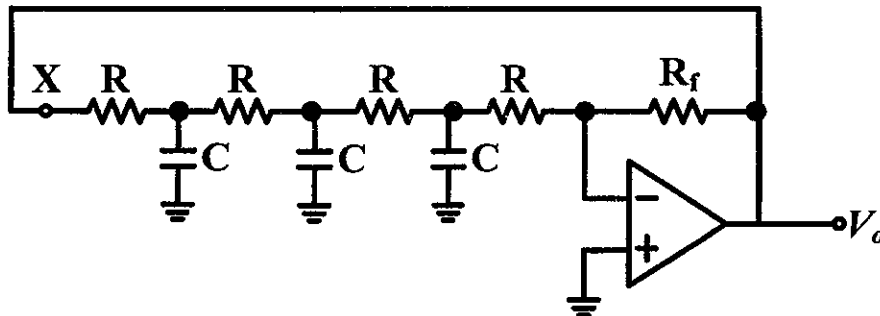


Fig. 7