

國立成功大學  
110學年度碩士班招生考試試題

編 號：171

系 所：電機工程學系

科 目：電力工程


日 期：0202


節 次：第 2 節

備 註：可使用計算機

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

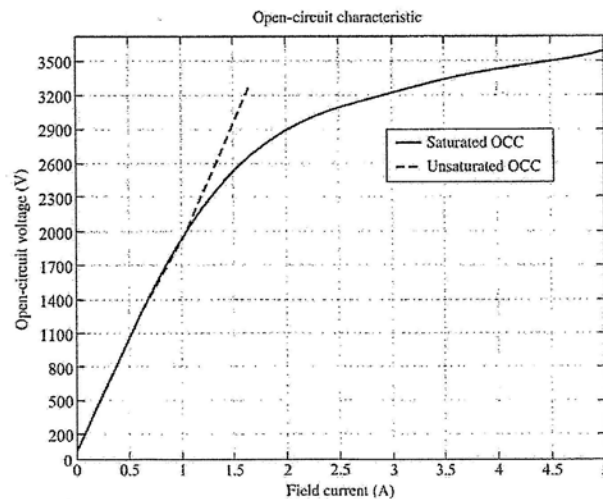1. (10%) The power crossing the air gap of a 60-Hz, six-pole induction motor is 50 kW, and the power converted from electrical to mechanical form in the motor is 47.5 kW.
  - (a) (3%) What is the slip of the motor at this time?
  - (b) (4%) What is the induced torque in this motor?
  - (c) (3%) Assuming that the mechanical losses are 750 W at this slip, what is the load torque of this motor?
2. (20%) A 100-MVA, 10/200-KV, single-phase power transformer has a per-unit resistance of 1.0 percent and a per-unit reactance of 5.0 percent. The magnetizing impedance is  $j100$  per unit.
  - (a) (5%) Find the equivalent circuit referred to the low-voltage side of this transformer.
  - (b) (5%) Calculate the voltage regulation of this transformer for a full-load current at power factor of 0.8 lagging.
  - (c) (4%) Calculate the copper loss in the transformer at the conditions in (b).
  - (d) (6%) Calculate the voltage regulation of this transformer for a full-load current at power factor of 1.0 and 0.8 leading.
3. (20%) A six-pole, Y-connected synchronous generator rates at 345 kVA, 2.0 kV, 0.9 PF lagging, and 60 Hz. Its armature resistance  $R_A$  is  $1.0 \Omega$ . The open-circuit and short-circuit characteristics are shown in the following figures.
  - (a) (6%) What is the saturated synchronous reactance of this generator at the rated conditions?
  - (b) (6%) What are the rated current and internal generated voltage of this generator?
  - (c) (4%) What field current does this generator require to operate at the rated voltage, current and power factor?
  - (d) (4%) What is the voltage regulation at the rated condition and power factor?



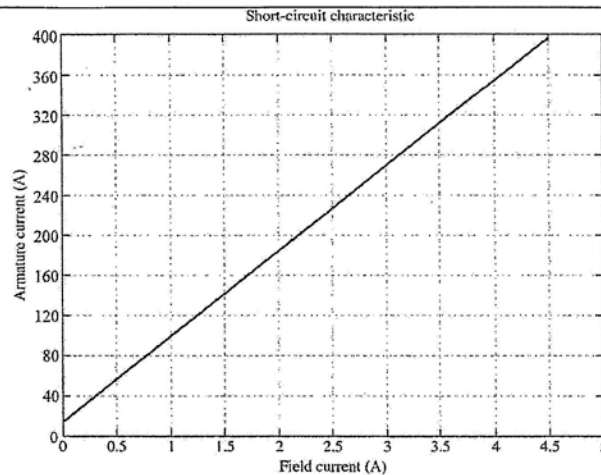

4. (35%) A 10kVA, 220 $\angle 0^\circ$  V, single phase generator is connected to a 20kVA 240/120V step-down transformer with a series reactance of 0.1pu on its own base. The load is connected at the 120V terminal with  $Z_{load} = 1.21 + j0.968\Omega$ . Take 10kVA and 220V as a common base and do the followings:
- (10%) Draw the per-unit circuit and determine the per-unit impedances and per-unit source voltage.
  - (10%) Calculate the load current both in per-unit and in ampere.
  - (5%) If the power factor at load side needs to be improved to 0.95 lagging, please calculate the reactive power in per-unit of the capacitor that is delivered at the load side.
  - (10%) If a sudden three phase fault occurs at the 120V side of the transformer, calculate the current in per-unit at the point of fault and the current in per-unit from the generator side.
5. (15%) Consider a synchronous generating unit connected through two parallel lines to an infinite bus. Suppose the unit is initially operating in steady state at mechanical power  $P_{m0}$  with power angle  $\delta_0$ , a three-phase short circuit bolted fault occurs at one of the line closing to the sending end bus and causes the generator power angle start to increase from  $\delta_0$ . As the power angle increase from  $\delta_0$  to  $\delta_1$ , the faulted line was removed. Then the power angle reaches its maximum value at  $\delta_2$  and then comes back to its new steady state value at the new steady state point  $\delta_3$ . Please plot the electrical power curve of  $P_e$  and mechanical power  $P_m$  versus power angle  $\delta$  by notating  $\delta_0 \sim \delta_3$  to describe the equal-area criterion.