

# 國立成功大學

## 115學年度碩士班招生考試試題

編號：131、134

系所：電機工程學系  
通訊工程研究所

科目：電子學

日期：0203

節次：第 1 節

注意：1. 可使用計算機  
2. 請於答案卷(卡)作答，於  
試題上作答，不予計分。

1. Design the circuit in Fig. 1 to obtain a dc voltage of +0.1 V at each of the drains of  $Q_1$  and  $Q_2$  when  $V_{G1}=V_{G2}=0$  V. Operate all transistors at  $V_{GS}-V_{tn}=V_{OV}=0.15$  V and assume that for the process technology in which the circuit is fabricated,  $V_{tn}=0.4$  V and  $\mu_n C_{ox}=400 \mu\text{A}/\text{V}^2$ . Neglect channel-length modulation.
  - (a) Determine the values of  $R$  and  $R_D$  (10%)
  - (b) Find the  $W/L$  ratios of  $Q_1$ ,  $Q_2$ ,  $Q_3$ , and  $Q_4$  (20%)
  - (c) What is the input common-mode voltage range for your design? (10%)

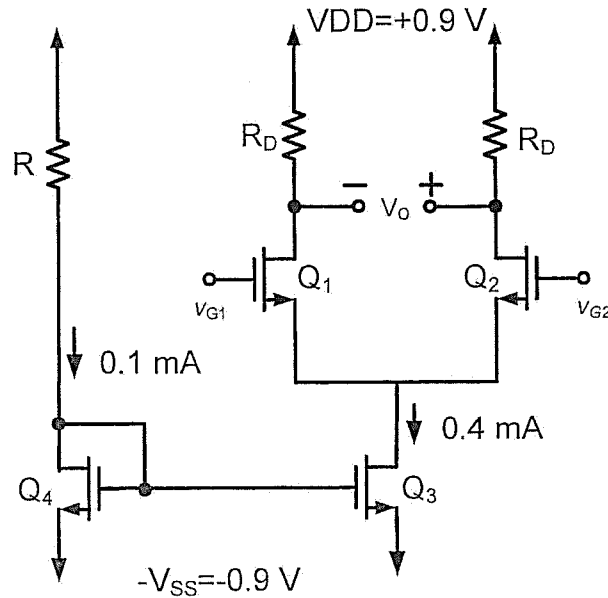


Fig. 1

2. Consider the circuit of Fig. 2 for the case:  $I = 200 \mu\text{A}$  and  $V_{GS}-V_{tn}=V_{OV}=0.2$  V,  $R_{sig}=100 \text{ k}\Omega$ ,  $R_D=50 \text{ k}\Omega$ ,  $C_{gs}=4 \text{ pF}$ , and  $C_{gd}=0.5 \text{ pF}$ .
  - (a) Find the dc gain (10%)
  - (b) Find the high-frequency poles ( $f_{p1}$  and  $f_{p2}$ ) (10%)
  - (c) Find the estimated -3 dB frequency ( $f_H$ ) (10%)

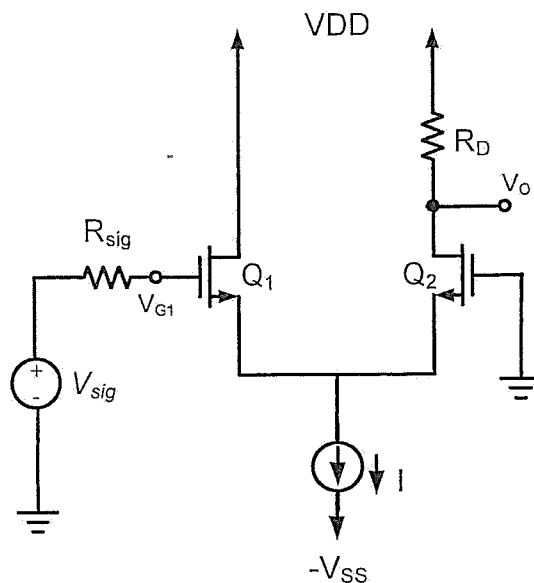


Fig. 2

3. The feedback current amplifier in Fig. 3 can be thought of as a “super” common gate (CG) transistor. Note that rather than connecting the gate of  $Q_2$  to the signal ground, an amplifier is placed between the source and gate.  $g_{m2} = 1 \text{ mA/V}$  and  $r_{o2} = 50 \text{ k}\Omega$  are the transconductance and output resistance of transistor  $Q_2$ , respectively.
- If  $\mu$  is infinite, what is the signal voltage at the input terminal ( $V_{in}$ )? What is the input resistance ( $R_{in}$ )? What is the current gain  $I_o/I_i$ ? (3%)
  - For finite  $\mu=1000$ , but assuming that the input resistance ( $R_{id}$ ) of the amplifier is infinite, find the values and derive expressions for  $A$ ,  $R_i$ , and  $R_o$  of the open-loop gain ( $A$ ) circuit. (9%)
  - What is the value of the feedback factor  $\beta$ ? (3%)
  - Find  $A\beta$  and  $A_f$ . If  $\mu$  is infinite, what is the value of  $A_f$ . (9%)
  - Find  $R_{in}$  and  $R_{out}$ . (6%)

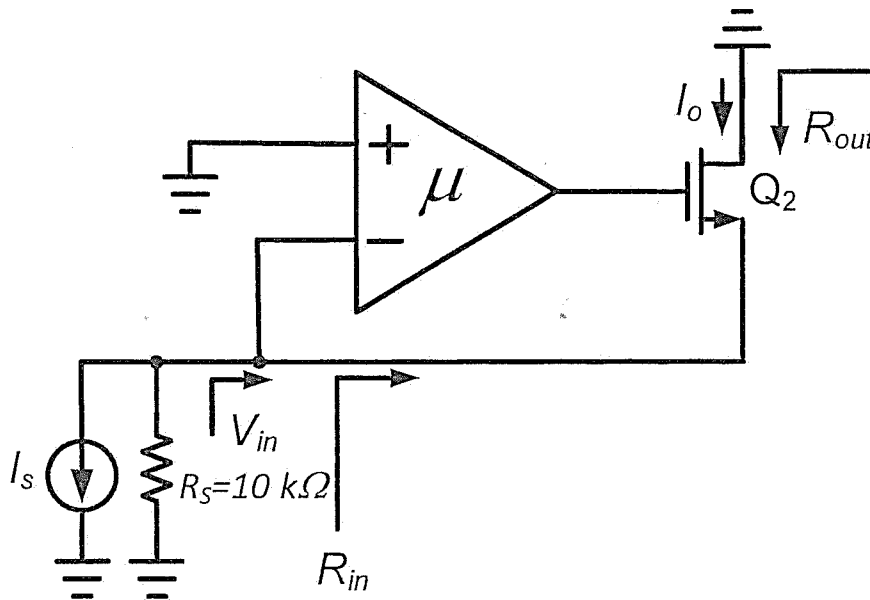


Fig. 3