

國立成功大學

115學年度碩士班招生考試試題

編 號： 121

系 所： 電機工程學系

科 目： 電路學

日 期： 0203

節 次： 第 1 節

注 意： 1. 可使用計算機
2. 請於答案卷(卡)作答，於
試題上作答，不予計分。

1. The voltage across an unknown electric device (a black box) is given by

$$v(t) = -2 + 10\cos(4t) + 8\cos(6t) + 6\cos(8t) - 5\sin(4t) - 3\sin(6t) - \sin(8t) \text{ V}$$

Please find the period, the average value, and the effective value of $v(t)$. (25%)

2. Please solve for the voltage gain $A_v = v_o/v_i$ of the ideal operational amplifier circuit shown in Fig. 2 if $R_f = 500 \text{ k}\Omega$, $R_1 = 25 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$, $R_3 = 2 \text{ k}\Omega$, $R_S = 20 \text{ k}\Omega$, $R_T = 30 \text{ k}\Omega$, $R_U = 40 \text{ k}\Omega$, and $R_V = 80 \text{ k}\Omega$. (25%)

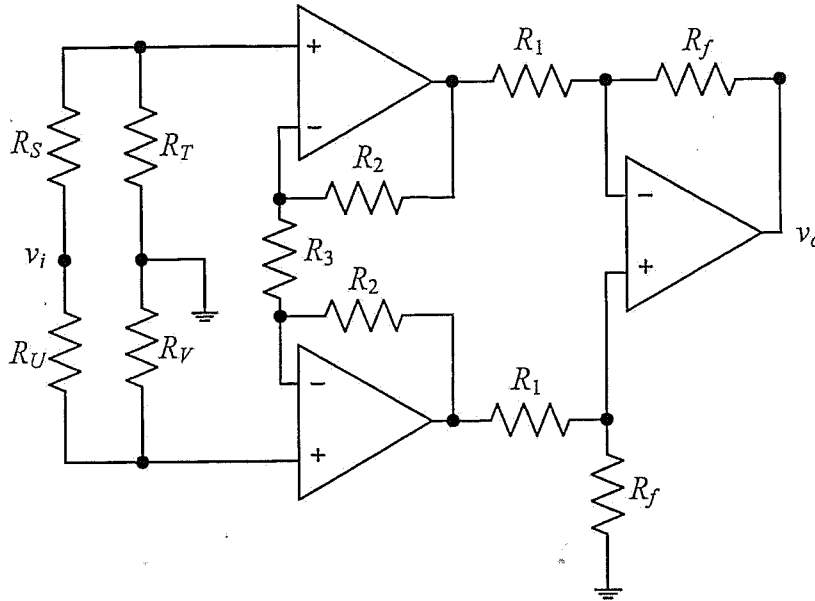


Fig. 2.

3. Please compute the z or open-circuit impedance parameters for the network in Fig. 3 when $R_a = 2 \Omega$, $R_b = 8 \Omega$, $R_c = 12 \Omega$, and $R_d = 4 \Omega$. (25%)

4. The switch in Fig. 4 has been open for a long time and is suddenly closed at $t = 0 \text{ s}$. Please determine $v(t)$ for $t > 0 \text{ s}$ if $I_{s1} = 4 \text{ A}$, $R_{s1} = 1 \Omega$, $I_{s2} = 2 \text{ A}$, $R_{s2} = 6 \Omega$, $L = 1 \text{ H}$, and $C = 0.04 \text{ F}$. (25%)

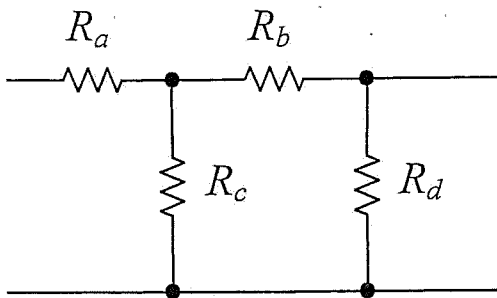


Fig. 3.

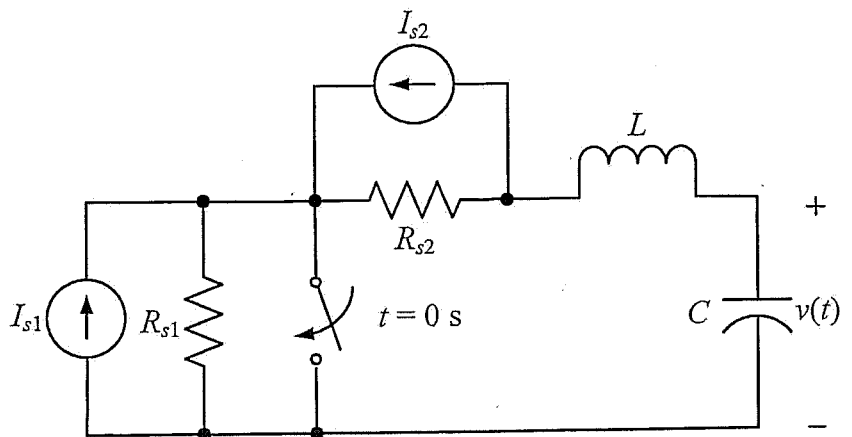


Fig. 4.