

國立成功大學

115學年度碩士班招生考試試題

編 號：124

系 所：電機工程學系

科 目：電儀表學

日 期：0203

節 次：第 2 節

注 意：1. 可使用計算機
2. 請於答案卷(卡)作答，於
試題上作答，不予計分。

1. (15%) As Fig. 1 displays, assumed the PMMC meter's accuracy is $\pm 2\%$ as the pointer stays at 200 μA , and the full scale is 400 μA . Please find the accuracy at I_{FSD} and the relative error of measuring an unknown resistance (R_x) with this PMMC meter when $I_m = 0.75 I_{\text{FSD}}$.

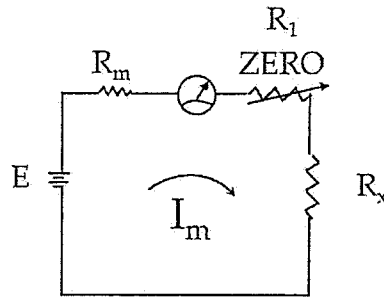


Fig. 1

2. (15%) For a Half-wave Average-Reading circuit as Fig. 2 shown, $R_m = 330 \Omega$, $I_{\text{FSD}} = 150 \mu\text{A}$, $V_D = 0.7\text{V}$, find R_s for full-scale 3.3 V_{rms} range.

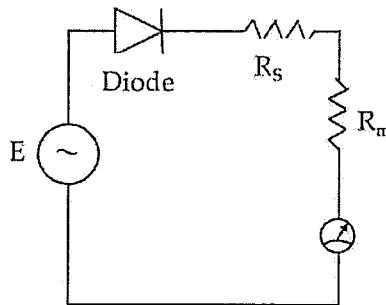


Fig. 2

3. (20%) As Fig. 3 illustrates, a Wheatstone Bridge with $P=2 \text{ k}\Omega$, $Q=3 \text{ k}\Omega$, $S=1.5 \text{ k}\Omega$, $E=10 \text{ V}$, minimum adjustable $\Delta S=\pm 0.3 \Omega$, $R_m=0.5 \text{ k}\Omega$, and $I_G(\text{min})=1 \mu\text{A}$. Find the resolution of the Wheatstone Bridge when measuring unknown resistance R.

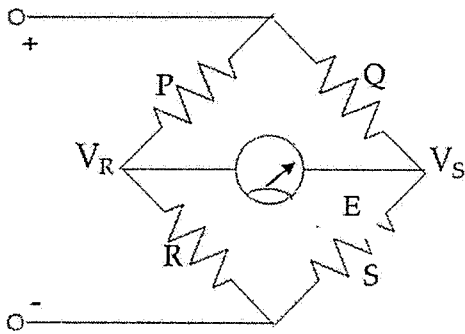


Fig. 3

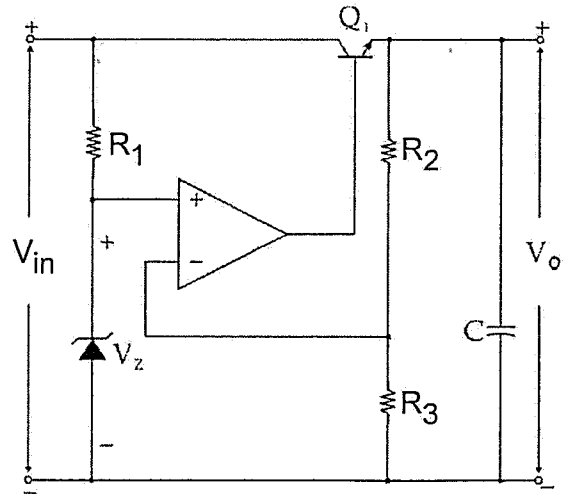


Fig. 4

4. (20%) As Fig. 4 illustrates, the input voltage (V_{in}) is 20 V. The breakdown voltage of the Zener diode (V_Z) is 4 V when its current is 10 mA, and V_Z increases to 4.05 V when its current increases to 20 mA. In addition, $R_2 = 4 \text{ k}\Omega$ and $R_3 = 8 \text{ k}\Omega$. (a) (4%) What is the function of this circuit? (b) (6%) Please calculate the dynamic resistance of the Zener diode (i.e., its equivalent resistance at its quiescent operating point). (c) (5%) Please calculate its output voltage (V_o) when the current of the Zener diode is 10 mA. (d) (5%) Please calculate the value of R_1 to make $V_Z = 4 \text{ V}$.

5. (15%) The block diagram of Superheterodyne Spectrum Analyzer is shown below (Fig. 5). (a) (5%) Explain the operations of figure below. (b) (5%) Show the output spectrum of the mixer. (c) (5%) If f_s is 2 GHz, f_{LO} sweeps from 4 to 7 GHz, and the waveform of LCD display is shown in figure, please plot the corresponding IF filter.

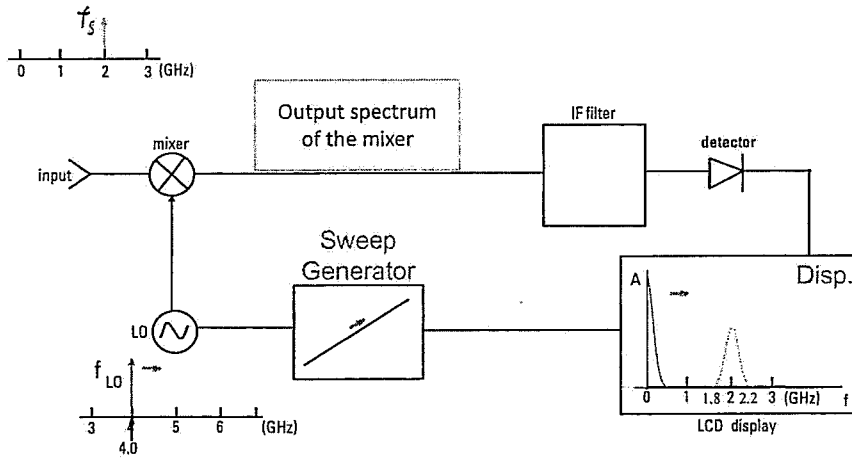


Fig. 5

6. (15%) The Q-meter circuit in Fig. 6 is in resonance when $E = 100$ mV, $R = 5 \Omega$, and $|X_L| = |X_C| = 200 \Omega$. Calculate the Q of the coil and the voltmeter (V_C) indication.

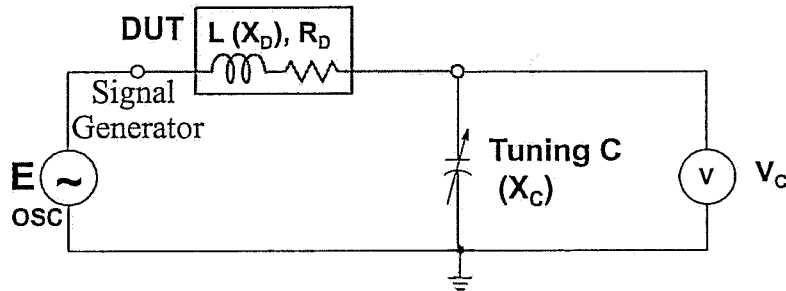


Fig. 6