

請依題號順序作答:

1. (a) How to determine the contact potential and ideal factor of an abrupt p-n junction? (5%)
 (b) What are the advantages of poly-silicon gate MOS process? (5%)
 (c) What is the real meaning of "TTL compatible"? Why does the ECL family have the lowest propagation delay? (5%)
2. (a) Explain how to measure time by means of a counter. (5%)
 (b) Sketch the block diagram of a PLA. How is PLA related to a ROM? (5%)
 (c) Draw the circuit of a Wilson current source and list two advantages. (5%)
 (d) Describe the LARAM organization of a CCD memory. (5%)
3. For the practical integrator shown in Fig. 1,
 (a) verify that the bias current through C is the input offset current I_{io} , (5%)
 (b) if the initial energy of C is zero, find $v_o(t)$. (5%)
4. (a) Explain why a switching regulator is capable of very high conversion efficiency. (3%)
 (b) Verify that, if the switching frequency (f_s) is much greater than the frequency of signal, a switched capacitor is equivalent to a resistance. (3%)
 (c) In a Schmitt trigger, what will happen if the system loop gain is less than 1? why? (3%)
 (d) From both dc and ac point of views, state the basic requirements of a level-shift network. (3%)
 (e) Explain how to use Bode plot and Nyquist diagram to test the stability of a feedback system. (3%)
5. (a) Find the transfer function of the active-RC filter shown in Fig. 2. (5%)
 (b) Sketch its frequency-response characteristics and determine what type of this filter is. (5%)
6. (a) If the common-emitter BJT (see Fig. 3) is operated under high frequency condition, draw the unilateral hybrid- π equivalent circuit by use of Miller's theorem. Assume the current in C_{μ} is negligibly small. (5%)
 (b) If the denominator of $A_{vH}(s) (= V_o(s)/V_i(s))$ is expressed as $(1 + a_1s + a_2s^2)$, use the time-constant method to calculate a_1 . (5%)
7. Assume the Op-Amp shown in Fig. 4 has infinite input impedance and zero output impedance, (a) determine the return ratio $T(s)$, (b) find the pole frequency ω_0 and the pole Q factor. (5% + 5%)
8. (a) Describe briefly the operation of the circuit shown in Fig. 5. (5%)
 (b) Assume a 5 V Zener diode, a current gain from base to emitter of 70, and a load current of 210 mA. Calculate a value for R that will set the Zener current to one third of the base current of the transistor. (5%)

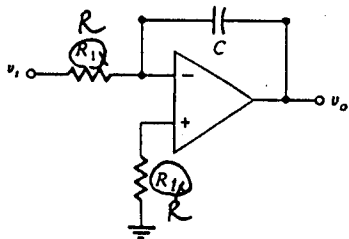


Fig. 1

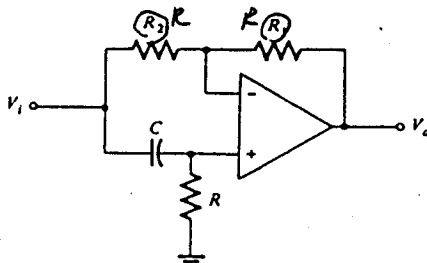


Fig. 2

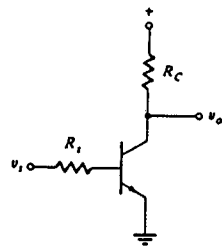


Fig. 3

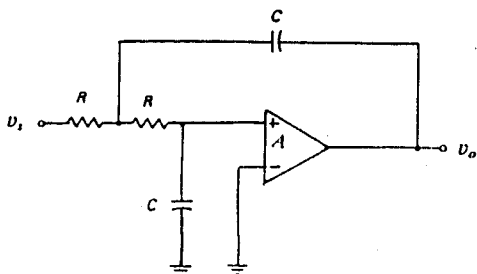


Fig. 4

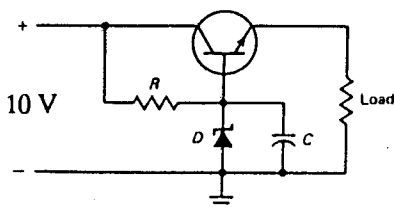


Fig. 5