
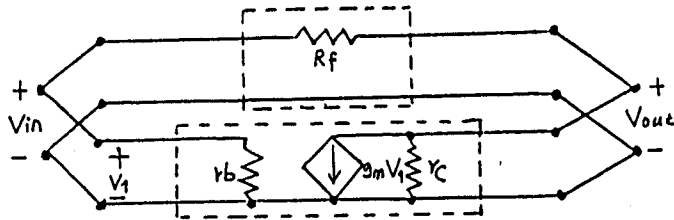


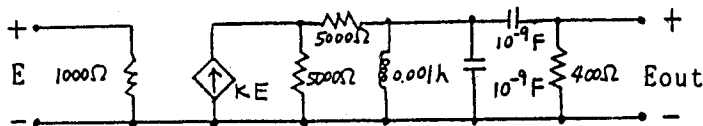- Describe the physical meanings of the following terms: (5% each)
  - phasor
  - maximum power transfer theorem
  - quality factor
  - load line
- Using y-parameters, obtain the total circuit y-parameters for the circuits indicated by the dashed lines. Hint: first find the y-parameters of the two indicated two-port networks, then combine them to obtain the total network y-parameters. (20%)





- An oscillator circuit is shown. Determine the minimum value of  $K$  such that  $E_{out} = E$ . Also, find the frequency at which  $E_{out} = E$ . (20%)



- The source in the RLC circuit shown in (a) has a frequency of 1 kHz, being the resonance frequency of this circuit. The oscillogram obtained with the scope connected as indicated is shown in (b). Here:

YA: V/div = 20    YB: V/div = unknown

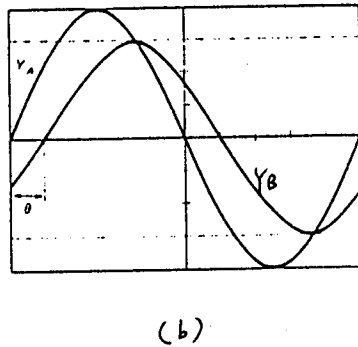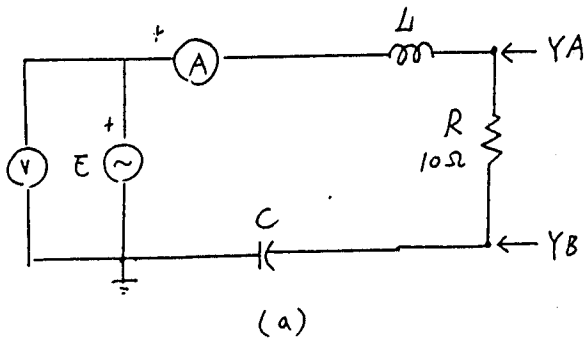- Find YB (V/div) and the readings of the voltmeter and ammeter. (10%)
- Find the values of L and C. (10%)



- Obtain the standard matrix state equation for the circuit shown. The initial state is zero. (20%)

