

1. (a) Draw the cross-sectional diagram of an NMOS transistor operated in saturation region and give the drain current equation for it to include the channel-length modulation effect. What is the relationship between Early voltage and output resistance ? (10%)  
 (b) Given a diode, how to determine the SPICE parameters emission coefficient N, ohmic resistance  $R_S$ , and junction grading coefficient M from experiment ? (10%)
2. Explain briefly (a) what is the totem-pole output structure for a TTL NAND gate? (4%) (b) what is the advantage of this structure. (2%)
3. (a) For the logic diagram of the digital counter shown in Fig. 1, please write the truth table for  $Q_0, Q_1, Q_2$ , and  $Q_3$  (starting with 0000) after each pulse. If no connection is shown to a J or K input, then this terminal is understood to be high (a 1). (10%)  
 (b) If this system can be used as a N:1 counter, please evaluate the value of N. (4%)
4. In the circuit of Fig. 2,  $Q_1$  and  $Q_2$  are identical and have  $\beta_o = \beta_F = 200$  and  $V_A = \infty$ . (20%)  
 (a) Explain the function of current source  $I_{EE}$  with  $R_E$  in this circuit.  
 (b) The current source is realized by a simple current mirror. Design the mirror. Transistor used for the mirror have  $\beta_o = \beta_F = 200$ . Estimate the Early voltage.  
 (c) Evaluate  $A_{DM}, A_{CM}$ , and CMRR.  
 (d) determine  $R_{id}$  and  $R_{ic}$ .
5. (a) Draw a NOR-gate astable multivibrator and derive the period of the output voltage. (4%)  
 (b) Draw the circuit diagram of a  $V_{BE}$  multiplier and explain its operation. (4%)
6. (a) Draw the circuit model of a two-pole feedback amplifier and derive the gain-crossover frequency. What will happen if the magnitude of loop gain at the phase-crossover frequency is greater than unity ? (8%)  
 (b) For a single-loop feedback oscillator, what starts the oscillation and what determine the oscillation frequency. (4%)
7. The normalized magnitude of the Butterworth filter function is  $|H(j\omega)| = \frac{1}{\sqrt{1+(\frac{\omega}{\omega_c})^{2n}}}$ . A low-pass Butterworth filter is to be designed to have a 3-dB bandwidth of 100Hz and an attenuation of 60 dB at 350Hz. Determine the order of the Butterworth filter required. (10%)
8. Draw the architectures of (a) a 2-bit flash A/D converter (5%) and (b) a 3-bit R-2R D/A converter. (5%)

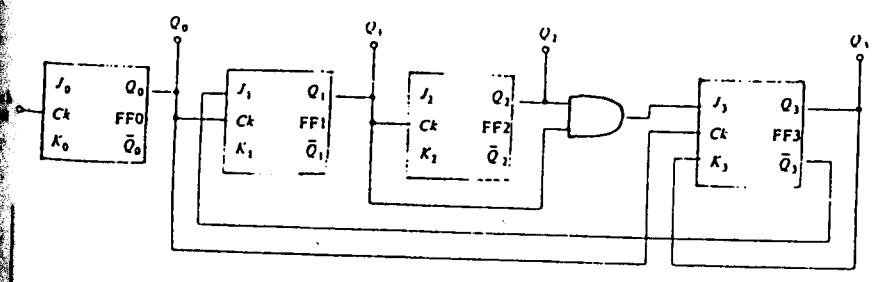


Fig. 1

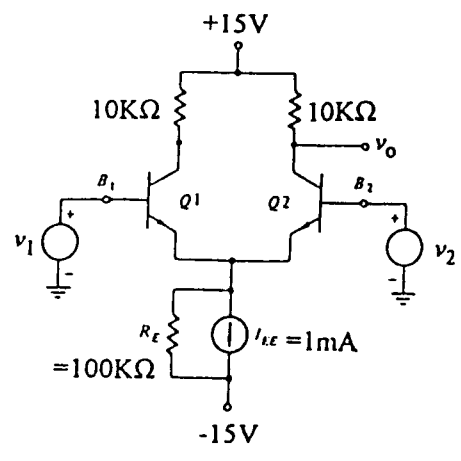


Fig. 2