

1. What is the position of the armature-reaction flux relative to the main-field flux for the following balanced-load conditions: (a) armature phase current is in phase with armature phase induced voltage; (b) armature phase current lags armature phase induced voltage; (c) armature phase current leads armature phase induced voltage? (15%)
2. A 30-kVA, 2.4-kV/0.6-kV transformer is connected as a step-up autotransformer from a 2.4 kV supply. Calculate the currents in each part of the transformer and the load rating. Neglect losses. (15%)
3. A 1000-kVA 4600-V three-phase 60-Hz Y-connected ac generator has a no-load voltage of 8350. The generator is operated at rated volt-amperes and 0.75 power factor lagging and rated voltage. Calculate
  - (a) the synchronous reactance (neglect armature resistance),
  - (b) the voltage regulation,
  - (c) the torque angle,
  - (d) the developed or air gap power, and
  - (e) the new voltage and kVA rating if the armature winding is connected in delta. (20%)

(背面仍有題目,請繼續作答)

4. 在任何線性、被動、對稱之四端網路中，對 ABCD 參數而言，請證

(a)  $AD - BC = 1$ . (8%)

(b)  $A = D$  (8%)


5. 在自載潮流 (power flow) 方程式求解中，一般設定了幾種型式之潮流排 (Bus type)，意義為何？ (5%)

(a) 求經濟調度中，用到 B 參數 (B loss coefficients)，其定義為何？ (5%)

6. 如下圖，求 (a) 正相序、負相序及零相序網路圖。 (16%)

(b) 若 F 發生單線接地故障，則故障電流多少？ (8%)

(以 10 MVA, 13.8 kV 為基準 (Base) 之標么表示)

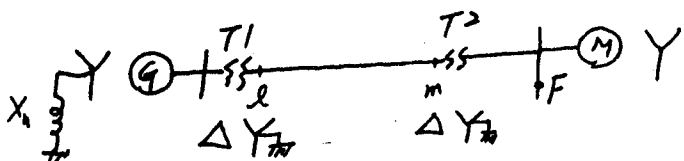

$X_n = 2 \Omega$

$G: 13.8 \text{ kV}, 50 \text{ MVA}, X_1 = X_2 = 0.25 \Omega, X_0 = 0.2 \Omega$

$T_1: 13.8 \text{ kV}/13.8 \text{ kV}, 25 \text{ MVA}, X_1 = X_2 = X_0 = 2.5 \Omega$

$T_2: 13.8 \text{ kV}/13.8 \text{ kV}, 10 \text{ MVA}, X_1 = X_2 = X_0 = 1.50 \Omega$

線  $l_m: X_1 = X_2 = X_0 = 200 \Omega$

$M: 13.8 \text{ kV}, 5 \text{ MVA}, X_1 = X_2 = 1.2 \Omega, X_0 = 0.4 \Omega$