
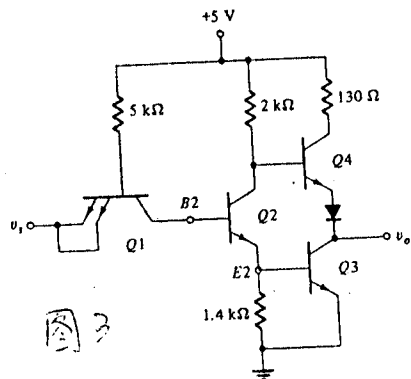
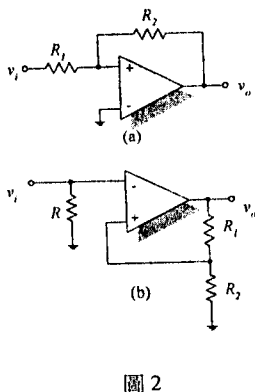


- 1. (a) A one-sided p⁺-n Si junction diode, if $N_D=1 \times 10^{16} \text{ cm}^{-3}$ and $N_A=1 \times 10^{18} \text{ cm}^{-3}$, please calculate the depletion region width of the diode with zero bias (assuming $n_i=1.45 \times 10^{10} \text{ cm}^{-3}$) (5%)
 (b) In a silicon crystal, which one is larger, μ_n or μ_p ? What are the factors that might influence the electron mobility μ_n and the hole mobility μ_p , why? (4%)
 (c) Please draw the small signal model of a bipolar junction transistor (3%), derive the transconductance $g_m = \frac{\Delta i_c}{\Delta v_{BE}} \Big|_{v_{CEQ}} = \frac{|I_{CQ}|}{\eta V_T}$ (3%)
 (d) Please state in your own words, what are the advantages of BJT and FET, respectively. (5%)
- 2. (a) 簡述射極隨偶器電壓增益小於 1 之原因。(3%)
 (b) 頻率補償之主要目的為何?(3%)
 (c) 試簡述振盪器之工作原理。振盪條件為何? 如何決定振盪頻率?(4%)
- 3. (a) 試推導圖 1 所示電路之電壓增益 $A_v(=v_o/v_i)$ 。設兩電晶体之輸出電阻均為 r_o 。(5%)
 (b) 試繪出圖 2 所示(a)、(b)兩電路之移轉特性曲線。於電路應用上何者較佳? 簡述其原因。(5%)
- 4. A TTL gate circuit is shown in Fig. 3, Both of the inputs are tied together. The transistors are identical and have $\beta_R=0.5$
 (a) Determine $\beta_{F(min)}$ for proper operation. Assume that Q2 and Q3 saturate for $v_s=V(1)$. (12%)
 (b) What is the fan-out? (8%)

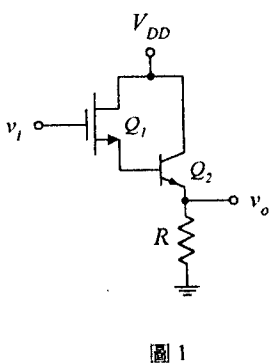

(背面仍有題目,請繼續作答)

5. An amplifier circuit is shown in Fig. 4, NPN transistors are identical. PNP transistors are identical. All transistors operate in the active region. Base current can be ignored. $V_{BE}=0.7V$, Early voltage $V_A=100V$, thermal voltage $V_T=kT/q=25mV$. Calculate (a) $I_1=?$ (3%), (b) $I_2=?$ (3%), (c) output resistance $R_o=?$ (3%) (d) low frequency gain $v_{out}/v_{in}=?$ (3%)

6. For a two stage OPAMP, explain (a) Miller compensation. (3%) (b) slew rate. (3%)

7. A single-pole amplifier as shown in Fig. 5(a) is assigned to have a low-frequency gain of 100 and a pole at $10^5 Hz$ (i.e. $2\pi \times 10^5 rad/sec$). The single-pole amplifier (transfer function= $A(S)$) is used to design a feedback amplifier (transfer function= $A_F(S)$) as shown in Fig. 5(b). (a) Derive $A(S)$ and draw its Bode plot. (3%) (b) What's the feedback type of the internal stage of the feedback amplifier? β for the internal stage =? (3%) (c) Derive $A_F(S)$ and draw its Bode plot. (3%) (d) If the gain of the single-pole amplifier is decreased by 20%, what is the corresponding gain decrease in the feedback amplifier? (3%)

8. (a) For a Butterworth filter that meets the following low-pass specifications: $f_p=3KHz$, 20dB attenuation at $f_s=6KHz$, calculate $N=?$ (5%)

(N_{th} order Butterworth transmission: $\left| \frac{H(f)}{H_o} \right|^2 = \frac{1}{1+(f/f_p)^{2N}}$)

(b) Draw the circuit diagram of an universal biquad filter and show how lowpass can be achieved (5%)

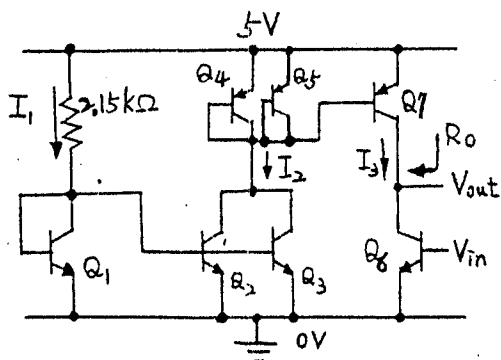


圖 4

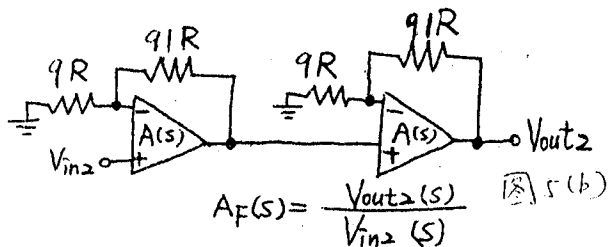
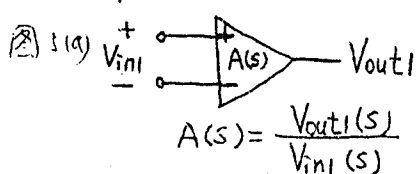


圖 5 (b)