
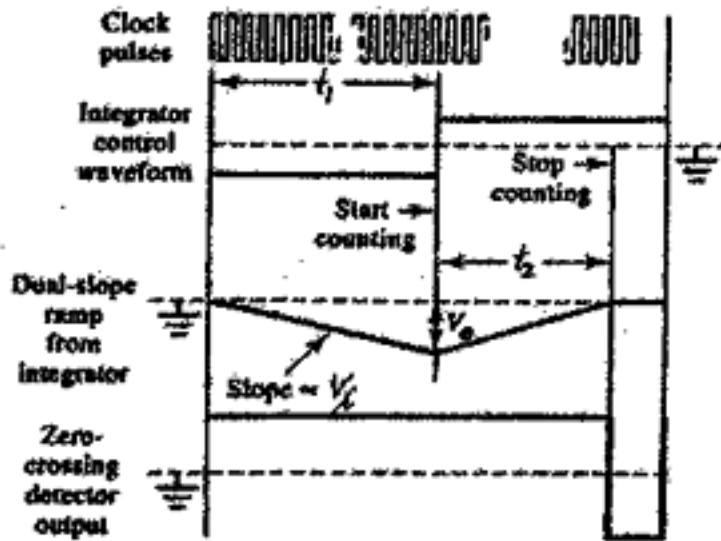


- (15%) Explain the operation of a dual-slope-integrator analog-to-digital converter (ADC)? What are the quantizing error and the resolution of a 16-bit ADC?
- (20%) Briefly explain the following terms: (1) Flash memory, (2) Cache RAM, (3) RS232C, (4) IEEE488/GPIB, (5) Handshaking.
- (10%) Using a 4.5 V battery together with a meter that has 100 μ A FSD and a coil resistance of 100 Ω , design a series ohmmeter to have a range of 1 k Ω (0.9FSD) to 100 k Ω (0.1FSD).

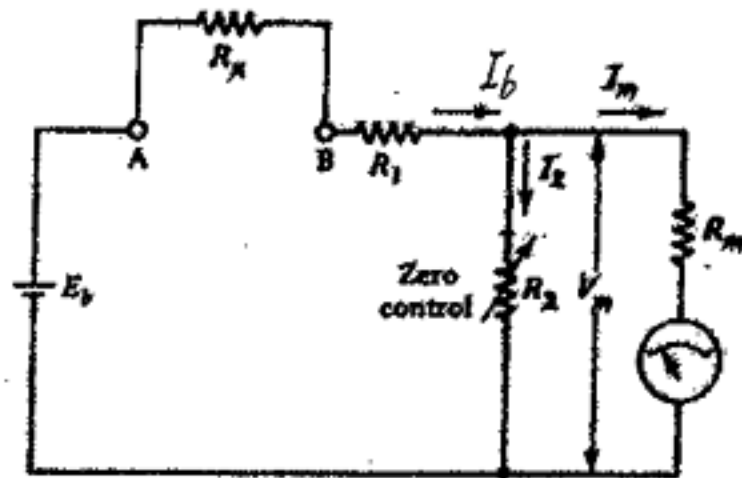


System waveforms of the dual-slope-integrator ADC (problem 1)




Series ohmmeter (problem 3)

- (15%) Find the series-equivalent inductance and resistance of the network (coil) that causes a bridge (as shown below) to null with the following component values: $\omega=3000$ rad/s, $R_2=10$ k Ω , $R_1=2$ k Ω , $R_3=1$ k Ω , $C_1=1$ μ F. Also, determine the Q factor of the coil
- (15%) Determine the dimensions of *magnetic flux* (ϕ), *inductance* (L), *resistance* (R), and *capacitance* (C). Using the results to show that the product of R and C has a time unit.
- (10%) Sketch half-wave rectifier ac electronic voltmeters using (a) a voltage follower and (b) a precision rectifier. Explain the operation of each circuit, and compare their performance.
- (15%) A 10:1 oscilloscope probe, as shown below, is used with an oscilloscope with $R_i = 1$ M Ω and $C_i = 40$ pF. If the probe uses a 9 M Ω series resistor and the coaxial cable has a capacitance of 80 pF, determine the value of capacitor C_1 that should be connected in parallel with the 9 M Ω resistor. Also calculate the signal frequency at which this probe will produce a 3 dB reduction in signal from a 1 k Ω source.

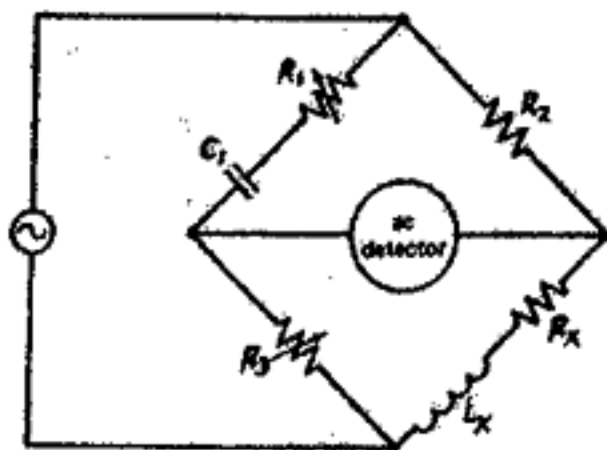

A bridge (problem 4)

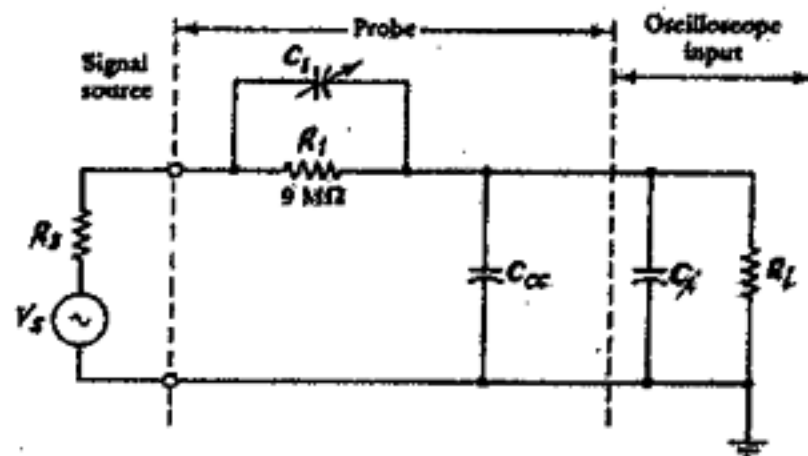

Circuit of 10:1 probe (problem 7)