

1. Use Δ -to-Y transformation to solve the phasor current I_A in Fig. 1. (15%)

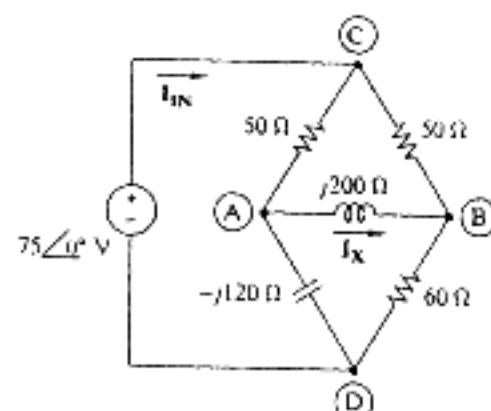


Fig. 1

2. Find I_A , I_B , V_1 , V_2 , and the impedance Z_{IN} seen by the source circuit in Fig. 2. (10 %)

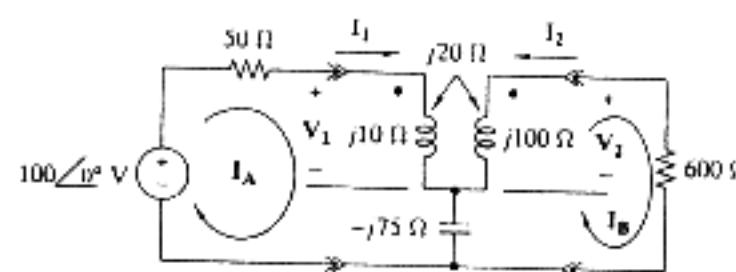


Fig. 2

3. (a) Use convolution to find the output of the circuit in Fig. 3 when the input is $v_1(t) = tu(t)$. (5%)
 (b) Use s-domain analysis to find the circuit output for the same input. (5%)

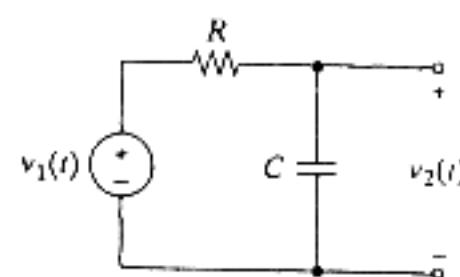


Fig. 3

4. A Δ -connected load with $Z=40+j30\Omega/\text{phase}$ is driven by a balanced, positive sequence three-phase generator with $V_L = 2400\text{ V}$ (rms). By using V_{AN} as the phase reference,

- (a) Find the phase currents. (5%)
 (b) Find the line current. (5%)
 (c) Find the average and reactive power delivered to the load. (5%)

(背面仍有題目，請繼續作答)

5. Please compute the power delivered by the dependent current source ($1.6V_a$) of Fig. 4. (15 %)

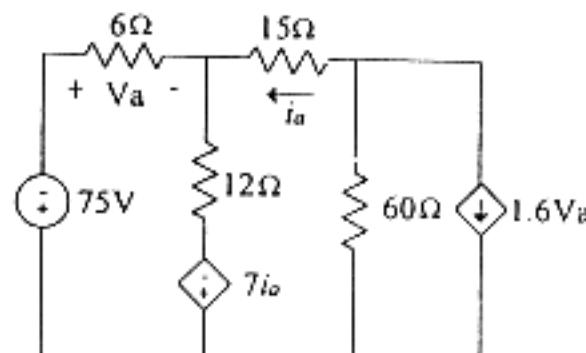


Fig. 4

6. Please find the voltage across the 40Ω resistor in Fig. 5. (15 %)

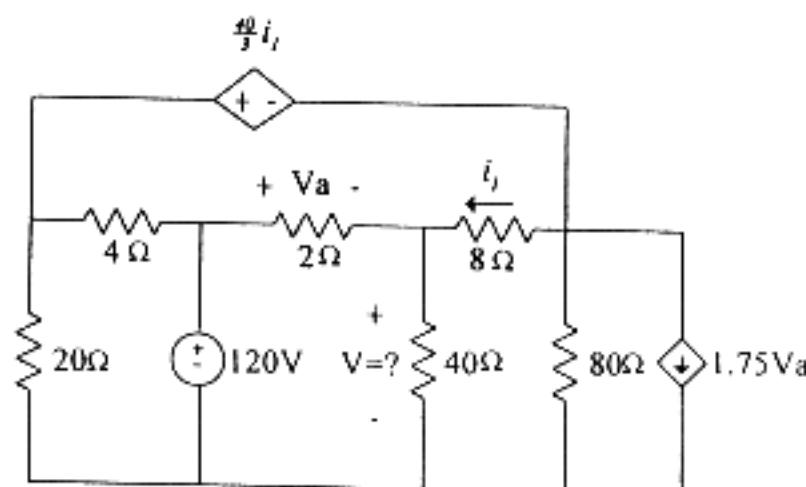


Fig. 5

7. In Fig. 6, please find the value of the resistor R_1 that is adjusted to consume the maximum power. (20 %)

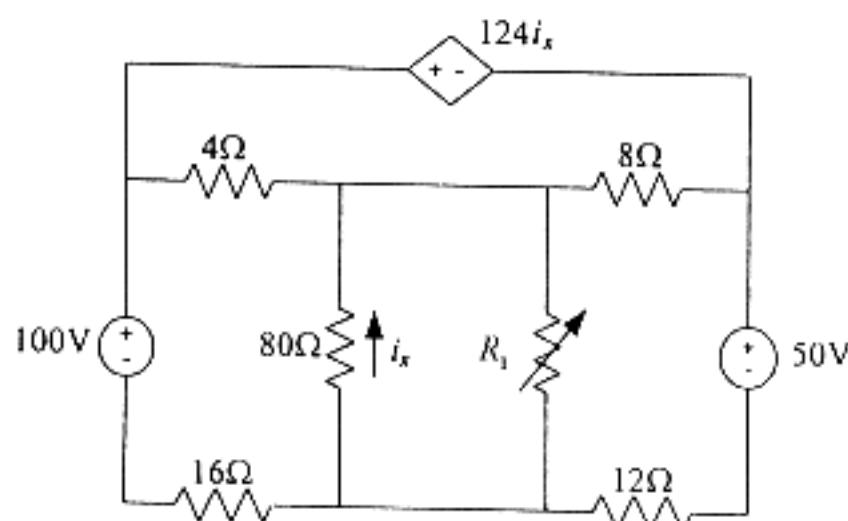


Fig. 6