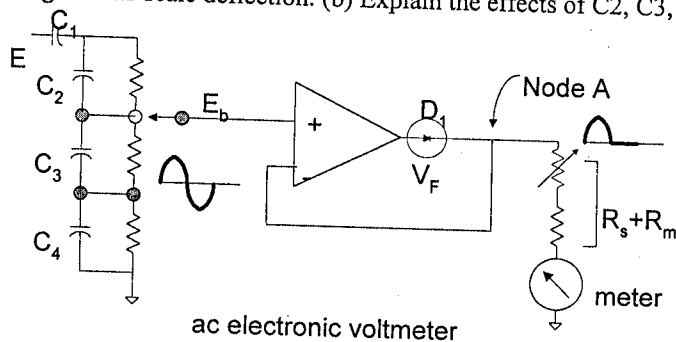


1. (20%) The half-wave rectifier electronic voltmeter in the figure shown below uses a 0.5 mA deflection meter with a 460Ω coil resistance. (a) If $R_s = 450 \Omega$, calculate the rms input voltage (i.e. E_b) required to give half-scale deflection. (b) Explain the effects of C_2 , C_3 , and C_4 . How if we place D_1 after node A?



2. (15%) Using a 4.5 V battery together with a PMMC meter that has $100 \mu A$ FSD and a coil resistance of 100Ω , design a series ohmmeter to have a range of $1 k\Omega$ to $100 k\Omega$.
3. (15%) Briefly explain the following terms: (1) Instrumentation Amplifier (2) Lock-in Amplifier (3) Chopper Amplifier (4) Isolation Amplifier (5) Linear Variable Differential Transformer (LVDT).
4. (15%) The parameters in a Wheatstone Bridge are: $P=4K\Omega$, $Q=1K\Omega$, $S=2K\Omega$, $E=10V$, minimum adjustable $\Delta S=\pm 0.2\Omega$, $R_m=1K\Omega$, and $I_G(\min)=0.5 \mu A$. Find the value of R when balance (5%) and the resolution of the Wheatstone bridge (10%).
5. (15%) To measure the inductance of an inductor, there are two bridges: Maxwell and Hay bridges. Describe these two bridges (10%) and find their differences (5%).
6. (10%) A low-capacitance probe contains a parallel RC circuit. Explain why it can expand the measurable frequency range. Assume a measured source E with R_s (source resistance) $=600\Omega$, $R=9M\Omega$ and $C=13pF$ for the low-capacitance probe, R_{in} (input resistance of an oscilloscope) $=1 M\Omega$, C_t (total capacitance shunt with R_{in}) $=120 pF$.
7. (10%) In IEEE-488 interface, describe the role of controller, listener, and talker.

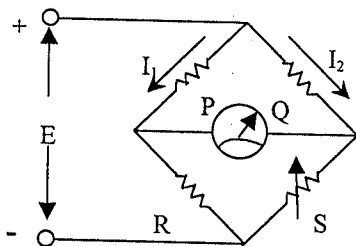


Figure for Problem 4