

- (10%) Explain the terminologies: accuracy, precision, resolution, reliability and repeatability.
- (20%) A cable is about 10 Km in length, and there is a ground fault shown in **Figure A**. The cable resistance is $10\ \Omega$ per 1 Km. The data measured by Varley loop are: $P = 4\ \text{k}\Omega$, $Q = 2\ \text{k}\Omega$, $S = 200\ \Omega$ when switch at point a; $S = 180\ \Omega$ when switch at point b. Find the location of ground fault.
- (20%) The parameters in a Wheatstone bridge are: $P=2\ \text{k}\Omega$, $Q=1\ \text{k}\Omega$, $S=4\ \text{k}\Omega$, $E=12\text{V}$, minimum adjustable $\angle S = \pm 0.1\ \Omega$, $R_m = 1\ \text{k}\Omega$, and $I_G(\text{min}) = 0.1\ \mu\text{A}$. Find the value of R and the sensitivity or resolution of the Wheatstone bridge in **Figure B**.

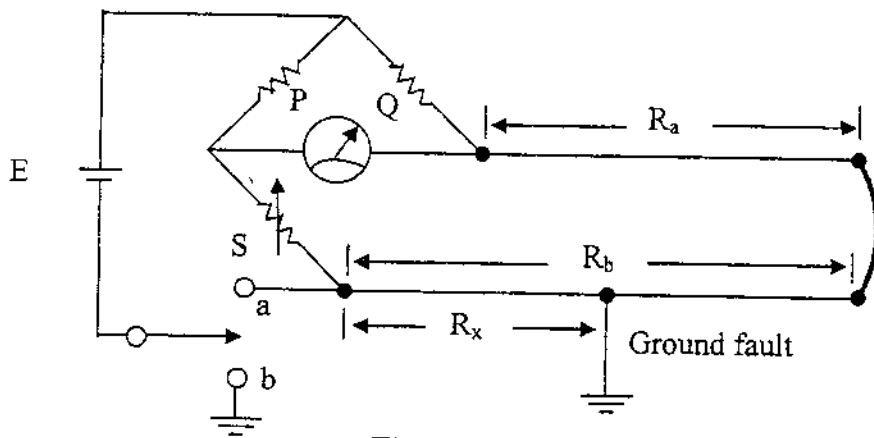


Figure A

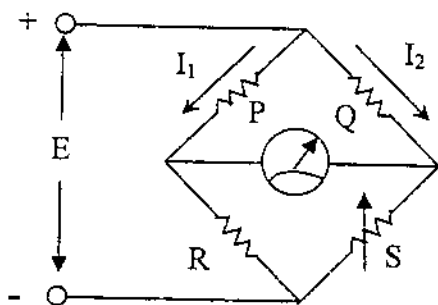


Figure B

(背面仍有題目,請繼續作答)

4. (20%) (a) Define the Q factor for an inductor. Write the equations for inductor Q factor with RL series and parallel equivalent circuits. (b) Define the D factor for a capacitor. Write the equations for capacitor D factor with RC series and parallel equivalent circuits. (c) Explain the physical meaning of Q and D factors.
5. (15%) Sketch a typical ohmmeter (Figure C) scale, explain why the scale is nonlinear, and explain which part of the scale gives the most accurate resistance measurement. (Hint: Assume that the PMMC meter has a 1% accuracy, $I_{FSD} = 100 \mu A$, and $E_b = 1.5 V$, find the accuracy when the pointer is at 0.2FSD, 0.5FSD, and 0.8FSD. Assuming that ohmmeter uses precision internal resistors)

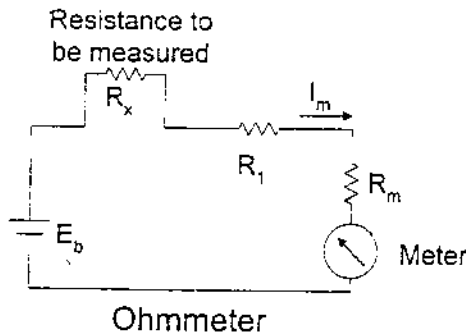


Figure C.

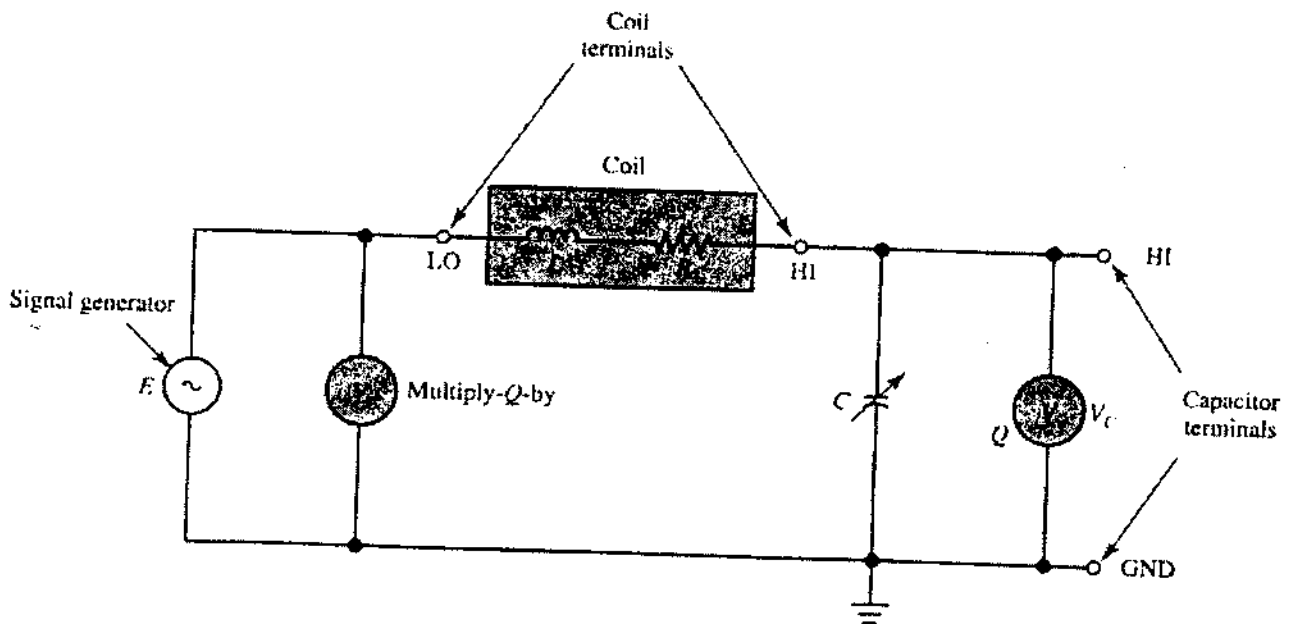


Figure D. A basic Q meter circuit.

6. (15%) With the signal generator frequency of a Q meter (Figure D) set to 1.25 MHz, the Q of a coil is measured as 98 when $C = 147 pF$. Determine the coil inductance (L) and resistance (R).