

1. In the circuit of Figure 1, the maximum power that a resistive load can absorb from the circuit is P_{AC} if the load is connected between nodes A and C, while the maximum power that a resistive load can absorb from the circuit is P_{BD} if the load is connected between nodes B and D. Please compute the value of $P_{AC} - P_{BD}$ (20 %)

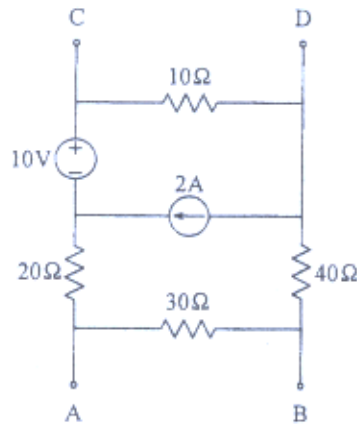


Figure 1

2. After having been closed for a long time, the switches of Figure 2 are opened simultaneously at $t=0$. Find the voltage $v_1(t)$ across $1\mu F$ capacitor for $t \geq 0$. (15 %)

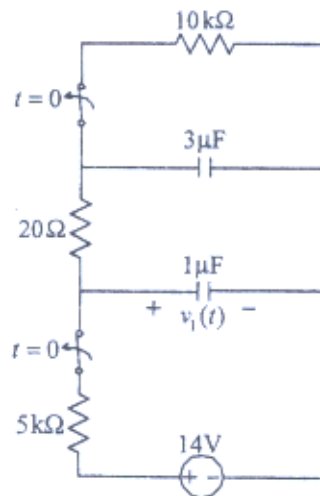


Figure 2

3. In Figure 3, at the time when the R_I is adjusted to be the value for the maximum power transfer, please calculate the power delivered from the 280V source. (15 %)

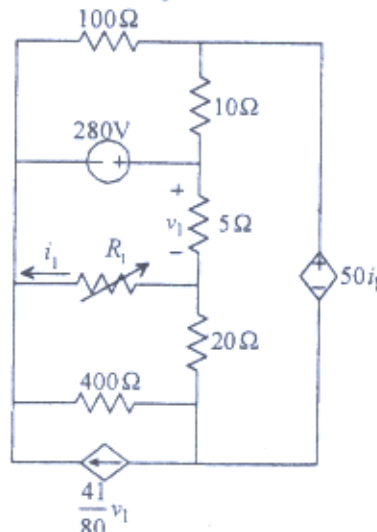


Figure 3

(背面仍有題目,請繼續作答)

4. The load on the linear transformer shown in the following circuit is a capacitance of value C_2 . The voltage V_1 is supplied by a voltage source.


(a) Calculate the transfer function V_2/V_1 . (5%)

(b) Define $\omega_0 = 1/\sqrt{L_2 C_2} = 1/\sqrt{L_1 C_1}$, $Q_1 = \omega_0 L_1 / R_1$, $Q_2 = \omega L_2 / R_2$ and


$k = M / \sqrt{L_1 L_2}$. Write the transfer function in a form that does not contain M , L_1 , L_2 , or C_1 . (10%)

(c) Define k_c to be the value of k for which $|V_2/V_1|$ is a maximum at $\omega = \omega_0$.

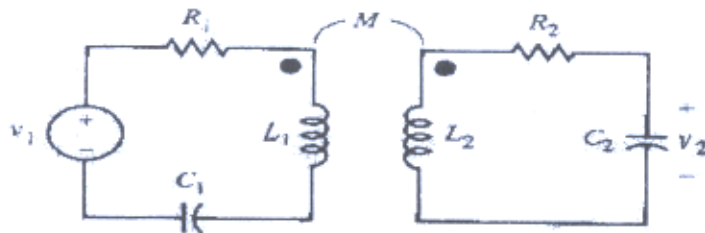Develop an expression for k_c in terms of Q_1 and Q_2 . (5%)



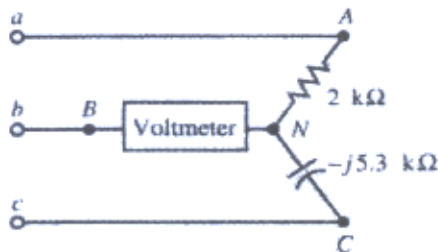5. The following circuit can be used to check for the phase sequence of a balanced three-phase voltage. Assume that the voltmeter is ideal (draws no current) and indicates rms values and that the line-to-line voltage is 208 V. Find the voltmeter reading for an abc phase sequence and an acb phase sequence. In practice, the voltmeter is often replaced by a small neon lamp and series resistance. The brightness of the lamp is used to indicate the phase sequence. (15%)



6. For following figure, $V_{an} = 120V \angle 0^\circ$. Compute the readings of each wattmeter and determine the total power of this system. (15%)

