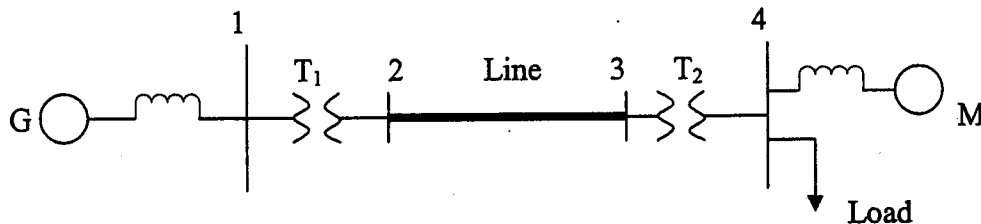


1. Answer all questions in your answer sheet.

- Define the term 'bolted fault'. (3%)
- State the conditions of an electric power system for which the augmented  $Y_{bus}$  matrix (i.e. the indefinite  $Y_{bus}$  matrix) is singular. (3%)
- Which common model is used for most load buses in a power flow study (choose the best answer): (A) PQ bus (B) PV bus (C) Swing bus (D) TCUL bus. (3%)
- Define the 'frequency sensitive load' and make an example of this kind in your real life. (3%)

2. The one-line diagram of a three-phase power system is depicted below.



The nameplate ratings for the power equipment are given as follow:

Generator G:	90MVA	11kV	X=15%
Transformer $T_1$ :	100MVA	11 $\Delta$ /121Y kV	X=10%
Transformer $T_2$ :	90MVA	138Y/69 $\Delta$ kV	X=15%

Transmission Line:  $j15\Omega$

Operating condition:

Motor M:	50MVA	60kV	X=15%	0.8 power factor lagging
Load:	30MVA	60kV	0.65 power factor lagging	

Select a common base of 100MVA and 121kV

- Draw an impedance diagram and label all impedances including Generator, Motor, and Load in per unit. (8%)
- Take bus 4 voltage as reference, determine the Motor current, and Load current in actual unit kA. (6%)
- Determine the internal emfs in kV for the Generator and Motor. (6%)
- A capacitor of negligible resistance is connected in parallel with Load to improve the power factor to 0.8 lagging. Determine the capacitance in  $\mu F$  for the capacitor. (4%)


(背面仍有題目,請繼續作答)

3. An engineering process has inputs  $x = (x_1, x_2)^T$  and outputs  $y = (y_1, y_2)^T$  and is modeled by the function

$$y_1 = f_1(x_1, x_2) = 0.1x_1x_2 + x_1^2 + 5.5$$
$$y_2 = f_2(x_1, x_2) = x_2^2 - 0.1x_1x_2$$

- A. Find the best linear approximation to the process about the operating point  $(x_1, x_2) = (1, 2)$ . (6%)
- B. Define  $(\Delta x_1, \Delta x_2) = (x_1 - 1, x_2 - 2)$  and  $(\Delta y_1, \Delta y_2) = (y_1 - f_1(1, 2), y_2 - f_2(1, 2))$ . From the linear approximation you find in (A), derive the relationship between  $(\Delta x_1, \Delta x_2)$  and  $(\Delta y_1, \Delta y_2)$  using the linear model (i.e. write the relationship using the Jacobian matrix). (4%)
- C. What do the entries in the Jacobian tell you about controlling the output of the process with the input near  $(x_1, x_2) = (1, 2)$ ? (4%)

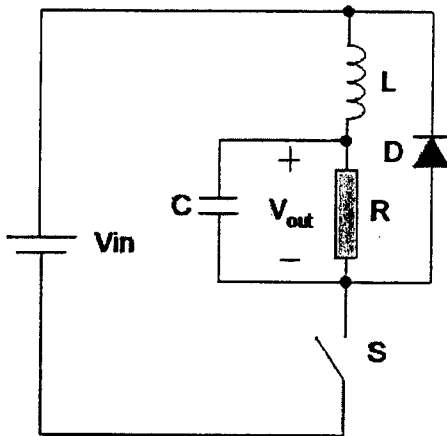4. Derive the DC voltage ratio,  $V_{out}/V_{in}$ , of the CCM DC-DC converter, as shown below. (10%) Plot the current and voltage waveforms of the inductor L. (10%)



5. A 200-kVA, 13,200V/2,200V, 60Hz, single-phase transformer has the following test data:

	Volts	Amps	Watts	Frequency	Volts
<b>Open Circuit</b>	2,200	3.1	1550	60	12,800
<b>Short Circuit</b>	210	90.9	2500	60	

Determine the parameters of the T-equivalent circuit when referred to the low voltage winding. (20%)

(背面仍有題目,請繼續作答)

6. A circuit, as shown below, is a typical layout which might be encountered in a micro-processor instrumentation system. The wire used in the connection between the transformer and the switching power supply is #14 gauge with a resistance of 2.5 ohms/1000ft measured at 60 Hz. The distance between the source voltage (97~132 VAC) and the transformer is negligible.

The following data applies:

$V_{in}$  is between 97 and 132 volts AC at 60Hz.

$I_1=5.0$  amps  $I_2=0.5$  amps  $I_3=0.5$  amps

Switching power supply efficiency = 75%

Minimum input voltage to switching power supply is 15VAC

Transformer turns ratio can vary by  $\pm 5\%$ .

Calculate the maximum distance  $D$  between the transformer and the switching power supply. (10%)

