

本試題是否可以使用計算機：  可使用，  不可使用 (請命題老師勾選)

1. The network N in Fig. 1(a) contains only R's, L's, and C's and has the following z-parameters.

$$Z_{11} = \frac{4s + 15}{2s + 3} \qquad Z_{12} = \frac{9}{2s + 3}$$

Prior to  $t=0$ , N is in the zero-energy state. It is excited as shown in Fig. 1(b) with the terminal C, D open-circuited.

(a) Determine the transfer function  $A(s)$  where  $v_2 = A(s)v_3$ . (10%)

(b) Find  $v_2(t)$  for  $t > 0$ , if  $v_2(0+) = 0$ . (10%)

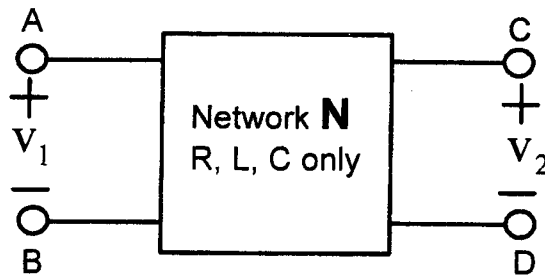


Fig. 1(a)

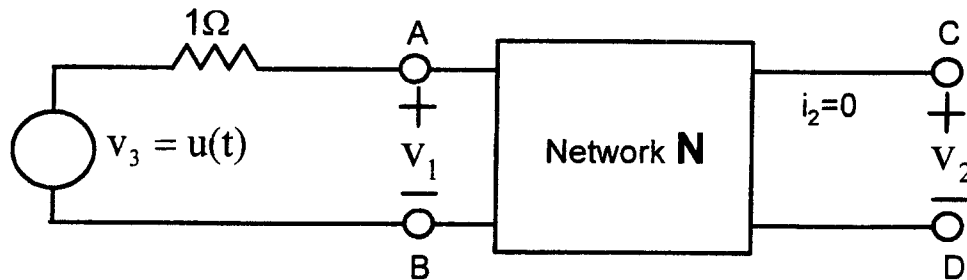


Fig. 1(b)

2. Determine the input admittance  $Y(s)$  for the circuit in Fig. 2. (10%)

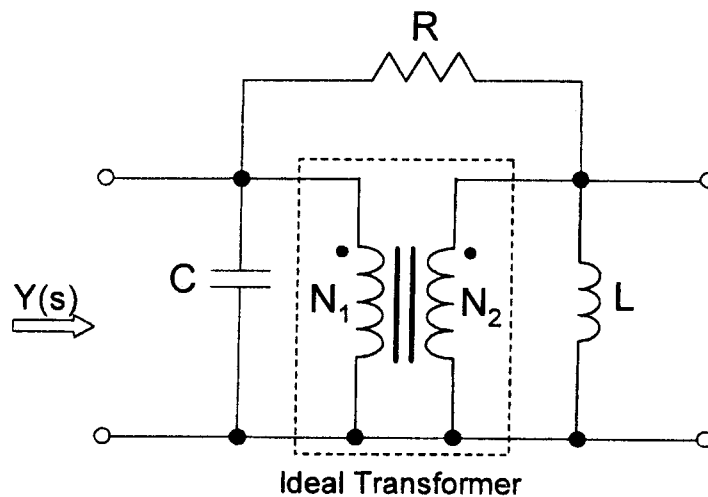


Fig. 2

(背面仍有題目,請繼續作答)

本試題是否可以使用計算機： 可使用， 不可使用（請命題老師勾選）

3. Derive the following transfer functions for the circuit shown in Fig. 3.

(a)  $V_S/I_S$  (10%)

(b)  $V_{OUT}/I_O$  (10%)

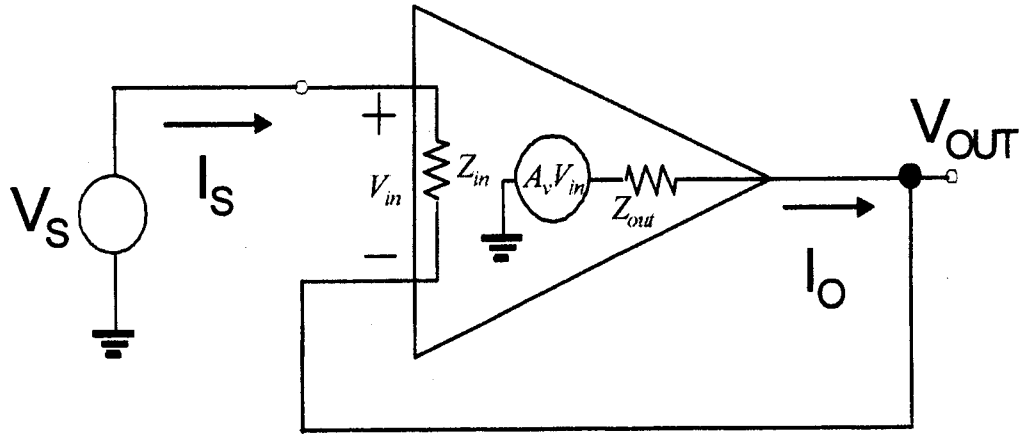


Fig. 3

4. Use mesh analysis to decide  $i_1$ ,  $i_2$ , and  $i_3$  in Fig. 4, where  $V_1 = 3V$ ;  $A_1 = 4A$ ;  $R_1 = 2\Omega$ ;  $R_2 = 1\Omega$ ;  $R_3 = 4\Omega$ ;  $R_4 = 1\Omega$ ;  $R_5 = 1\Omega$ ; (a) Formulate mesh analysis in

matrix form, i.e.,  $M \times \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} y_1 \\ y_2 \\ y_3 \end{bmatrix}$ , where  $y_1, y_2, y_3$  and all entries of matrix  $M$

must be scalar. (b) Solve the equations and obtain  $i_1$ ,  $i_2$ , and  $i_3$ . (20%)

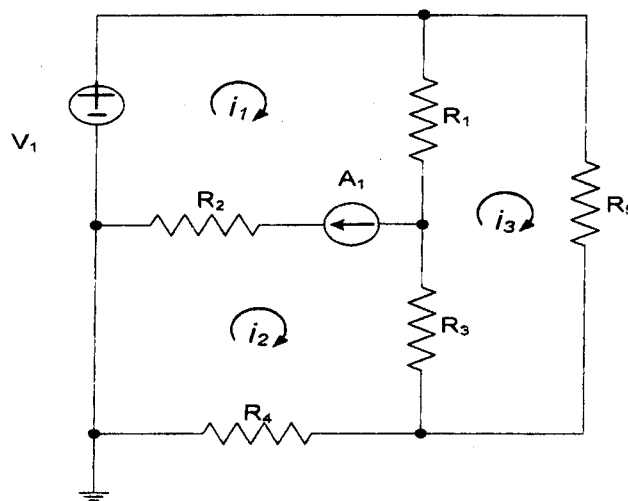


Fig. 4

本試題是否可以使用計算機： 可使用， 不可使用（請命題老師勾選）

5. Given the circuit as shown in Fig. 5 whose  $R_1 = 10\text{k}\Omega$ ;  $R_2 = 40\text{k}\Omega$ ;  $R_3 = 20\text{k}\Omega$ ;  $R_4 = 10\text{k}\Omega$ ;  $R_5 = 10\text{k}\Omega$ . Determine (a) the closed-loop gain  $v_{out}/v_S$ ; (b) find  $i_{out}$  when  $v_S = 0.5\text{V}$ . Assuming the operational amplifier is ideal. (15%)

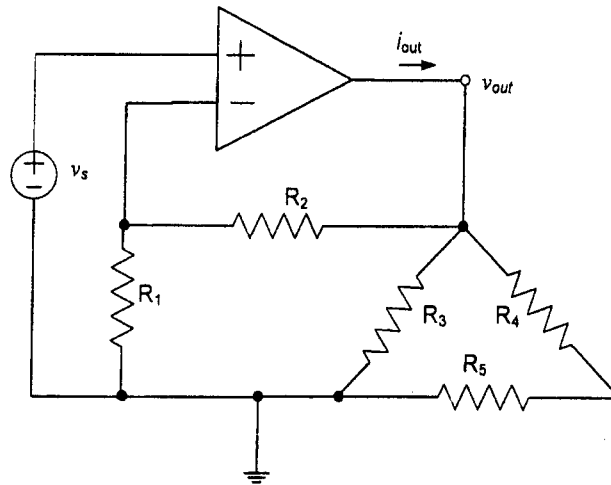


Fig. 5

(背面仍有題目,請繼續作答)

本試題是否可以使用計算機： 可使用， 不可使用（請命題老師勾選）

6. Given the input voltage as shown in Fig. 6-1, derive the output voltage ( $v_{out}$ ) in term of  $v_{in}$ ,  $R_1$  and  $C_1$ . Then sketch  $v_{out}$  of the circuit in Fig. 6-2 when  $C_1 = 0.1 \mu\text{F}$  and  $R_1 = 10\text{k}\Omega$ . (15%)

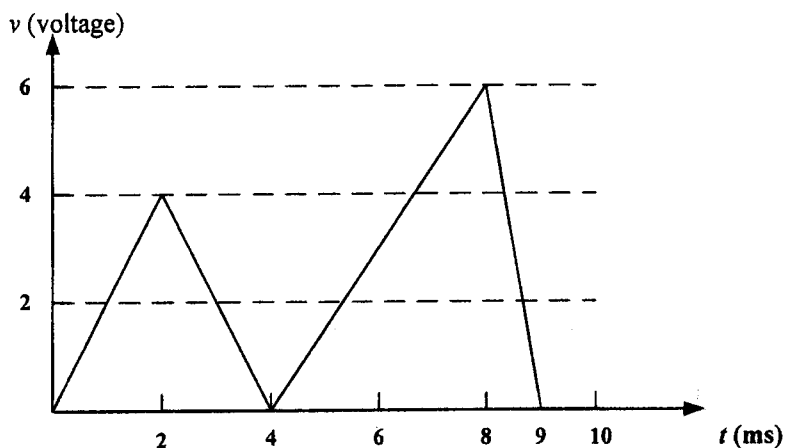


Fig. 6-1

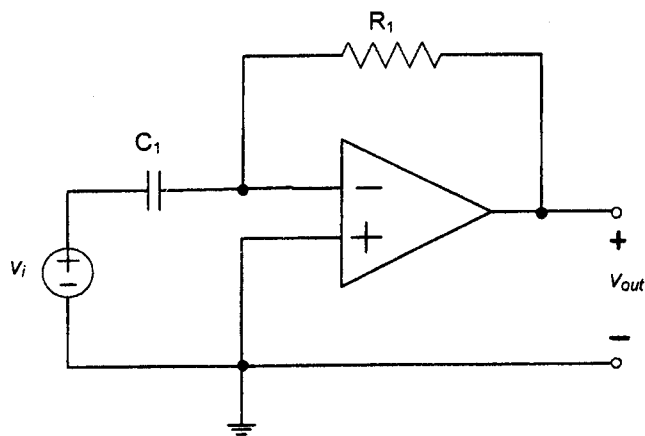


Fig. 6-2