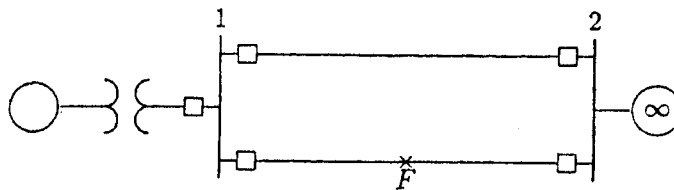


本試題是否可以使用計算機：可使用，不可使用（請命題老師勾選）

考試日期：0301，節次：2

1. (20%) One 60 Hz machine system connected to infinite bus is shown below. Assume the input mechanical power  $P_m$  is constant, the generator is delivering power steadily with a power angle  $\delta_0$ . Consider a temporary three-phase bolted fault occurs at point  $F$  where  $F$  is at some distance away from the sending end. The fault is then cleared at power angle  $\delta_C$  by removing the faulty line. Due to the energy conversion, the power angle reaches  $\delta_{max}$  at the stable operating region. The power angle finally returns to a new stable operating point at  $\delta_1$ .



Please answer the following:

- I. (15%) Draw the power angle curves (electric power  $P_e$  vs. power angle  $\delta$ ), and power line  $P_m$ . Label the operating points associated with  $\delta_0$ ,  $\delta_C$ ,  $\delta_{max}$ ,  $\delta_1$  on the curves.
  - II. (5%) Mark and discuss the areas for the stability criteria.
2. (20%) With the same 60Hz power system structure in the previous question, assume the generator has inertia constant  $H=5\text{MJ/MVA}$ , a direct transient reactance  $X_d'=0.3$  pu is connected to a transformer with reactance  $X_t = 0.1$ pu. Between the transformer and infinite bus, a pair of transmission lines (each line's reactance is 0.6pu) are delivering real power  $P_e = 0.8$ pu and  $Q = 0.08$ pu to the infinite bus at a voltage of  $V = 1$ pu.
- I. (10%) Consider the first-order differential equation

$$\frac{dx}{dt} = f(x)$$

Express the solution  $x(t)$  by using Euler's method and point out its flaw

- II. (10%) A sudden line trip occurs on one of the transmission line and the faulty line is removed immediately at  $t = 0$  second. Please find the power angle  $\delta$  in degree and rotor speed deviation  $\Delta\omega$  in rad/sec after the fault at  $t = 0.02$  second. Using the Euler method with a step size of  $\Delta t = 0.01$  second. Perform two iterations.

swing equation: 
$$\frac{d^2\delta}{dt^2} = \frac{\pi f_0}{H} (P_m - P_{max} \sin\delta)$$

(背面仍有題目,請繼續作答)


3. (20%) The following data were obtained for a 20kVA, 60Hz, 2kV: 200V distribution transformer tested at 60Hz:

With high-voltage winding open-circuited 240V 1A 120Watts

With low-voltage terminals short-circuited 50V 8A 280Watts

- a) (10%) Compute the efficiency at full-load current and the rated terminal voltage at 0.8 lagging power factor.
- b) (10%) Assume that the load power factor is varied while the load current and secondary terminal voltage are held constant. Use a phasor diagram to determine the load power factor for which the regulation is greatest. What is this regulation?
4. (20%) As following figure,  $V_{in}=10V$ ,  $L=1mH$ ,  $R=500\Omega$ , the switching frequency is 100kHz and duty cycle of S is 50%.

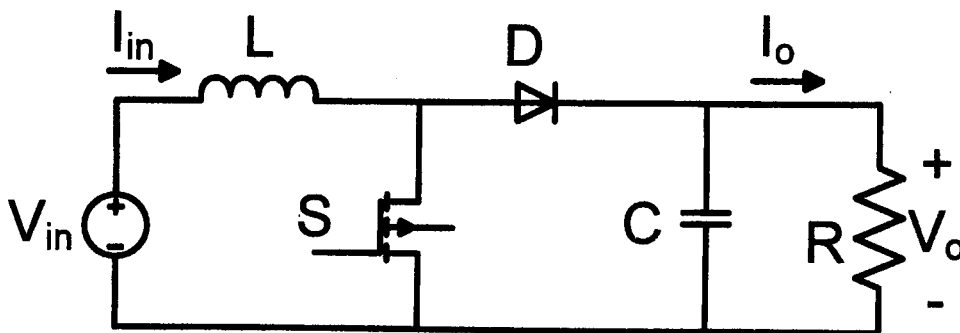- a) (10%) Is this converter operating in continuous mode or discontinuous mode? And why?
- b) (10%) What is the output voltage  $V_o$  and the average input current  $I_{in}$ ?



5. (20%) Short Answer

- a) (7%) What are the differences between ZCS (zero current switching) and ZVS (zero voltage switching)?
- b) (7%) What are the advantages of the double-squirrel-cage rotors?
- c) (6%) How to obtain the reverse rotation of the single-phase induction motors?