

※ 考生請注意：本試題 可 不可 使用計算機

1. (9%) (a) Describe and explain the measurement factors of **precision, accuracy, and resolution.**  
 (6%) (b) A meter reads **28.00 with  $\pm 2\%$  error**, find the possible range of real data.  
 (5%) (c) Describe and explain the relationship between **resolution and sweep time in spectrum analyzer.**
2. (12%) (a) A Hay bridge is shown in **Fig. 1**. Please derive the equations of **Q** and express **L1** and **R4** in terms of **Q**.  
 (6%) (b) Now, a **Hay bridge** has a **0.003  $\mu\text{F}$**  standard capacitor for **C1**, **R2 = 10 k $\Omega$** , and **R3 = 6 k $\Omega$** . Balance is achieved with a **2 kHz** supply frequency when **R1 = 0.1 k $\Omega$** . Calculate the value of **L1** and **R4** and its **Q**.

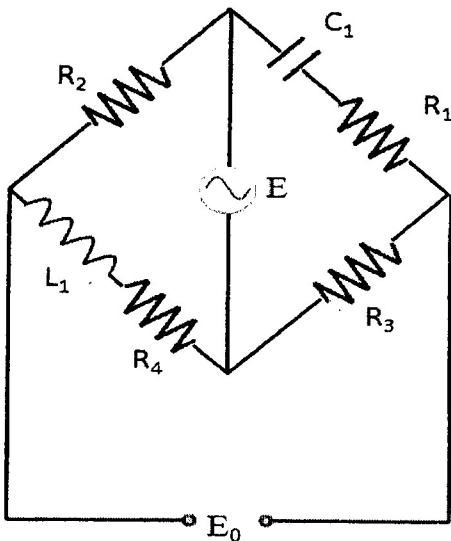


Fig. 1


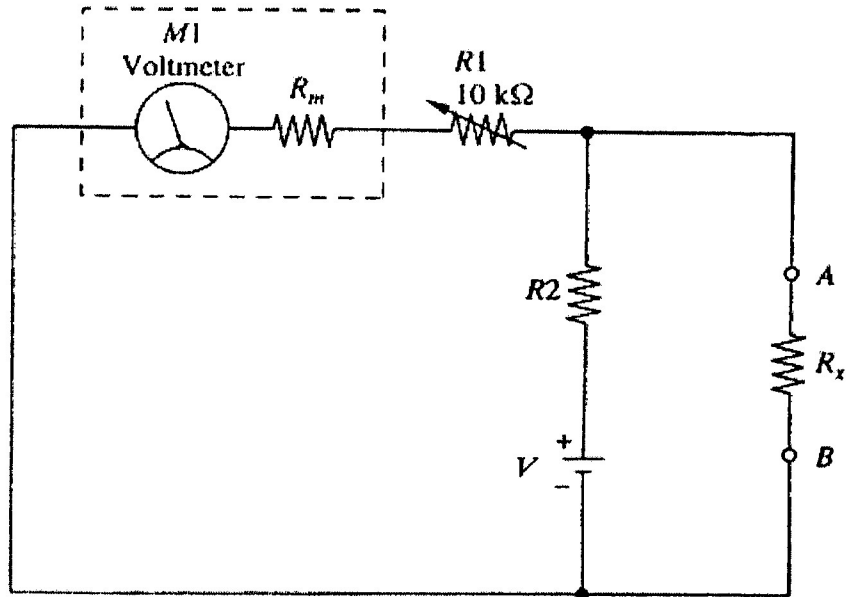


Fig. 2

3. (12%) A series-parallel ohmmeter circuit is shown in **Fig. 2**. There are three resistors in the circuit: **Rm** is the internal resistor of the voltmeter, **R1** is the zero-control resistance, **R2** is a resistance in series with the battery, and **Rx** is the unknown resistor. The value **E** is the voltmeter reading value when nodes **A** and **B** are opened and the value **e** is the voltmeter reading value when the **Rx** is connected across nodes **A** and **B**. The **Rx** connects to nodes **A** and **B** when we are measuring. Please calculate the formula of the **Rx** using **R1, R2, Rm, E**, and **e**.
4. (24%) A digital frequency meter (**Fig. 3**) uses a time base consisting of a **1 MHz** clock generator frequency divided by six decade counters. Determine the meter indication (a) when input frequency is **5 kHz** and the time base output is selected at the sixth decade counter and (b) when the input frequency is **2.9 kHz** and the time base output is selected at the fifth decade counter. (c) Rearrange the frequency meter for **reciprocal counting**. Determine the **error** that can occur when a **30 Hz** frequency is measured on this system.


(背面仍有題目,請繼續作答)

※ 考生請注意：本試題  可  不可 使用計算機

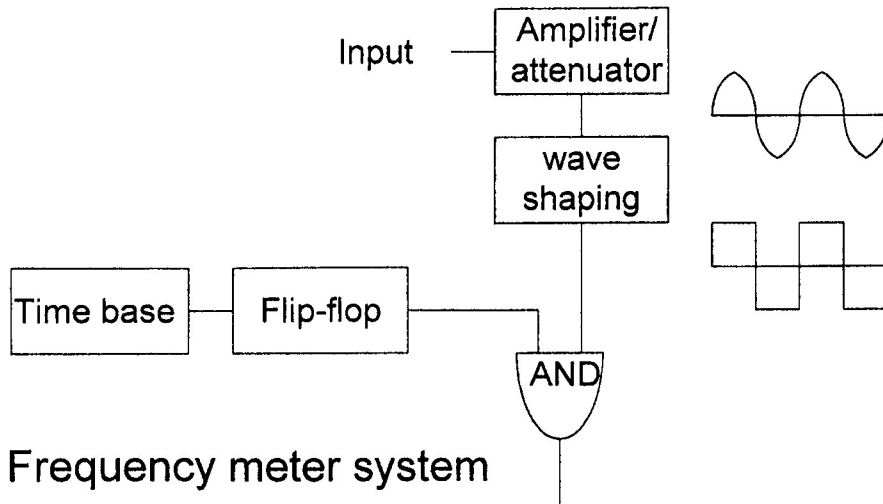

(Fig. 3)

5. (10%) Describe the operation theory of auto balancing bridge that shown below (Fig. 4). (Assume the resistance of the unknwn DUT is  $R_x$ .)

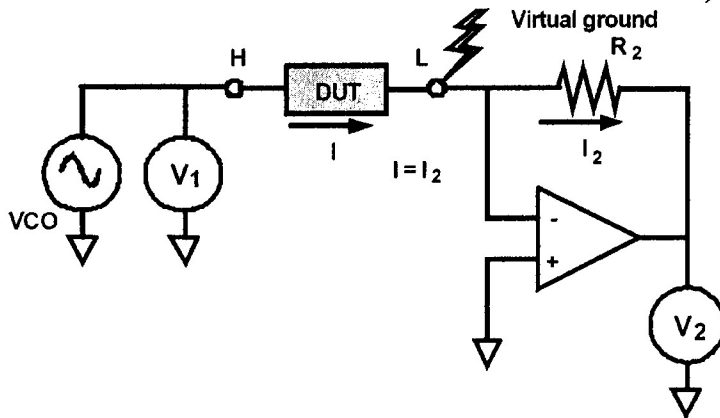

(Fig. 4)

6. (16%) Explain the operation principle of the basic bridge-controlled heater circuit.

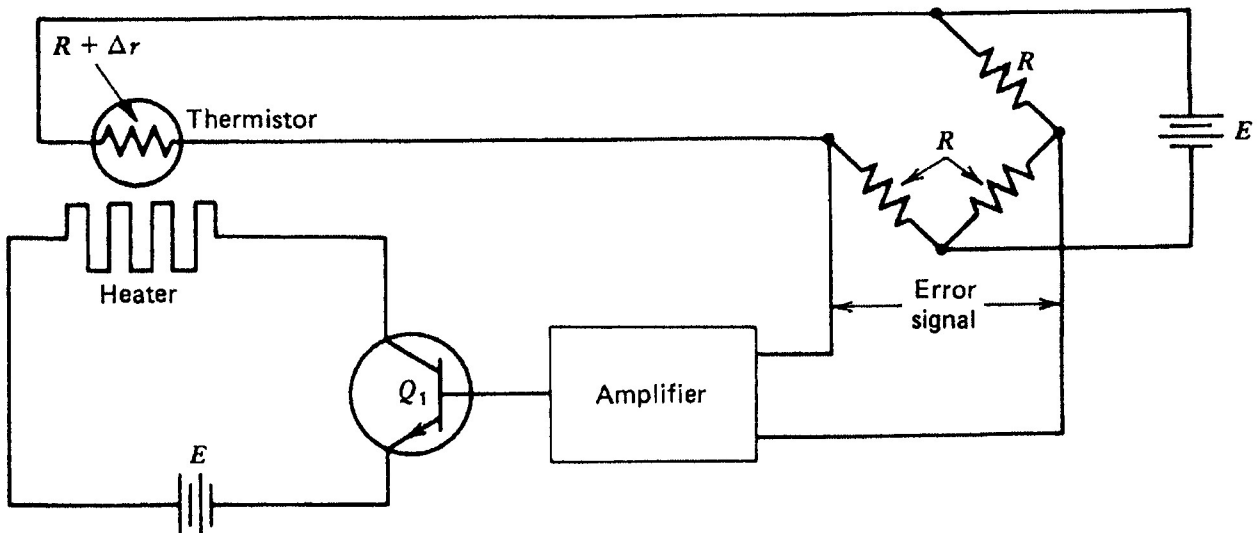


Fig. 5. Basic bridge-controlled heater circuit.