

系所組別： 生物醫學工程學系乙組

考試科目： 電子學

考試日期： 0219 · 節次： 1

※ 考生請注意：本試題 可 不可 使用計算機

1. In X-ray imaging system, the high voltage power supply is one of important components. Fig. 1 shows a circuit that may be extended to provide a dc voltage having higher multiples of input peak voltage. When excited by a sinusoid of amplitude  $V_p$ , and assuming ideal diodes, describe how this circuit works, and draw the waveform of the voltage across  $D_1$ . (20%)
2. For a  $pn$  junction in equilibrium at room temperature with the doping concentration  $N_A=10^{18}/\text{cm}^3$  and  $N_D=10^{16}/\text{cm}^3$ , the cross-sectional area  $A=10^{-4} \text{ cm}^2$ , and the intrinsic carrier density  $n_i=1.5 \times 10^{10}/\text{cm}^3$ , let the diffusion length of holes  $L_p=5 \mu\text{m}$ , the diffusion length of electrons  $L_n=10 \mu\text{m}$ , the diffusion constant of holes (in the  $n$  region)  $D_p=10 \text{ cm}^2/\text{V.s}$ , the diffusion constant of electrons (in the  $p$  region)  $D_n=18 \text{ cm}^2/\text{V.s}$ . If the  $pn$  junction is forward biased and conducting a current  $I=0.1 \text{ mA}$ , calculate (a) the saturation current  $I_S$ , (b) the forward-bias voltage  $V$ , and (c) the component of the current  $I$  due to hole injection and that due to electron injection across the junction. (20%)
3. Fig 2 shows two circuits for generating a constant current  $I_O=10 \mu\text{A}$  under a 10 V voltage supply. Assuming that  $V_{BE}$  is 0.7 V at a current of 1 mA and neglecting the effect of finite  $\beta$ , determine the values of resistances for  $R_1$ ,  $R_2$ , and  $R_3$ . (15%)
4. For a differential amplifier as shown in Fig. 3 and neglecting the transistor  $r_o$ , calculate the CMRR if there is a mismatch  $\Delta R_C$  between the two collector resistances (i.e.,  $Q_1$  has  $R_C$ , and  $Q_2$  has  $R_C+\Delta R_C$ ). (15%)
5. A capacitively coupled amplifier has a midband gain of 100 V/V, a single high-frequency pole at 10 kHz, and a single low-frequency pole at 100 Hz. If negative feedback is employed so that the midband gain is reduced to 10, determine the upper and lower 3-dB frequencies of the closed-loop gain. (10%)
6. The Antoniou inductance-simulation circuit is often used to realize the second-order active filters. Design a bandpass filter using the Antoniou inductance-simulation circuit and derive its transfer function with the center-frequency gain  $K$ . (20%)

(背面仍有題目,請繼續作答)

系所組別： 生物醫學工程學系乙組

考試科目： 電子學

考試日期： 0219，節次： 1

※ 考生請注意：本試題 可 不可 使用計算機

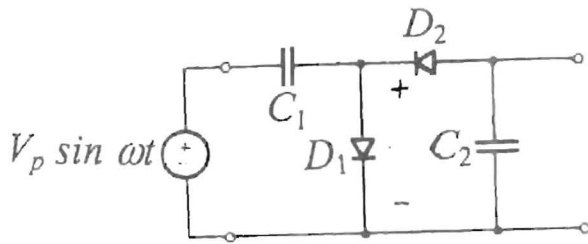


Fig. 1

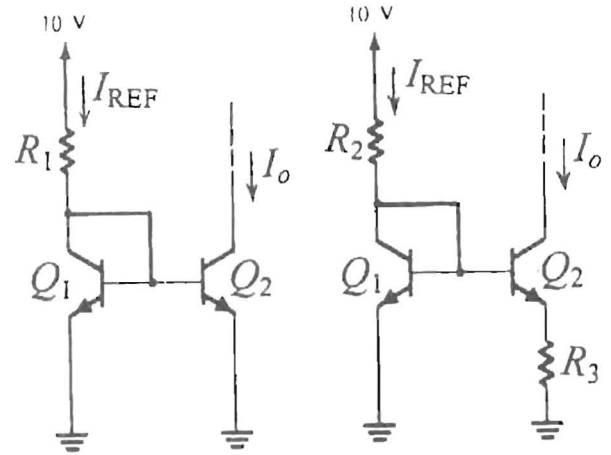


Fig. 2

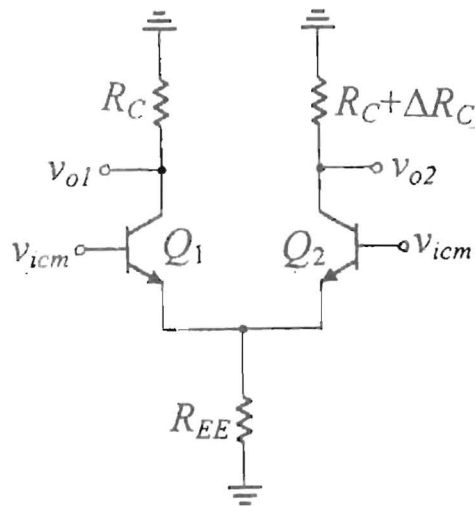


Fig. 3