

國立成功大學  
110學年度碩士班招生考試試題

編 號： 156

系 所： 生物醫學工程學系

科 目： 電子學

日 期： 0202

節 次： 第 2 節

備 註： 可使用計算機

※ 考生請注意：本試題可使用計算機。請於答案卷(卡)作答，於本試題紙上作答者，不予計分。

1. (15%) Please explain the following terminologies:
  - a) Miller compensation, b) SRAM and DRAM, c) TTL logic, d) Transconductance, e) Mass action law
2. (15%) Please answer following questions for the circuit shown in Figure 1.
  - i. (5 pts) Please derive the transfer function  $V_{out}(s)/V_{in}(s)$ .
  - ii. (5 pts) Please represent the  $V_{out}(t)$  in terms of R, C, and  $V_{in}(t)$ .
  - iii. (5 pts) Please explain what kind of applications can be applied by the circuit shown in Figure 1.
3. (5%) Please derive the differential gain for the circuit shown in Figure 2.
4. (10%) The lattice structure of Germanium is the same as silicon (diamond structure), the atomic weight of Germanium is 72.59, and the lattice constant is 0.564 nm. Find the density ( $\text{g}/\text{cm}^3$ ) (3%), atomic density ( $\text{atoms}/\text{cm}^3$ ) (3%), and the spacing between nearest-neighbor atoms in Germanium (4%).
5. (10%) Use the equation (E1) to (E3) to show that an *npn* transistor operated in saturation region exhibits a collector-to-emitter voltage,  $V_{CESat}$ , given by

$$V_{CESat} = V_T \ln \left[ \left( \frac{I_{SC}}{I_S} \right) \frac{1 + \beta_{forced}}{1 - \beta_{forced}/\beta} \right]$$

Use this relationship to evaluate  $V_{CESat}$  for  $\beta_{forced} = 50, 10, 5,$  and  $1$  for a transistor with  $\beta = 100$  and with a CBJ area 100 times that of the EBJ. Present your results in a table.

$$i_C = I_S e^{v_{BE}/V_T} - I_{SC} e^{v_{BC}/V_T} \tag{E1}$$

$$i_B = \frac{I_S}{\beta} e^{v_{BE}/V_T} + I_{SC} e^{v_{BC}/V_T} \tag{E2}$$

$$\beta_{forced} = \left. \frac{i_C}{i_B} \right|_{\text{saturation}} \leq \beta \tag{E3}$$

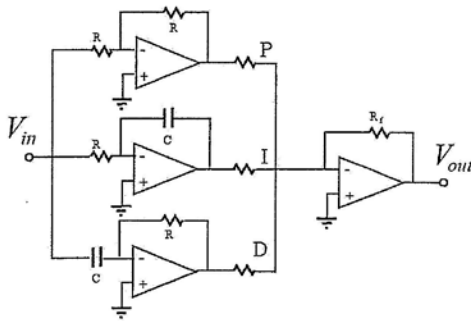


Figure 1

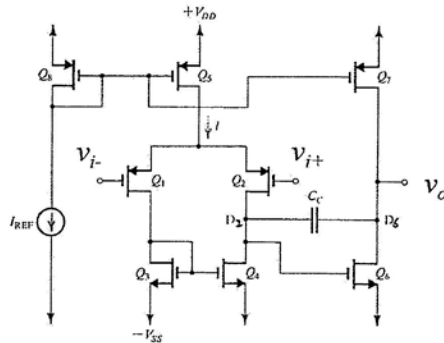


Figure 2

6. (10%) Please find the output resistance of the double-cascode current mirror shown in Figure 3.
7. (10%) Find the voltages at all nodes and the currents through all branches in the circuit of Figure 4. Assume  $|V_{BE}| = 0.7\text{ V}$  and  $\beta = \infty$ .

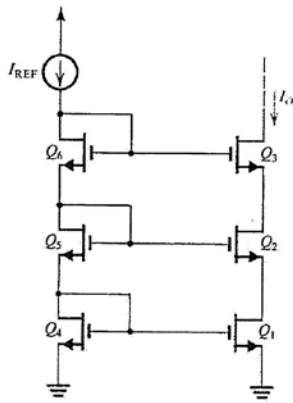


Figure 3

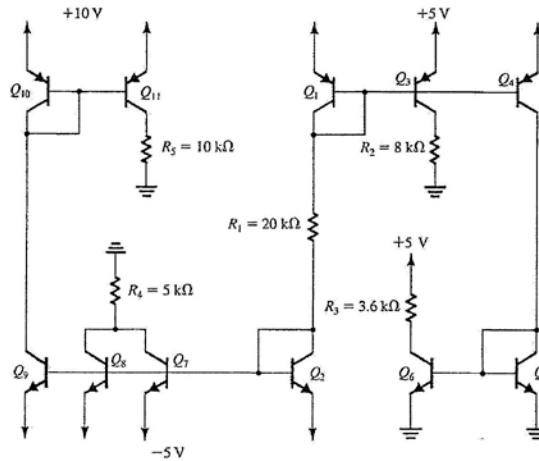


Figure 4

8. (15%) Please answer the following questions related to the emitter follower shown in Figure 5.
- (5 pts) Please draw the high-frequency equivalent circuit of the emitter follower shown in Figure 5.
  - (10 pts) Please derive the transfer function of the emitter follower shown in Figure 5.

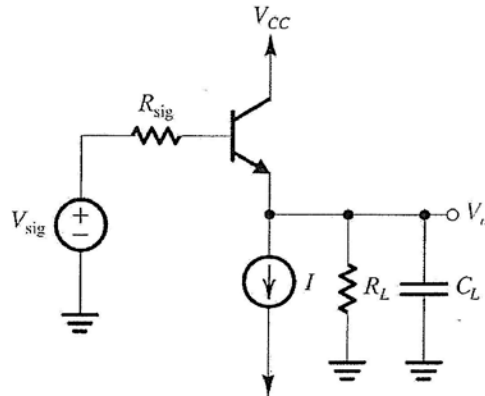


Figure 5

9. (10%) Figure 6 shows a discrete-circuit amplifier. The input signal  $v_{sig}$  is coupled to the gate through a very large capacitor (shown as infinite). The transistor source is connected to the ground at signal frequencies via a very large capacitor (shown as infinite). The output voltage signal that develops at the drain is coupled to a load resistance via a very large capacitor (shown as infinite). All capacitors behave as short circuits for signals and as open circuits for DC.
- (2 pts) If the transistor has  $V_t = 1$  V, and  $k_n = 4$  mA/V<sup>2</sup>, verify that the bias circuit establishes  $V_{GS} = 1.5$  V,  $I_D = 0.5$  mA, and  $V_D = +0.7$  V. That is, assume these values, and verify that they are consistent with the values of the circuit components and the device parameters.
  - (2 pts) Find  $g_m$  and  $r_o$  if  $V_A = 100$  V.
  - (2 pts) Draw a complete small-signal equivalent circuit for the amplifier, assuming all capacitors behave as short circuits as signal frequencies.
  - (4 pts) Find  $R_{in}$ ,  $v_{gs}/v_{sig}$ ,  $v_o/v_{gs}$ , and  $v_o/v_{sig}$ .

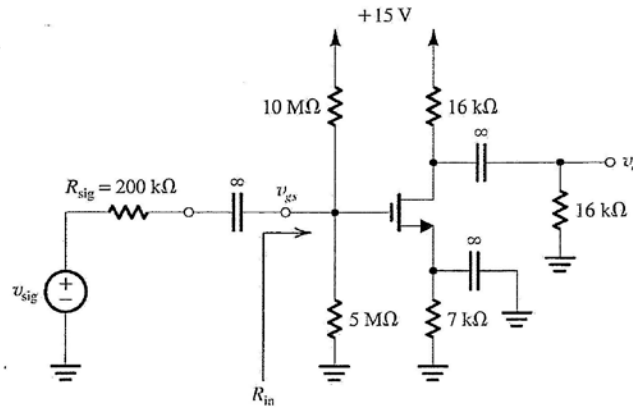


Figure 6